



# Computers

Janik Euskirchen

6


Memory

Memory (Random Access Memory, RAM)

  


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

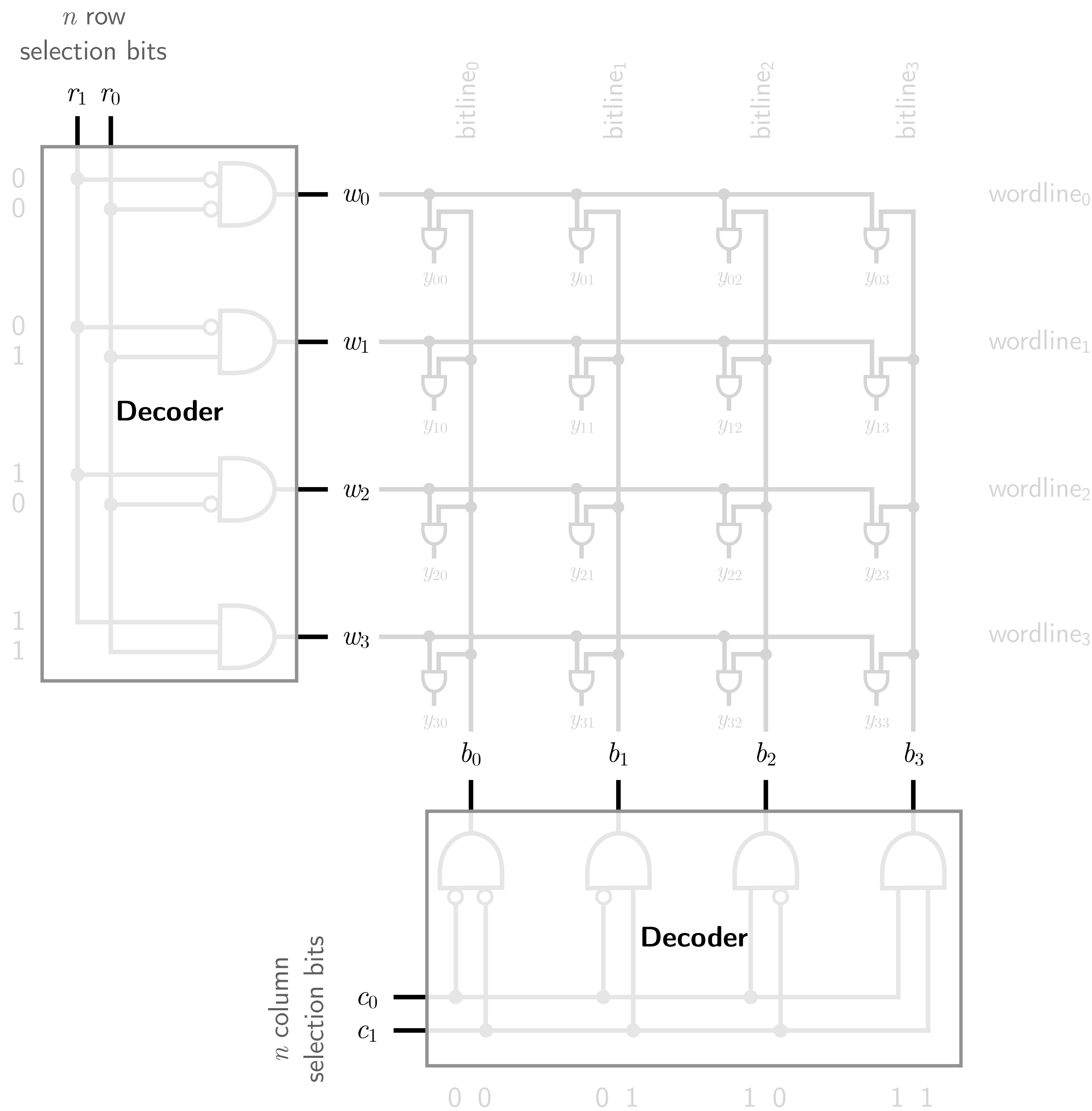


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

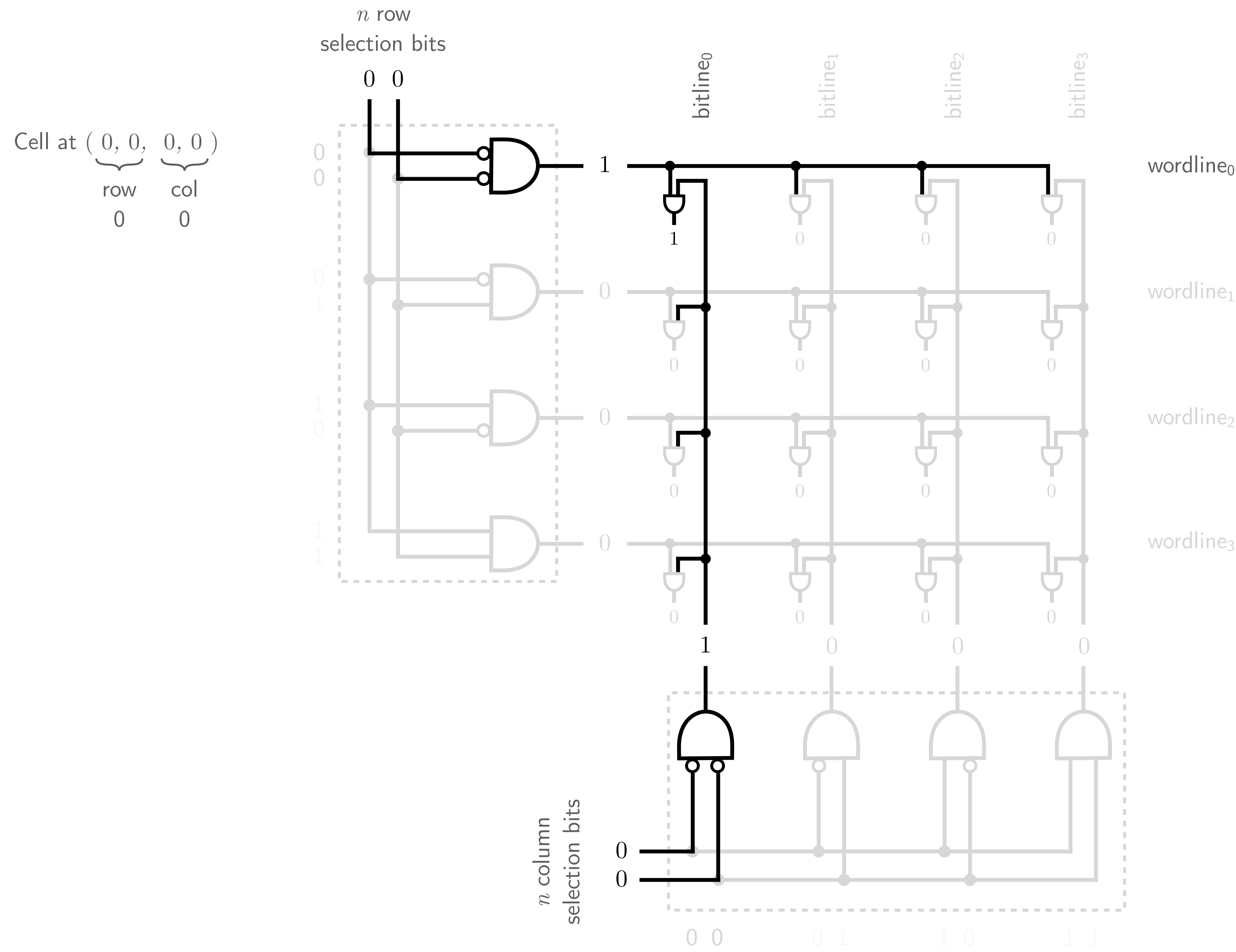


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

## Memory (Random Access Memory, RAM)

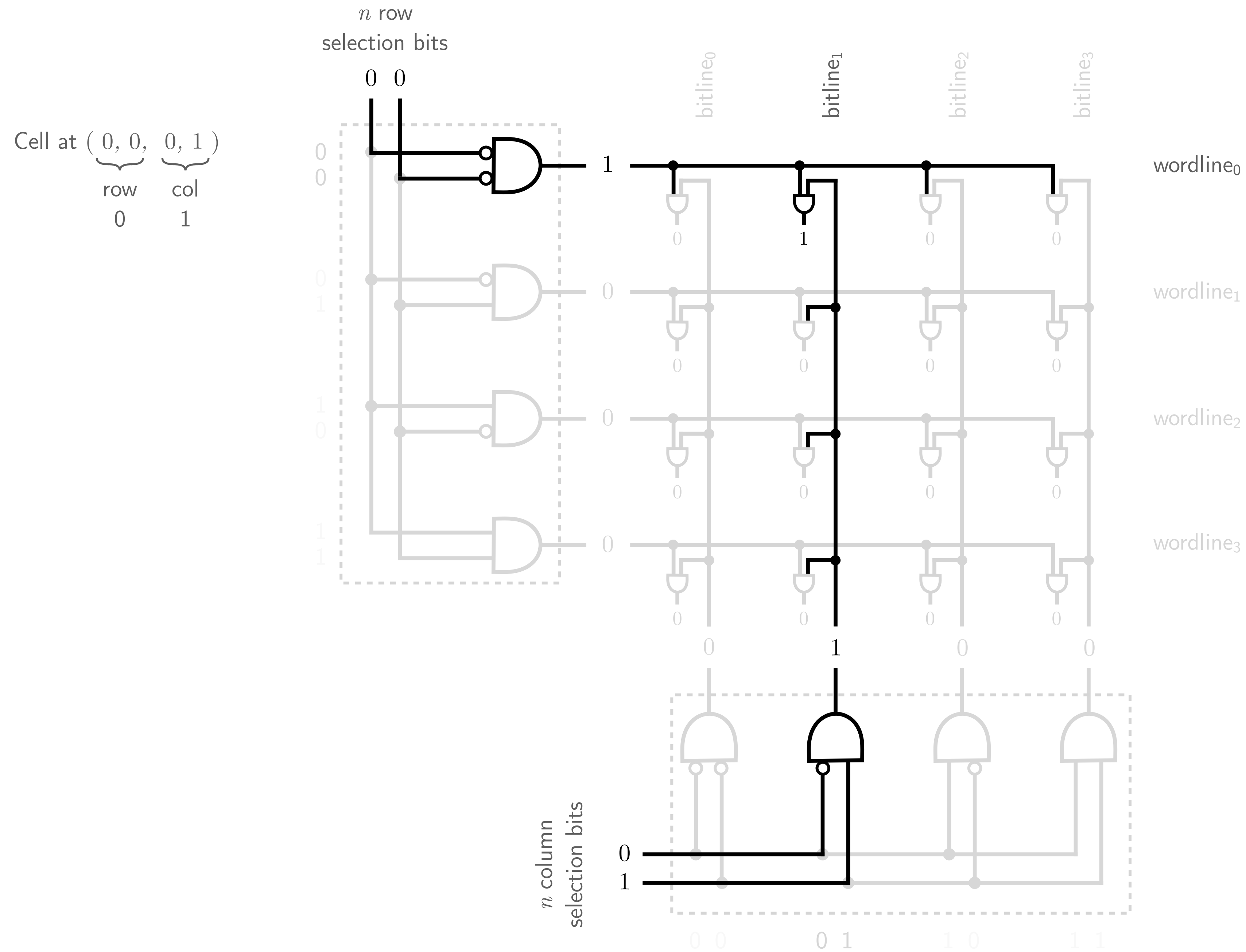


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

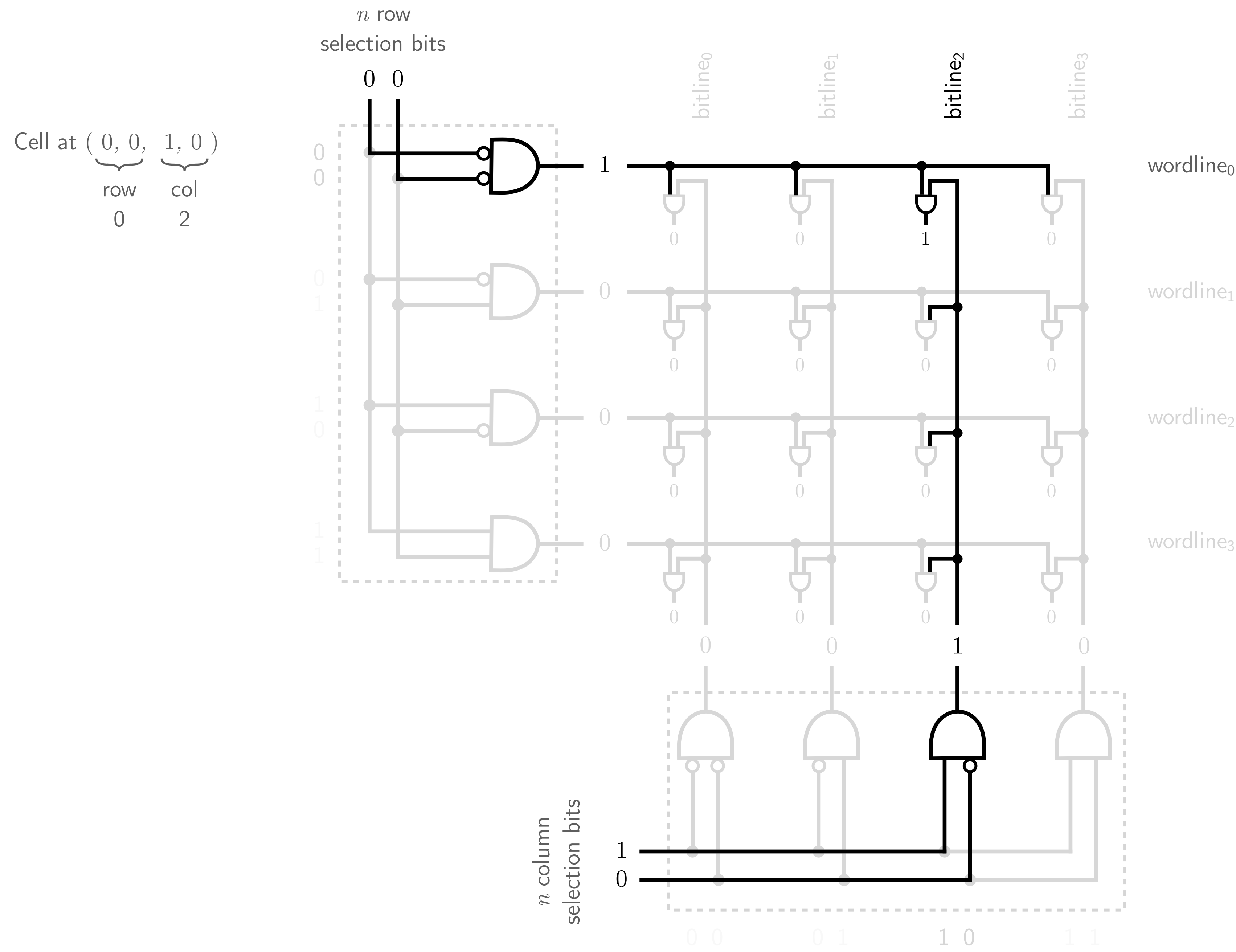

$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$


Memory (Random Access Memory, RAM)

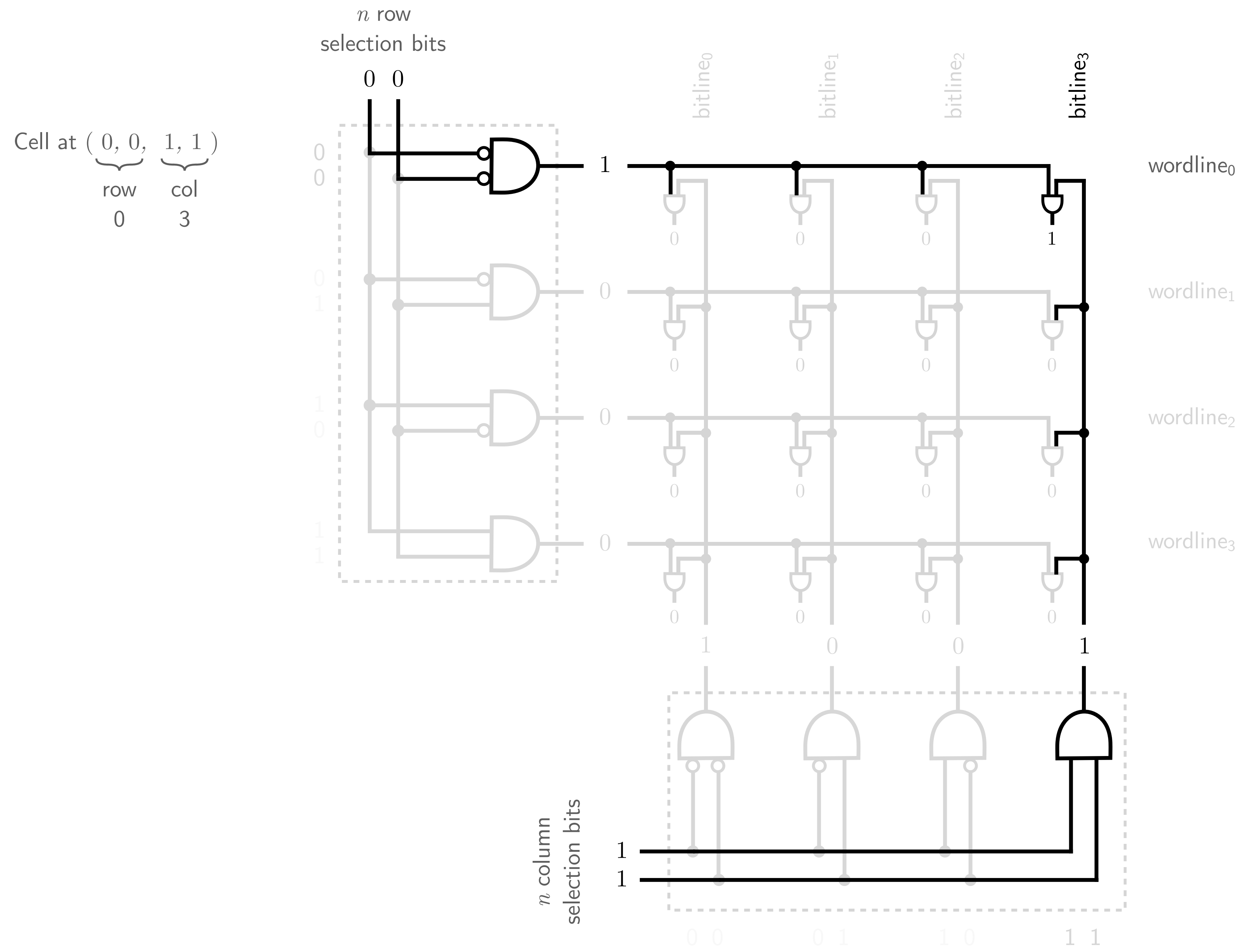

$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$




Memory (Random Access Memory, RAM)

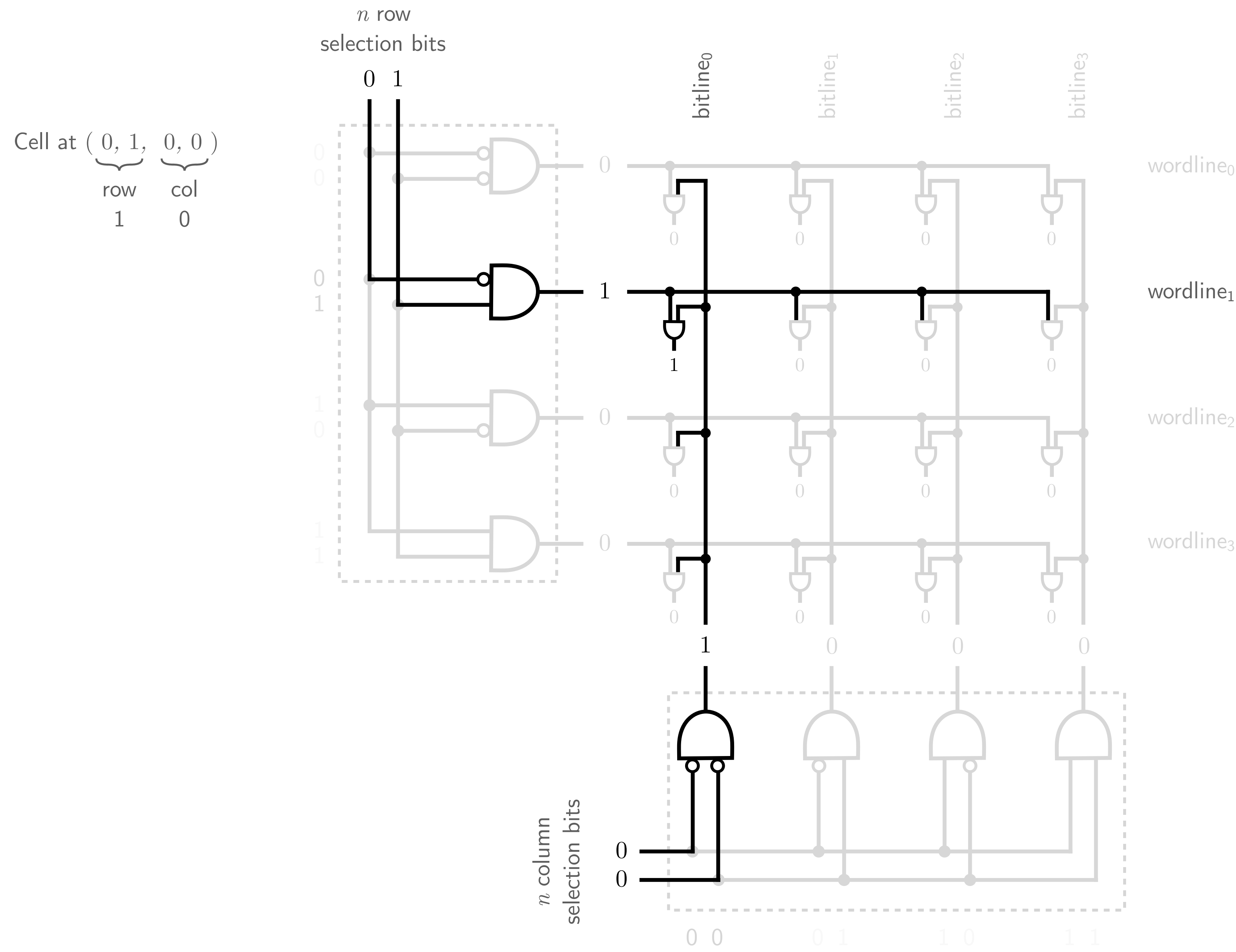


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

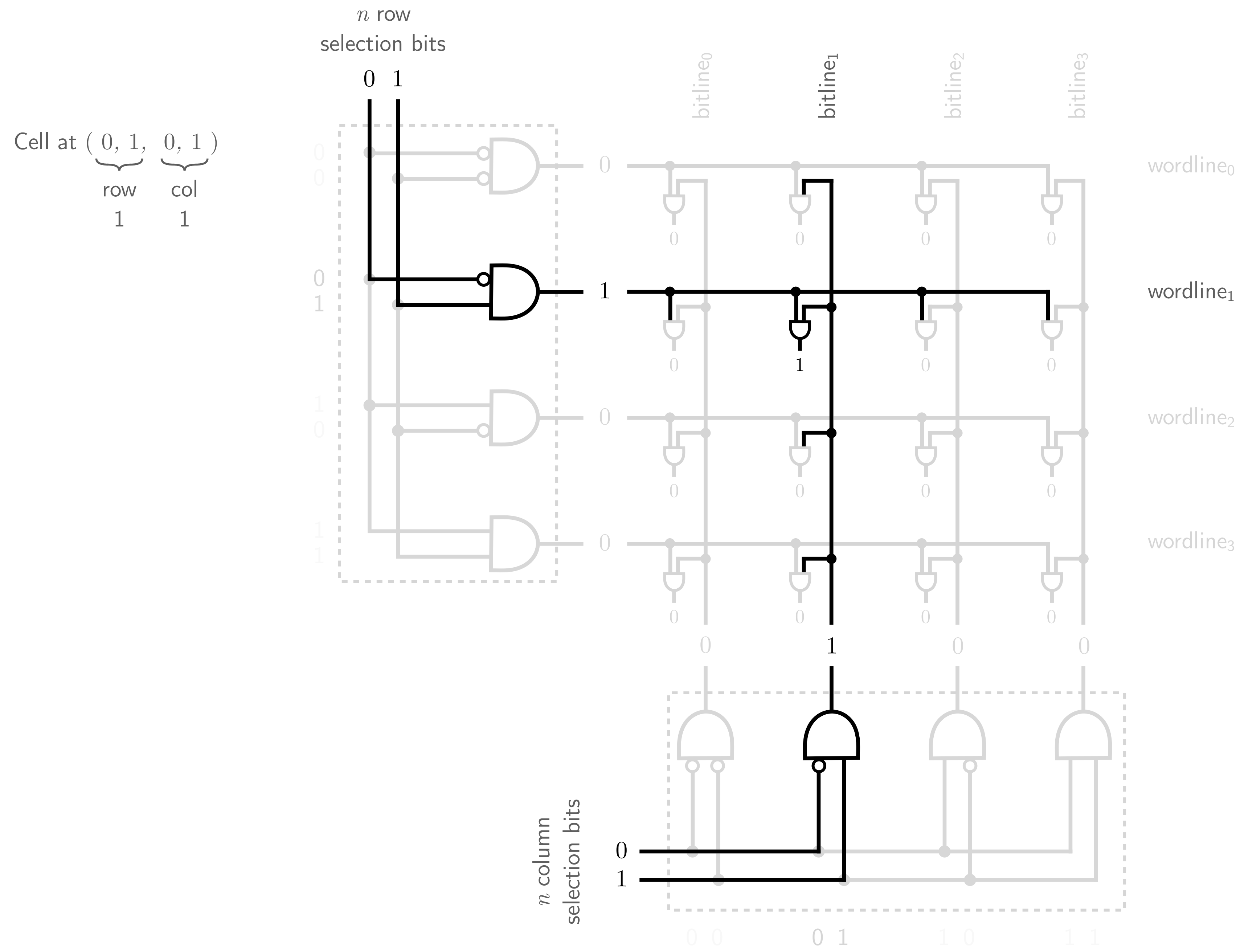


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

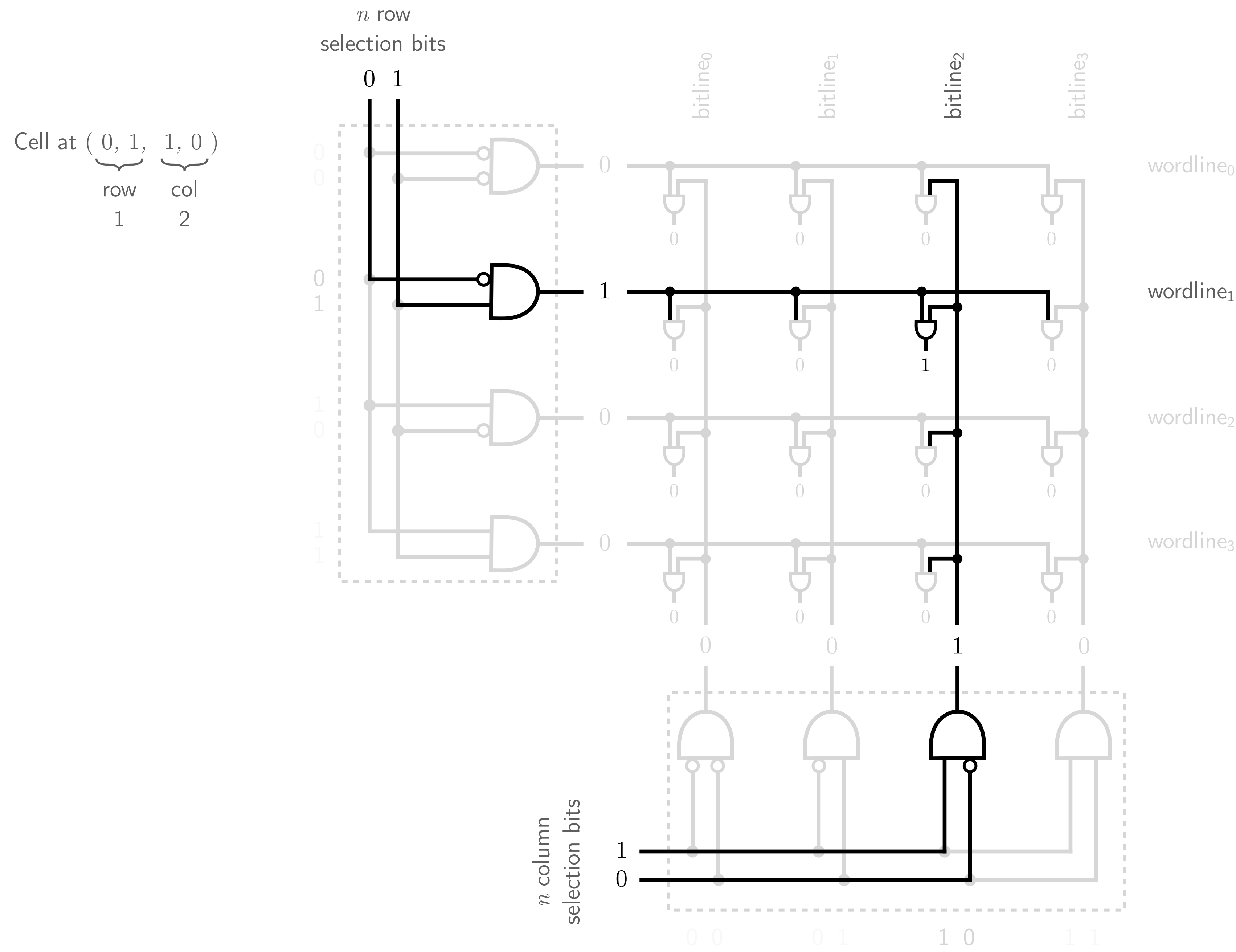


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

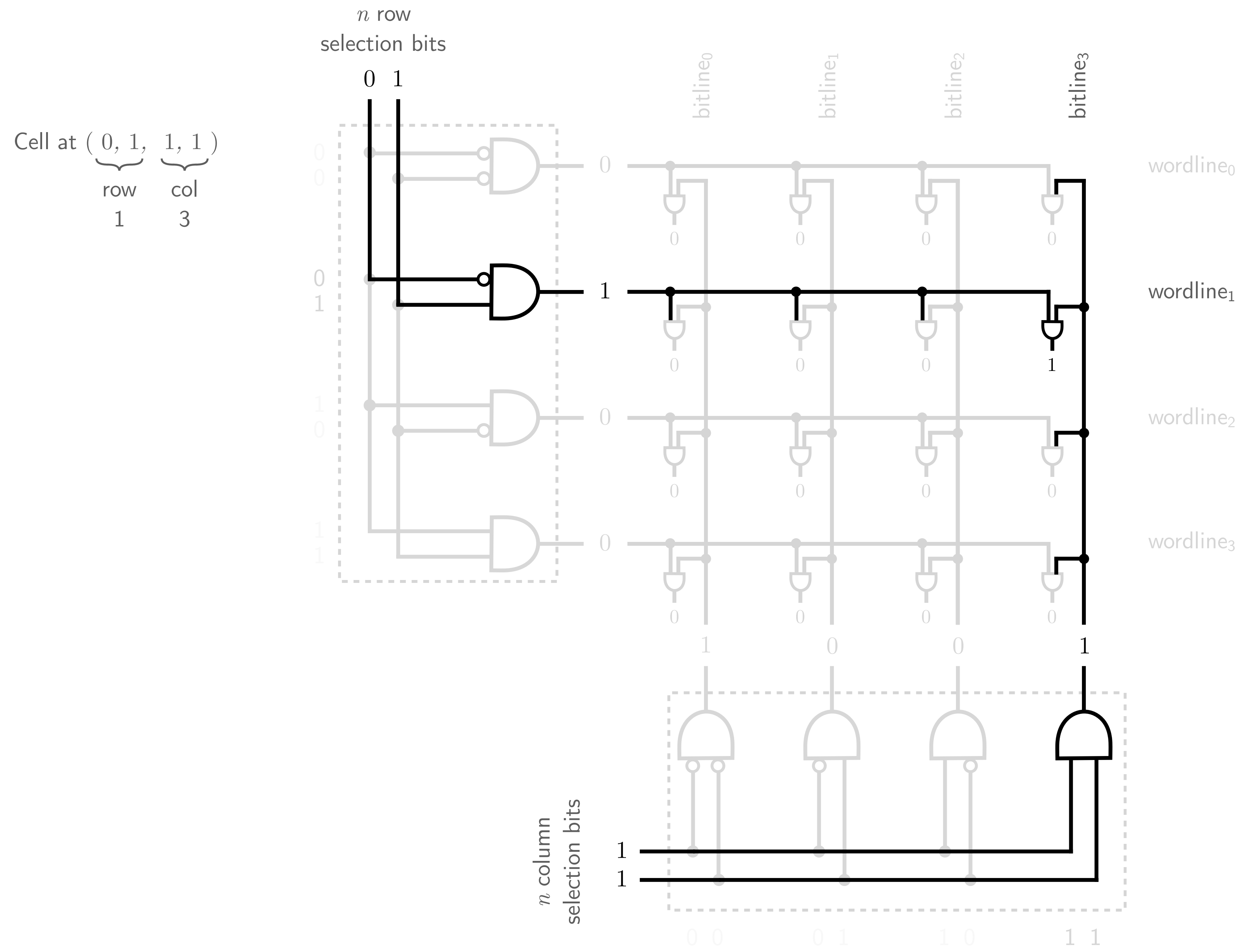


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

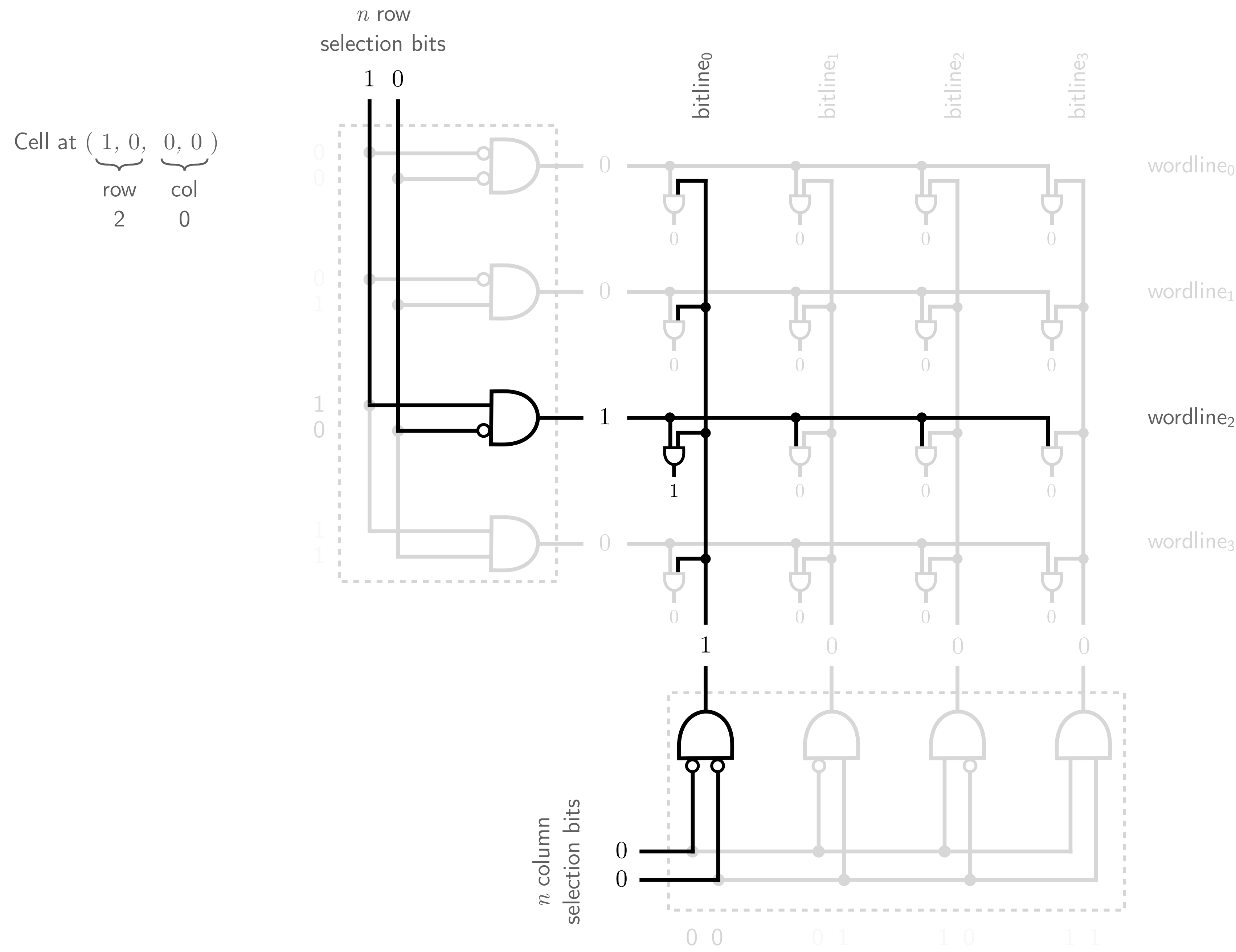


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

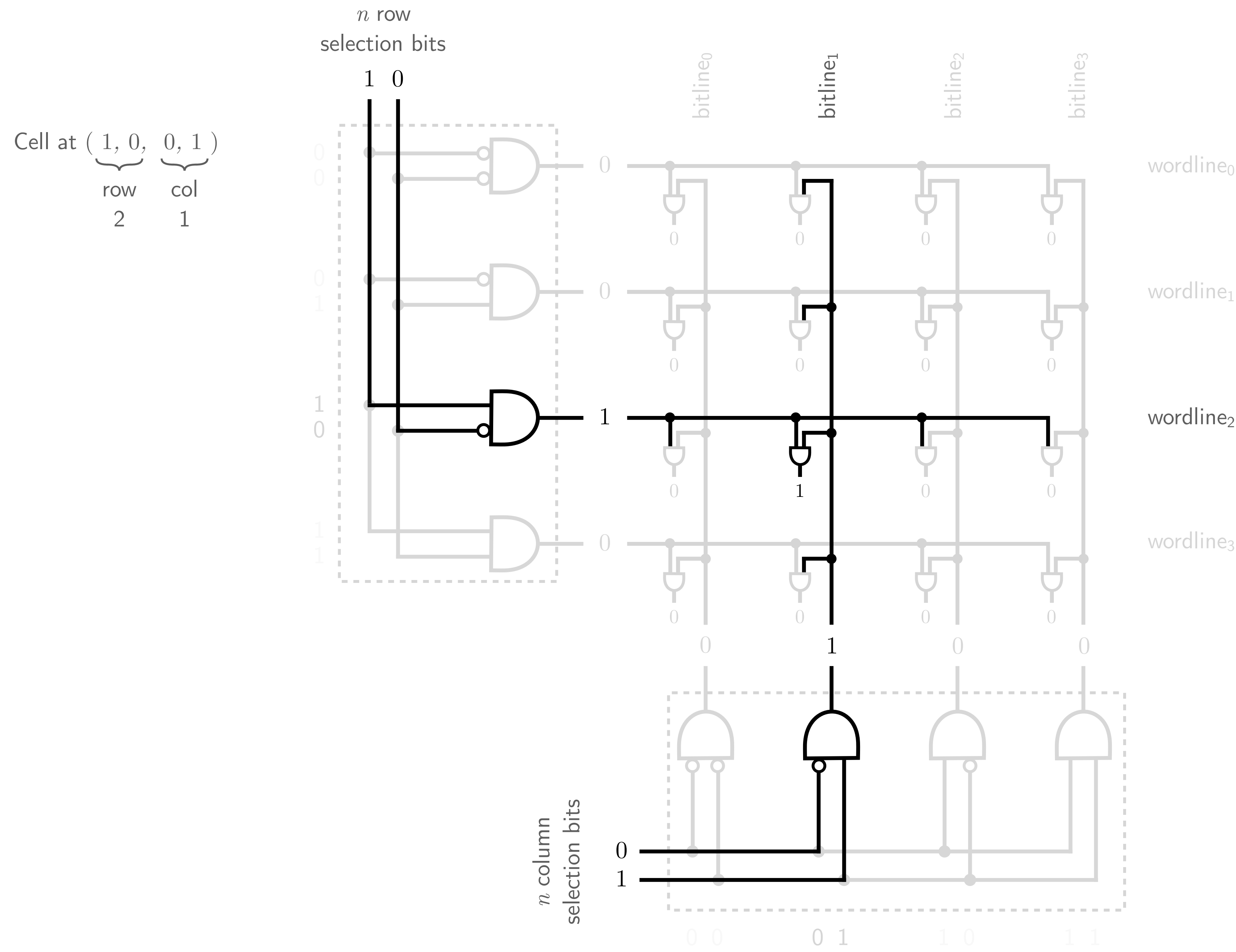


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

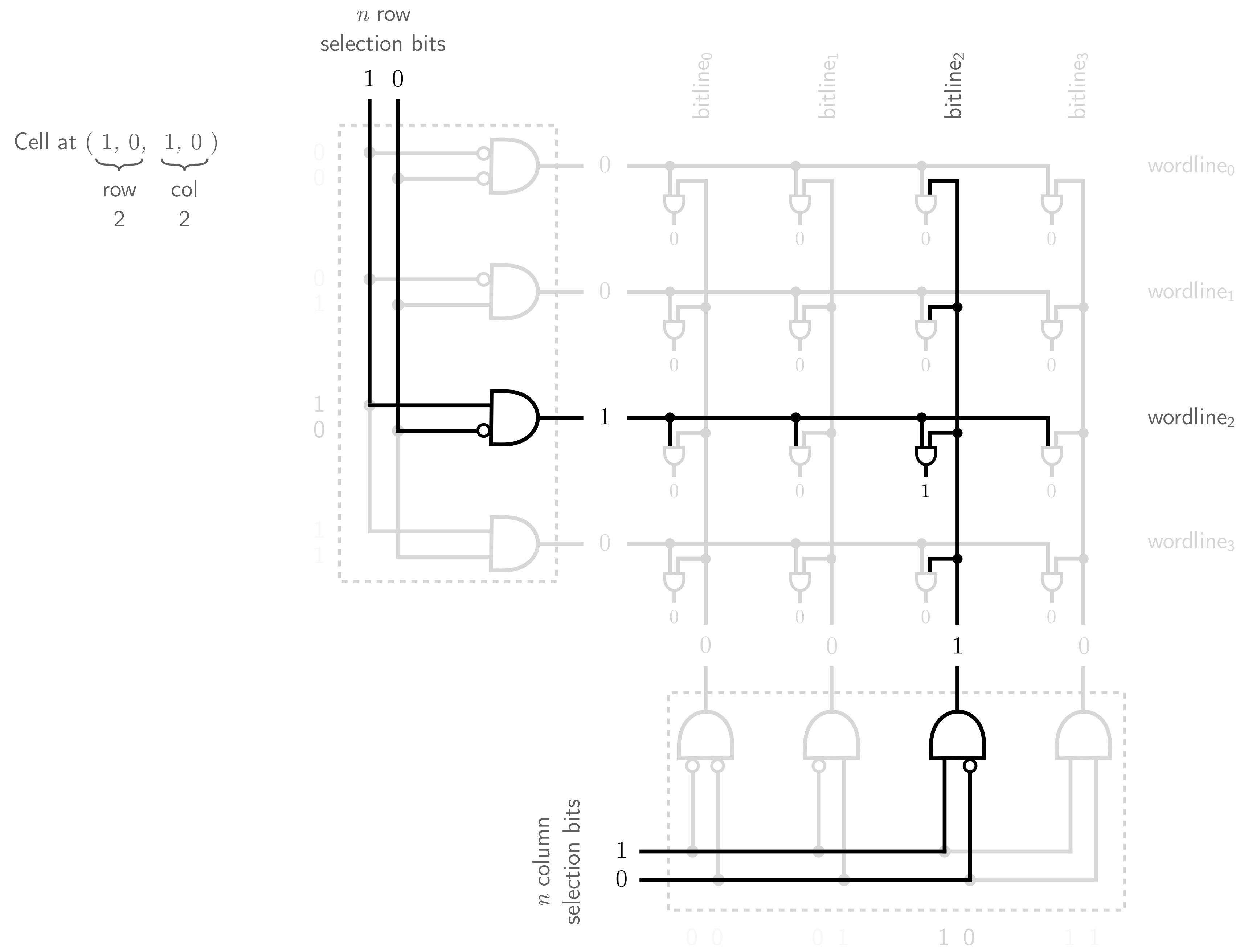

$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$


Memory (Random Access Memory, RAM)

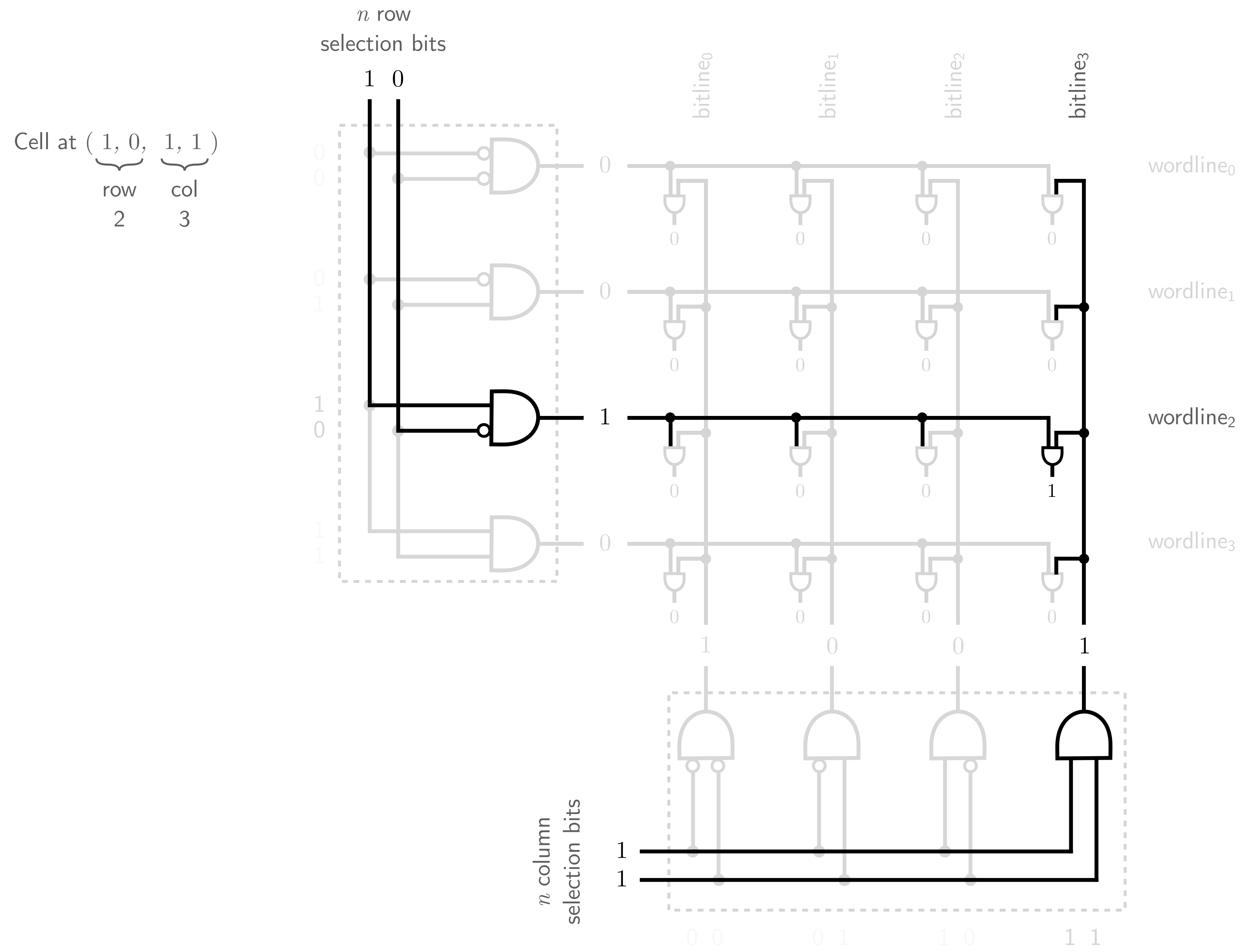

$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$




## Memory (Random Access Memory, RAM)

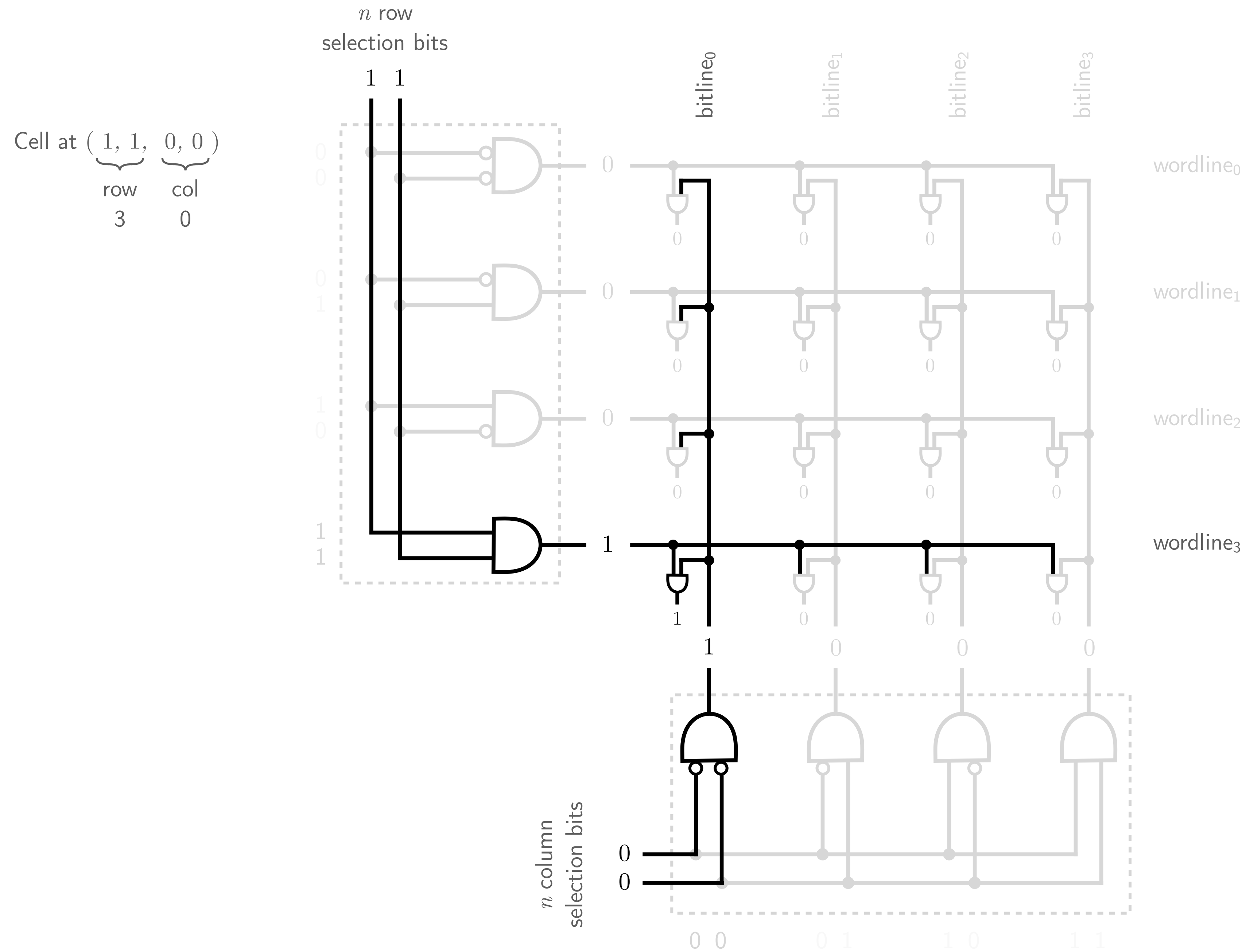


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

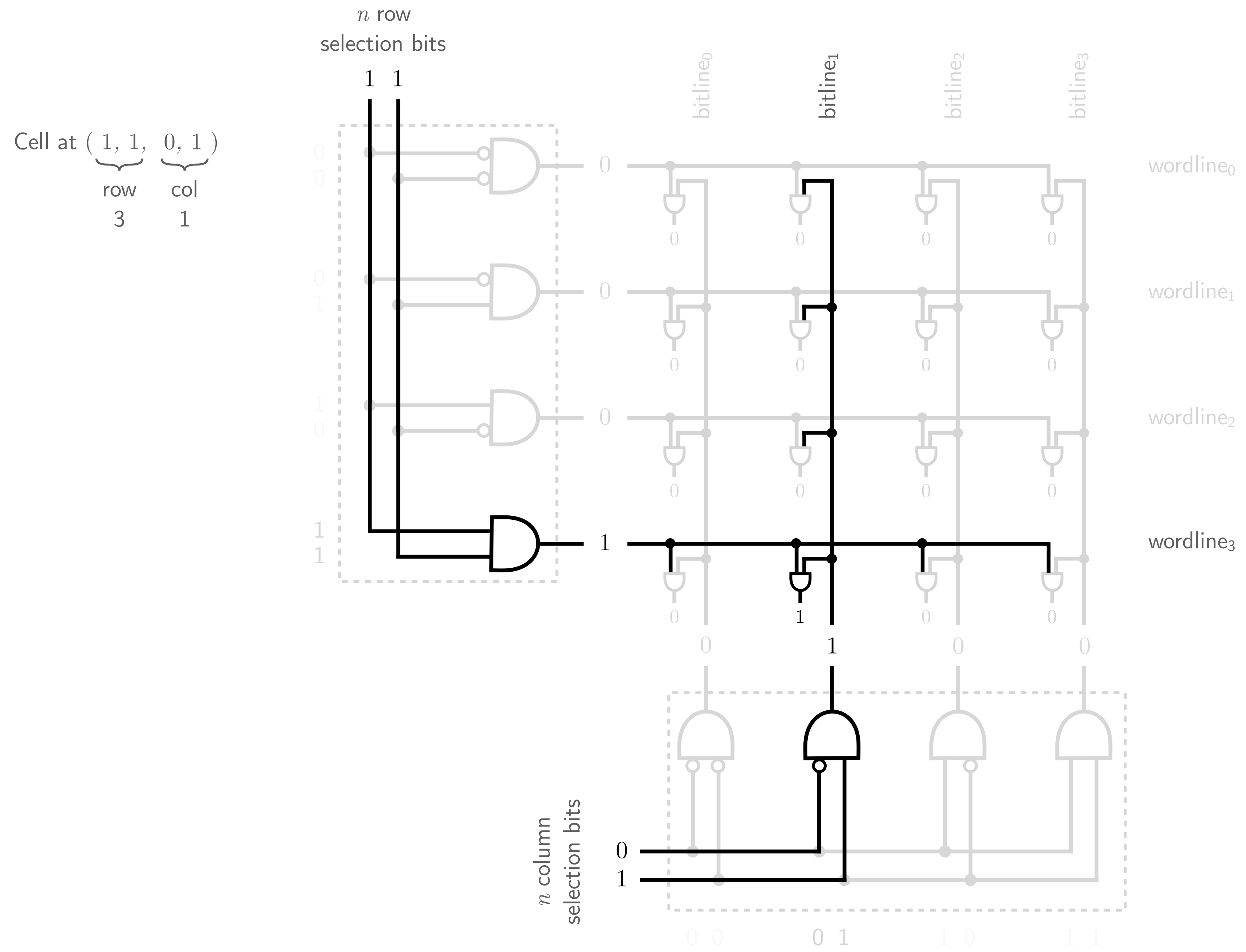


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

## Memory (Random Access Memory, RAM)

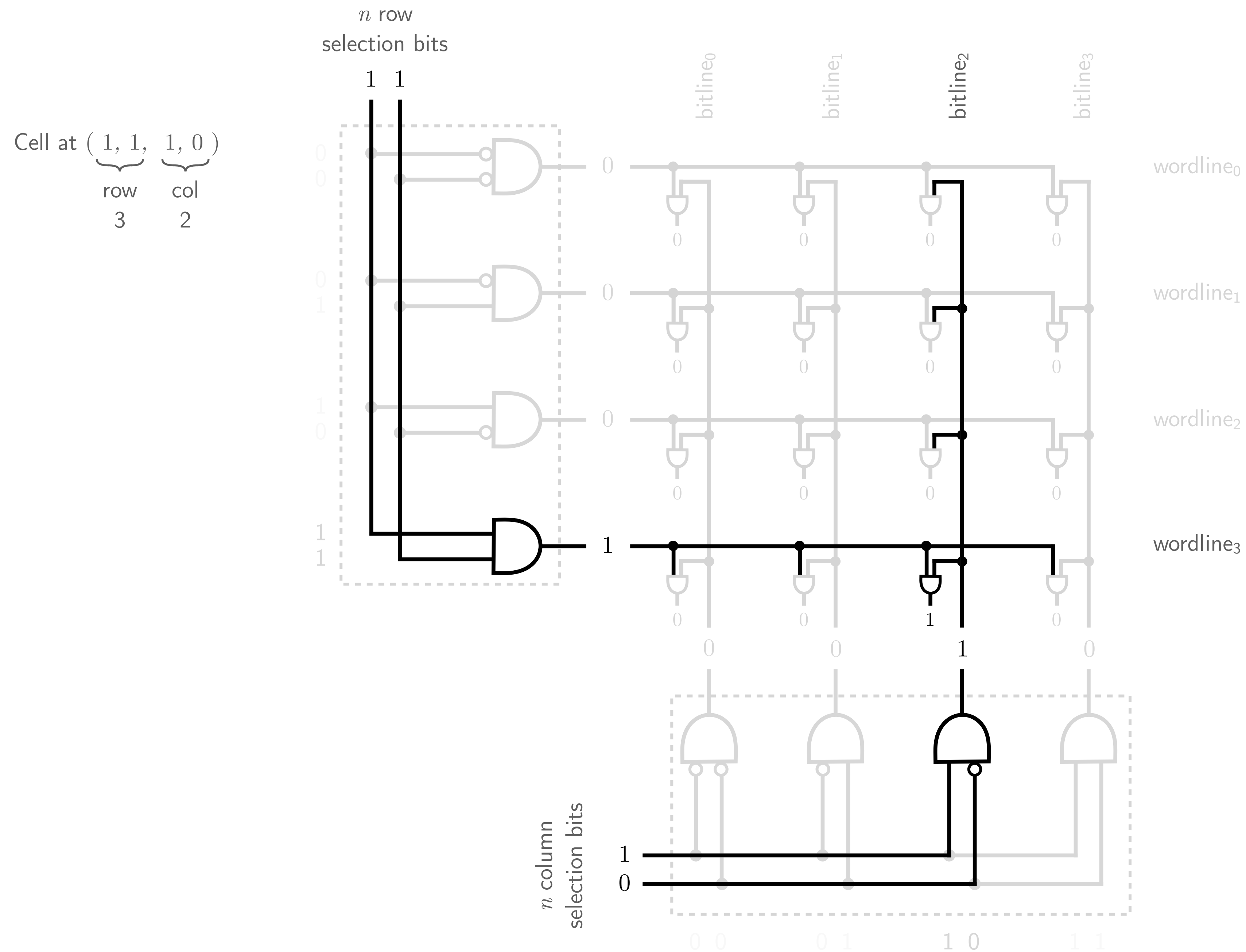


$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$

Memory (Random Access Memory, RAM)

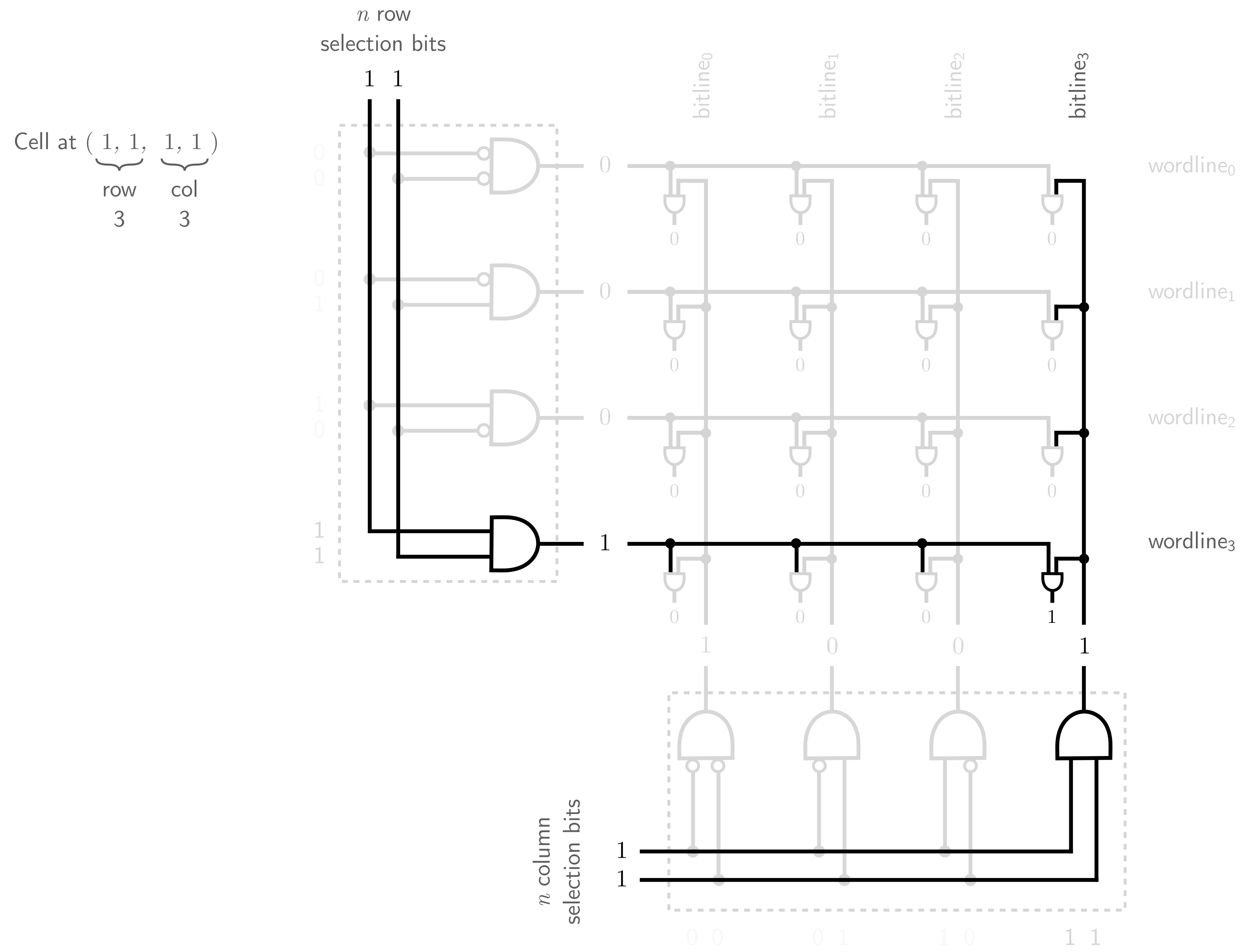

$r_1$	$r_0$	$c_1$	$c_0$	$Q$
0	0	0	0	$y_{00}$
0	0	0	1	$y_{01}$
0	0	1	0	$y_{02}$
0	0	1	1	$y_{03}$
0	1	0	0	$y_{10}$
0	1	0	1	$y_{11}$
0	1	1	0	$y_{12}$
0	1	1	1	$y_{13}$
1	0	0	0	$y_{20}$
1	0	0	1	$y_{21}$
1	0	1	0	$y_{22}$
1	0	1	1	$y_{23}$
1	1	0	0	$y_{30}$
1	1	0	1	$y_{31}$
1	1	1	0	$y_{32}$
1	1	1	1	$y_{33}$


Memory (Random Access Memory, RAM)

 

Only memory cell at  $(r, c)$  is active

address	4 bits (2 row bits, 2 col bits)
ENABLE_READ	1 bit
ENABLE_WRITE	1 bit
data	1 bit

Memory (Random Access Memory, RAM)

 


Only memory cell at  $(r, c)$  is active

Only if ENABLE bit is 1

address	4 bits (2 row bits, 2 col bits)
ENABLE_READ	1 bit
ENABLE_WRITE	1 bit
data	1 bit

Memory (Random Access Memory, RAM)

 


Only memory cell at  $(r, c)$  is active

Only if ENABLE\_READ bit is 1

Only if ENABLE\_WRITE bit is 1

address	4 bits (2 row bits, 2 col bits)
ENABLE_READ	1 bit
ENABLE_WRITE	1 bit
data	1 bit

Memory (Random Access Memory, RAM)

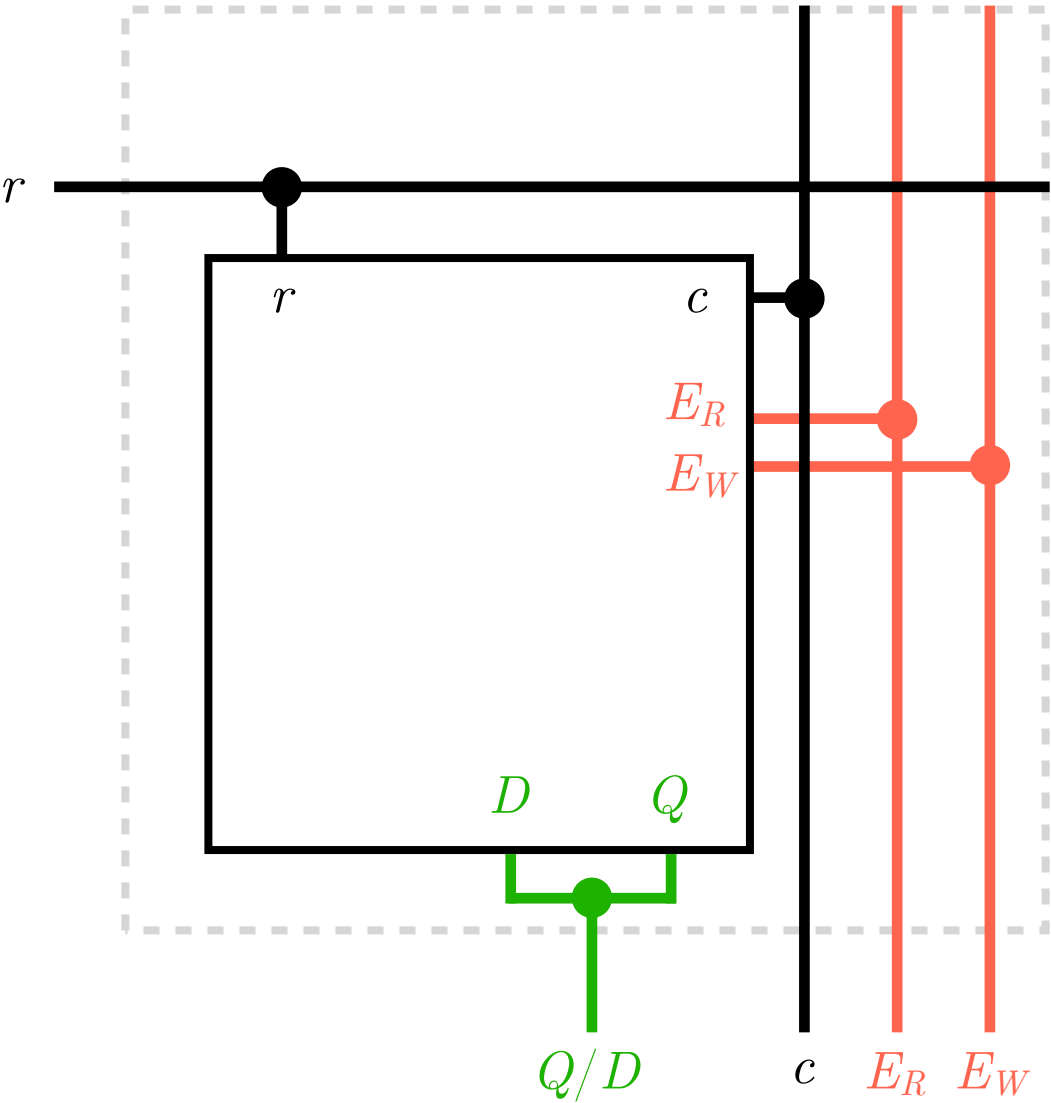

Only memory cell at  $(r, c)$  is active


Only if ENABLE\_READ bit is 1

Only if ENABLE\_WRITE bit is 1

address	4 bits (2 row bits, 2 col bits)
ENABLE_READ	1 bit
ENABLE_WRITE	1 bit
data	1 bit





Memory (Random Access Memory, RAM)

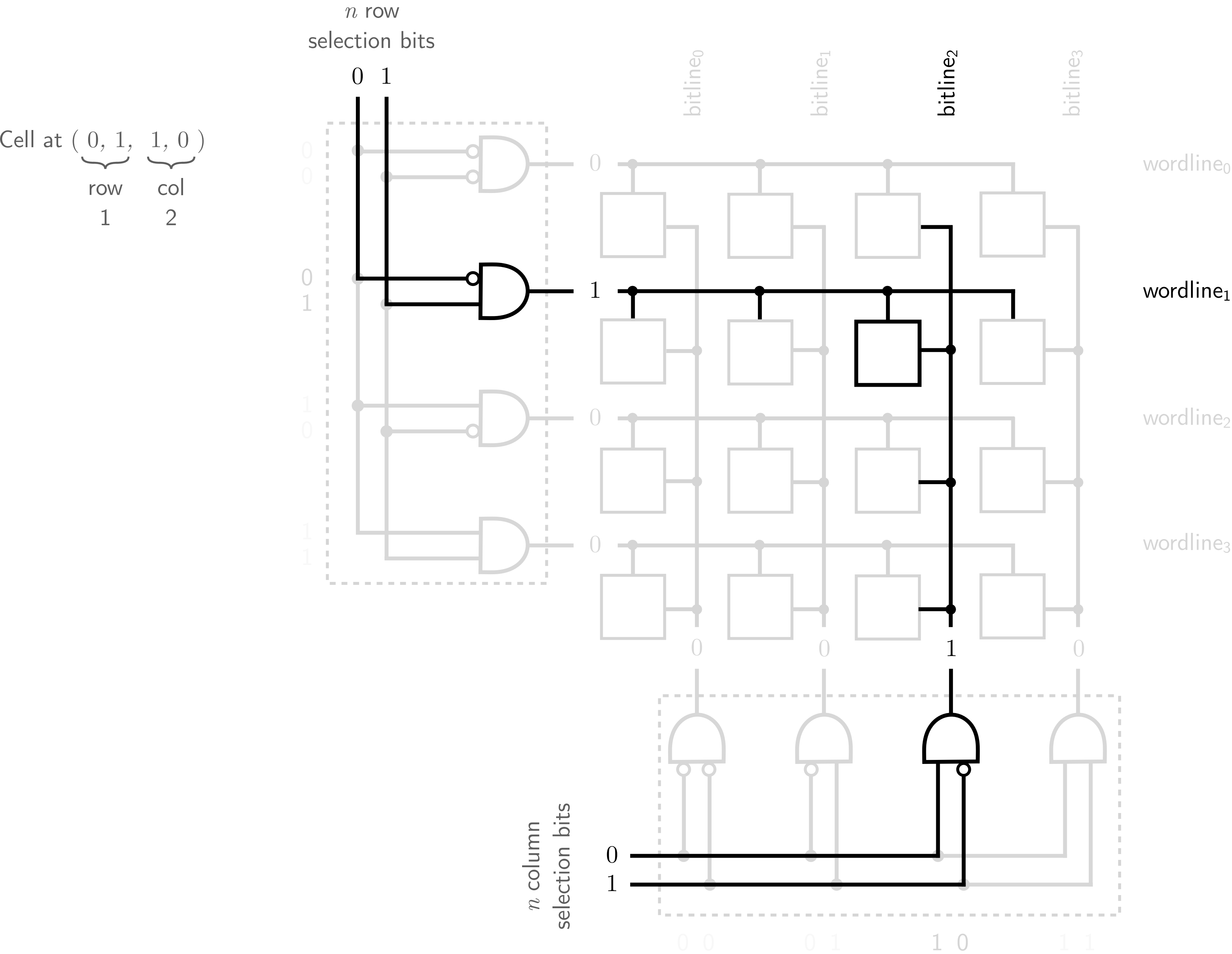

Memory (Random Access Memory, RAM)


Cell at ( 0, 1, 1, 0 )  
row 1 col 2

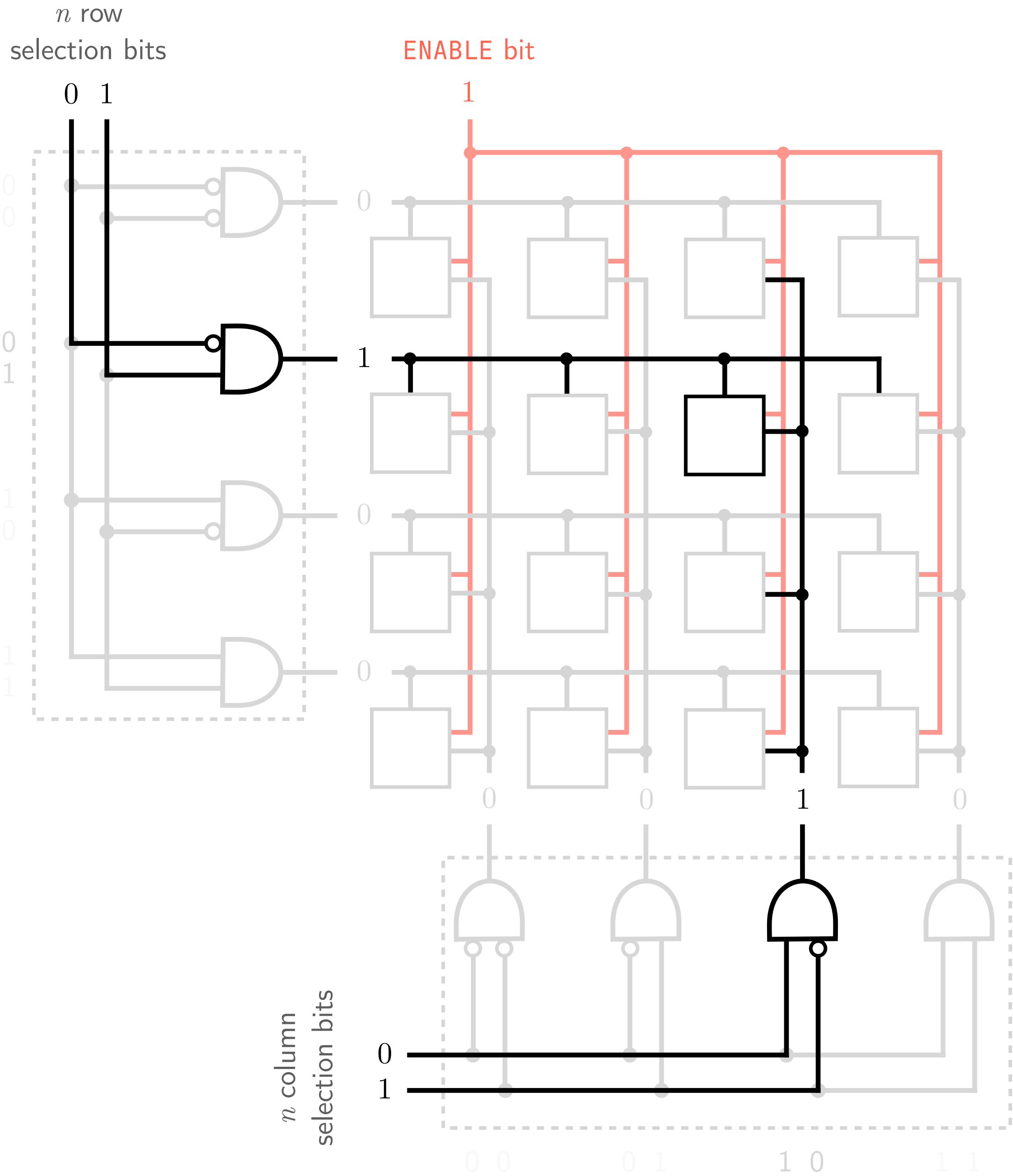

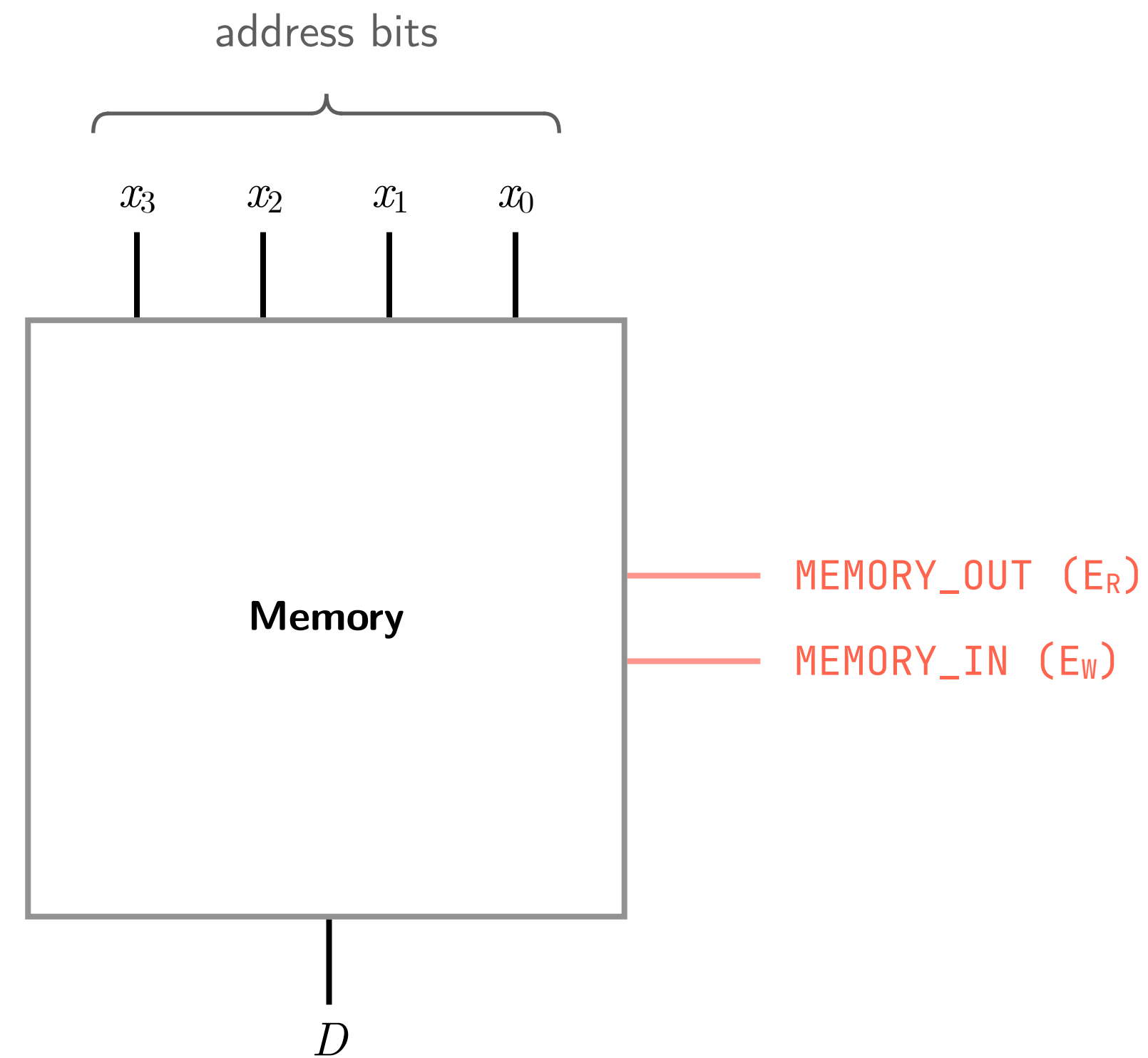


The design we have seen so far only stores 1 bit, but we can use 8 copies of this system to store 1 byte. Each bit in a byte has the same address in its respective 'copy'.

Bit interleaving

 


## Bit interleaving

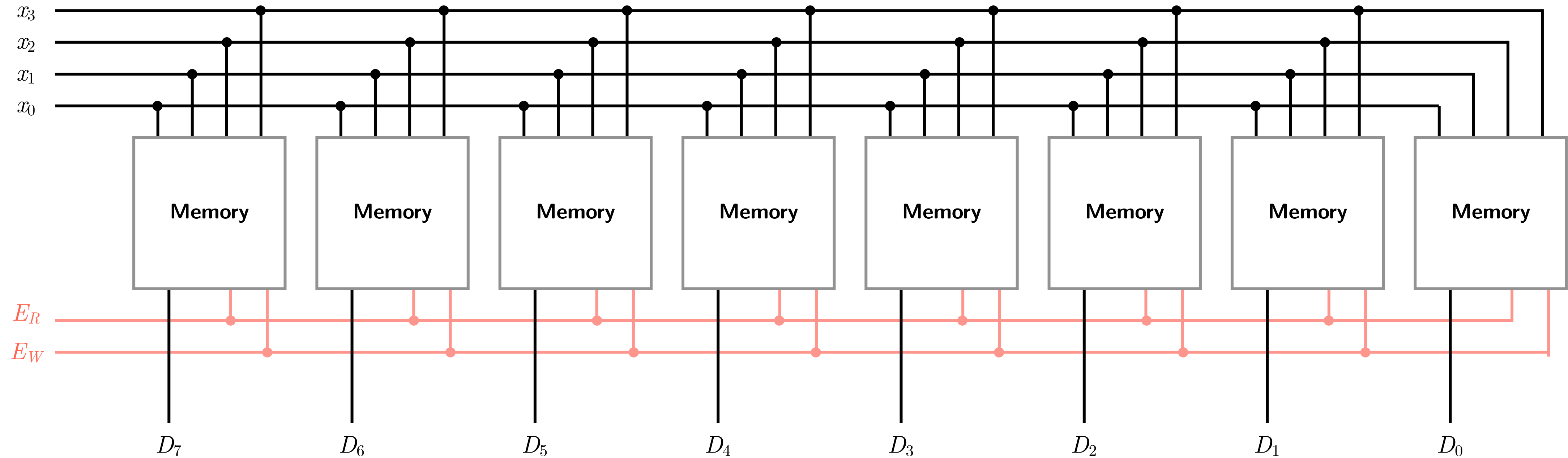

Each bit in the **byte**  $D_7D_6D_5D_4D_3D_2D_1D_0$  is stored in a separate matrix at the same address.


This is just one of many possible ways of organizing memory.

Bit interleaving

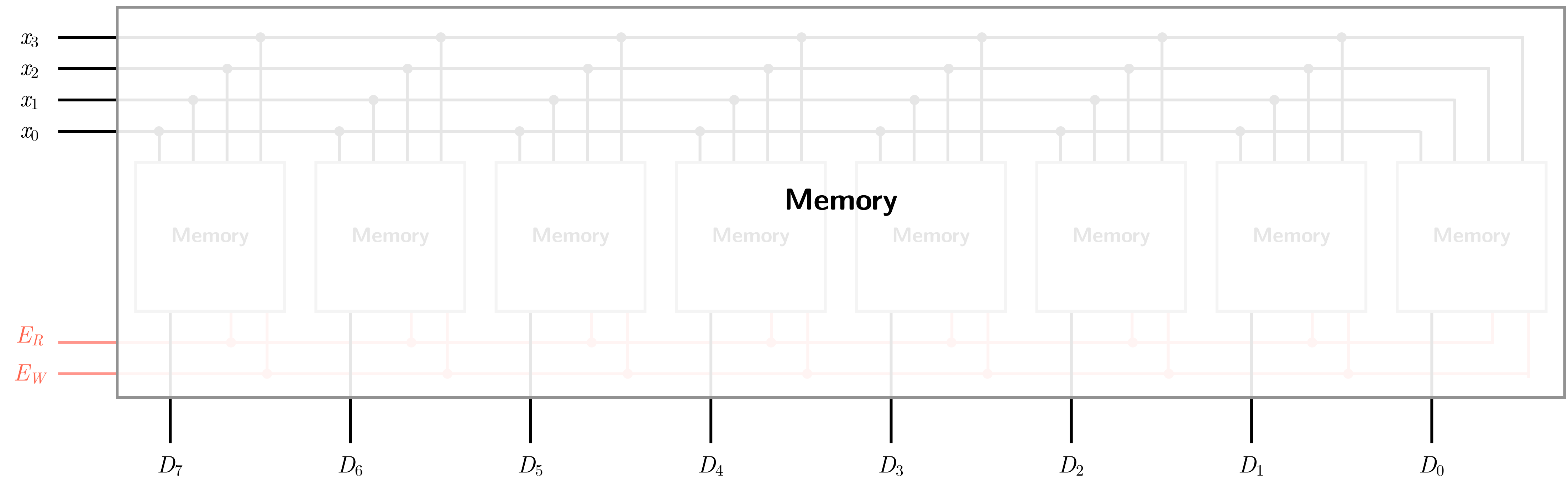


Each bit in the **byte**  $D_7D_6D_5D_4D_3D_2D_1D_0$  is stored in a separate matrix at the same address.

 This is just one of many possible ways of organizing memory.




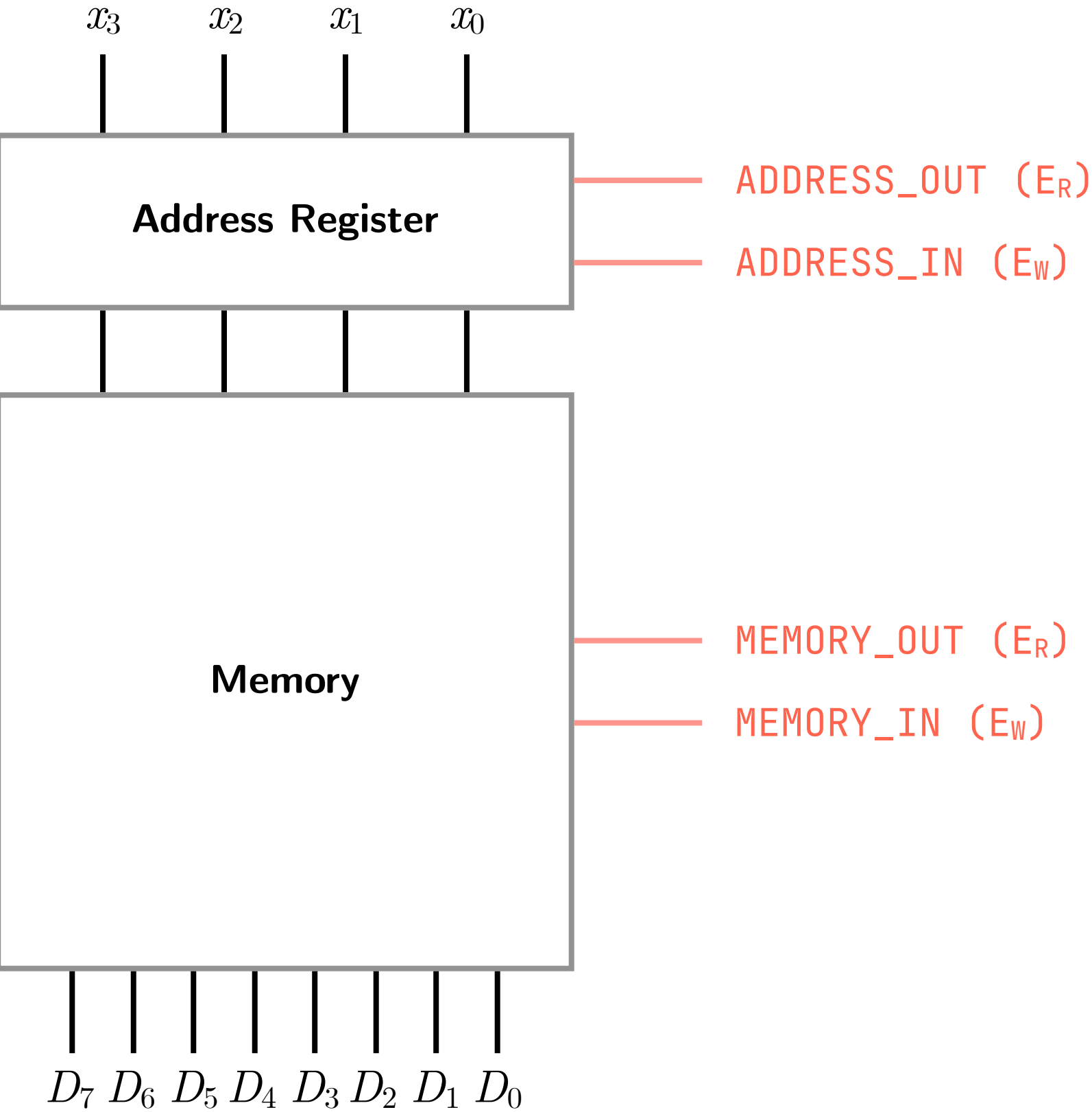The design we have seen so far only stores 1 bit, but we can use 8 copies of this system to store 1 byte. Each bit in a byte has the same address in its respective ‘copy’.



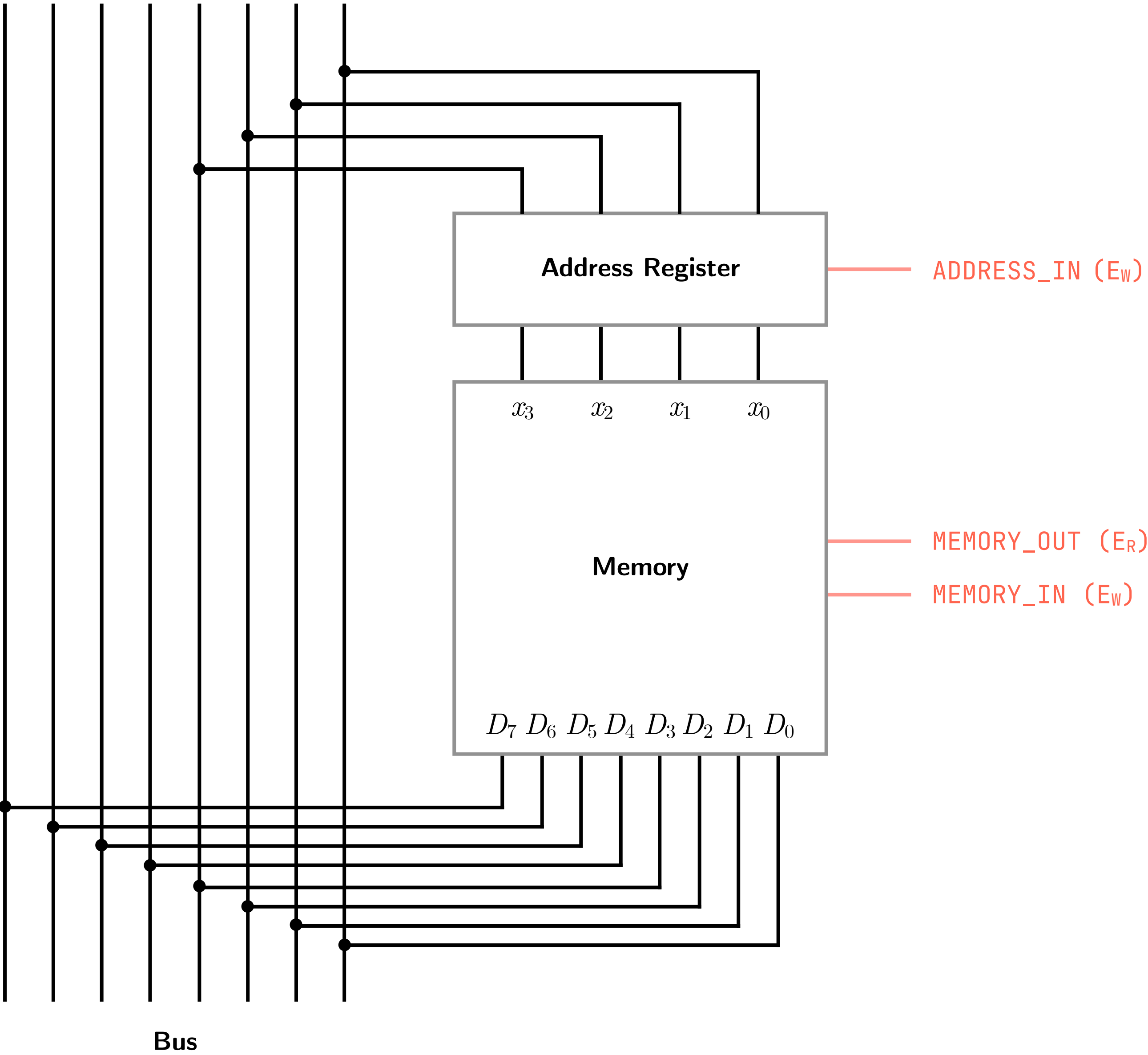The design we have seen so far only stores 1 bit, but we can use 8 copies of this system to store 1 byte. Each bit in a byte has the same address in its respective ‘copy’.






We are always “pointing” at the memory address specified in the address register.

When we do MEMORY\_OUT, we get the data at the address specified in the address register.

The design we have seen so far only stores 1 bit, but we can use 8 copies of this system to store 1 byte. Each bit in a byte has the same address in its respective ‘copy’.

By the way, we can use the same data lines for both reading and writing.

Memory (Random Access Memory, RAM)

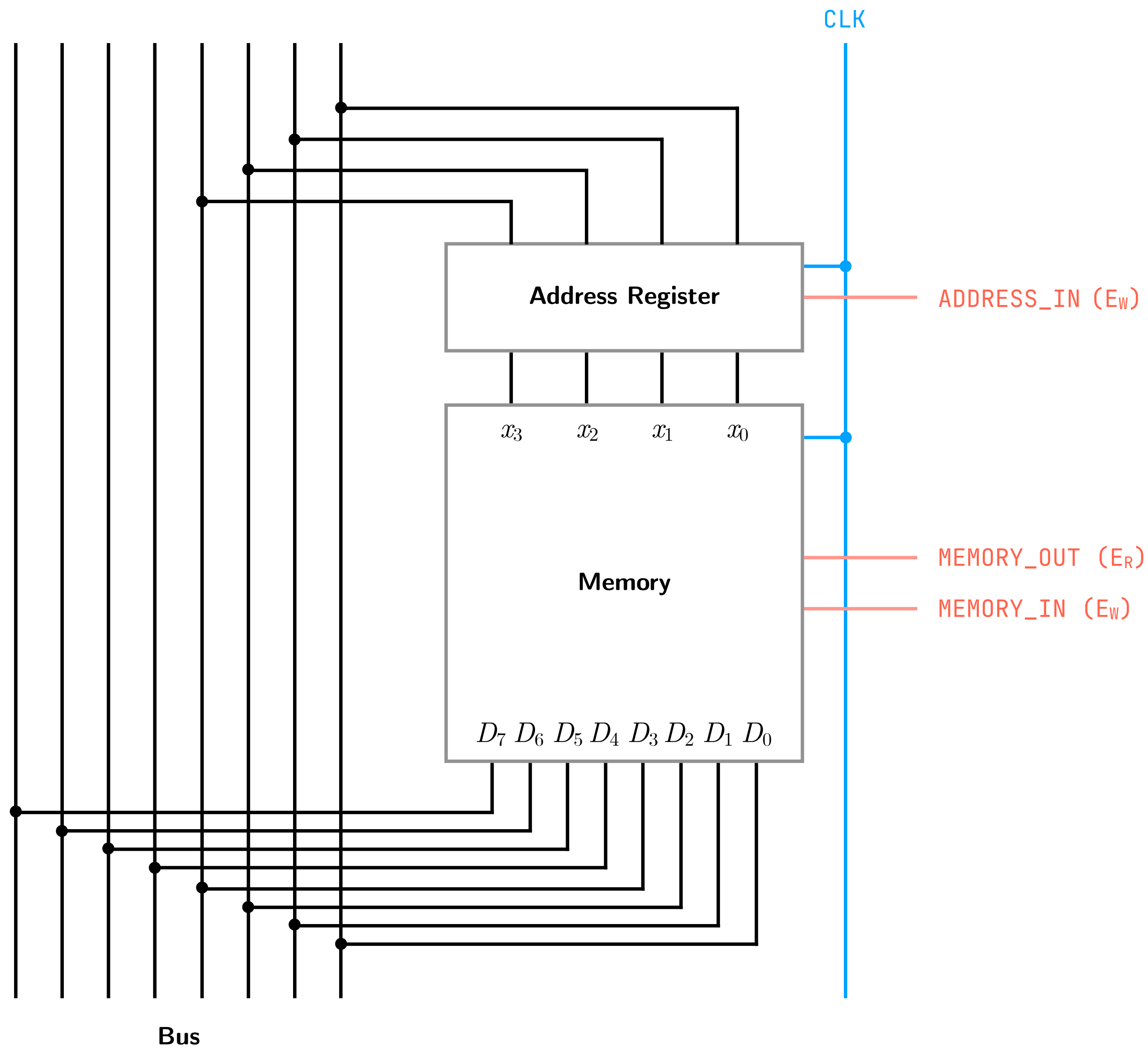

We are always “pointing” at the memory address specified in the address register.

When we do MEMORY\_OUT, we get the data at the address specified in the address register.

The design we have seen so far only stores 1 bit, but we can use 8 copies of this system to store 1 byte. Each bit in a byte has the same address in its respective ‘copy’.

By the way, we can use the same data lines for both reading and writing.

**Random access** is the ability to access an arbitrary element of a sequence in equal time from a population of addressable elements roughly as easily and efficiently as any other, no matter how many elements may be in the set. A better name might be *arbitrary access*.

In computer science it is typically contrasted to **sequential access** which requires data to be retrieved in the order it was stored.


7

Control

The components that we have already talked about  
connected via a common bus  
With control signals that we can set manually

Based on SAP-1 (also see Ben Eater)

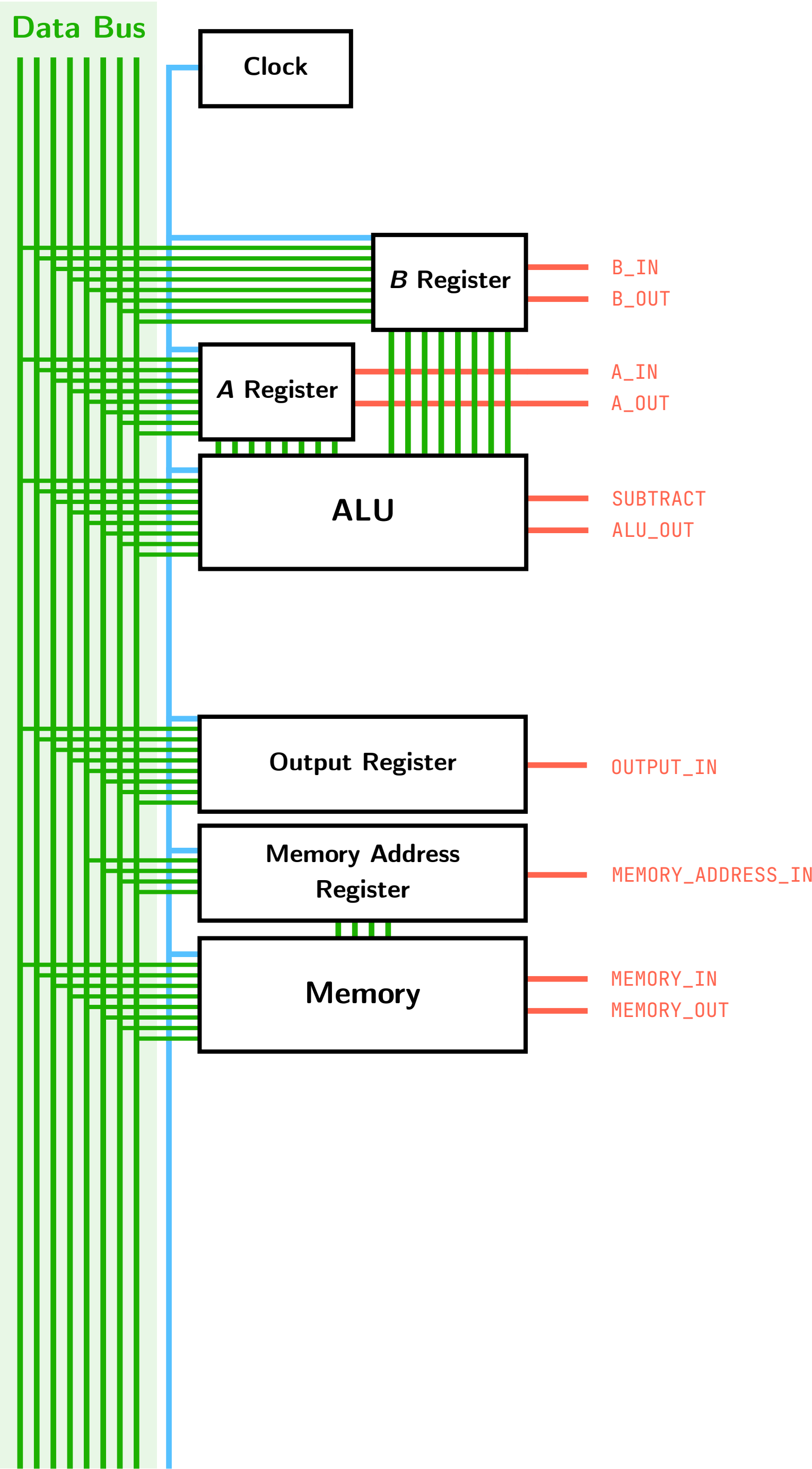Simplification: I'm only showing one connection  
between component and bus, but of course  
there are two: one for reading from the bus  
and one for writing to the bus  
(We could actually use a bidirectional register  
though, then this is correct. But not going into  
that here...)



We can have any number of registers that we like

Some registers might be used for specific purposes, rather than be general-purpose registers that any component can read from or write to

One specialized register is the **instruction register**

## Program Counter (aka Instruction Pointer)

Other names are: **instruction pointer** and **instruction address register**, which might help make sense of what its purpose is.

We count the instructions; we start at 0, and each time an instruction is finished, we'll increment it

If addresses are, say, 4 bits, then the program counter is simply a register with 4 bits in it,

where these 4 bits constitute a counter; i.e. we start at 0000 and increment it under certain circumstances using control signals

Before going into the other details of the program counter,

let's quickly have a look at how we have to modify the binary counter that we have encountered before (T flip-flop)

## Program Counter (aka Instruction Pointer)


We already know how to make a binary counter using T flip-flops.

Unlike the ordinary binary counter, we only want the program counter to increment when an instruction is finished (in which case we want to go to the next instruction), and an instruction might take multiple clock cycles. I.e. it should not simply increment with each clock pulse, but only when we tell it to (by providing a control signal)

But we also want to be able to write an arbitrary instruction address into the register rather than just incrementing it. For this, we need another control signal and some additional logic.



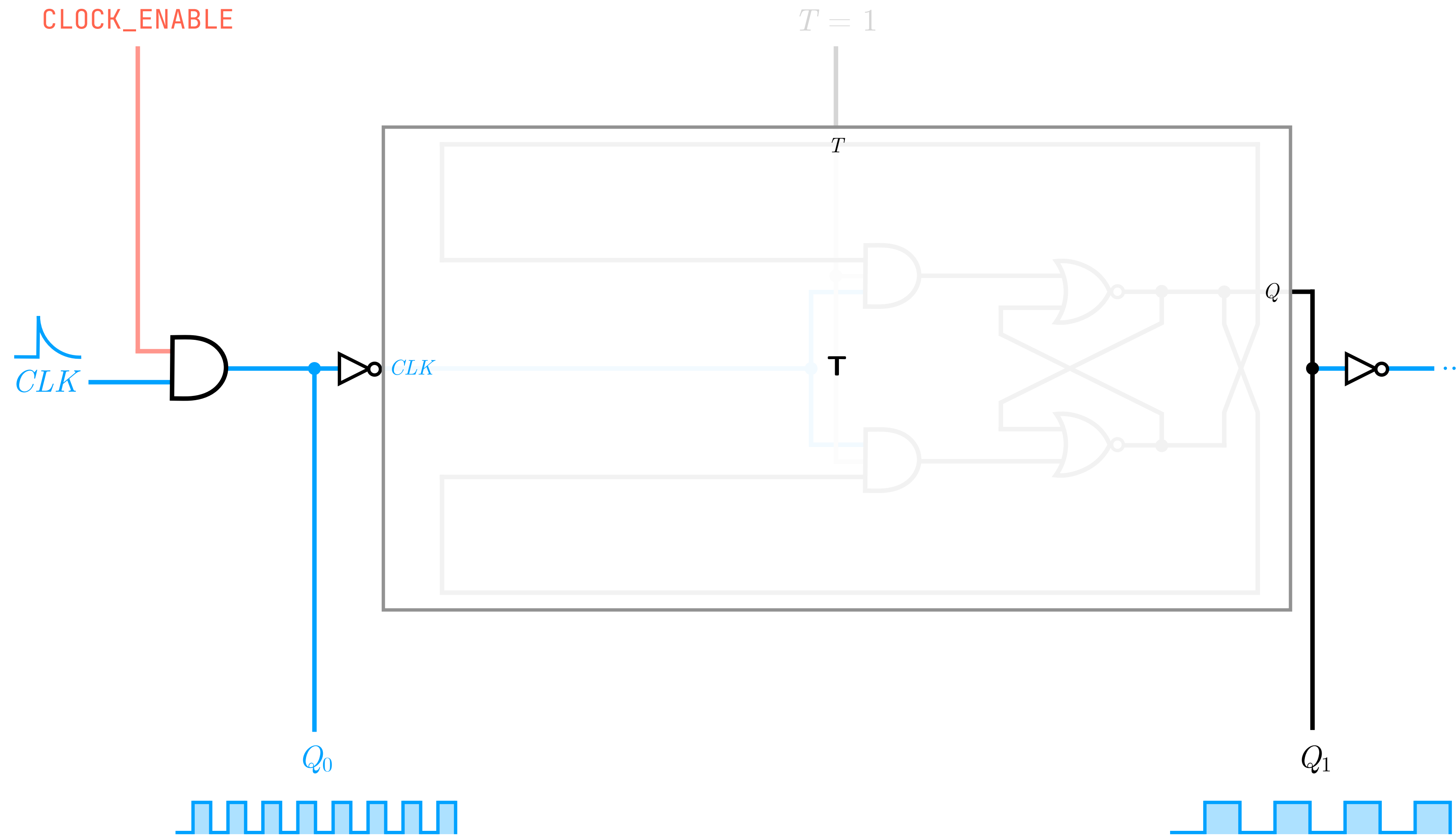
## Program Counter (aka Instruction Pointer)




Clock gating is not recommended in more complex computers, but fine in this example.

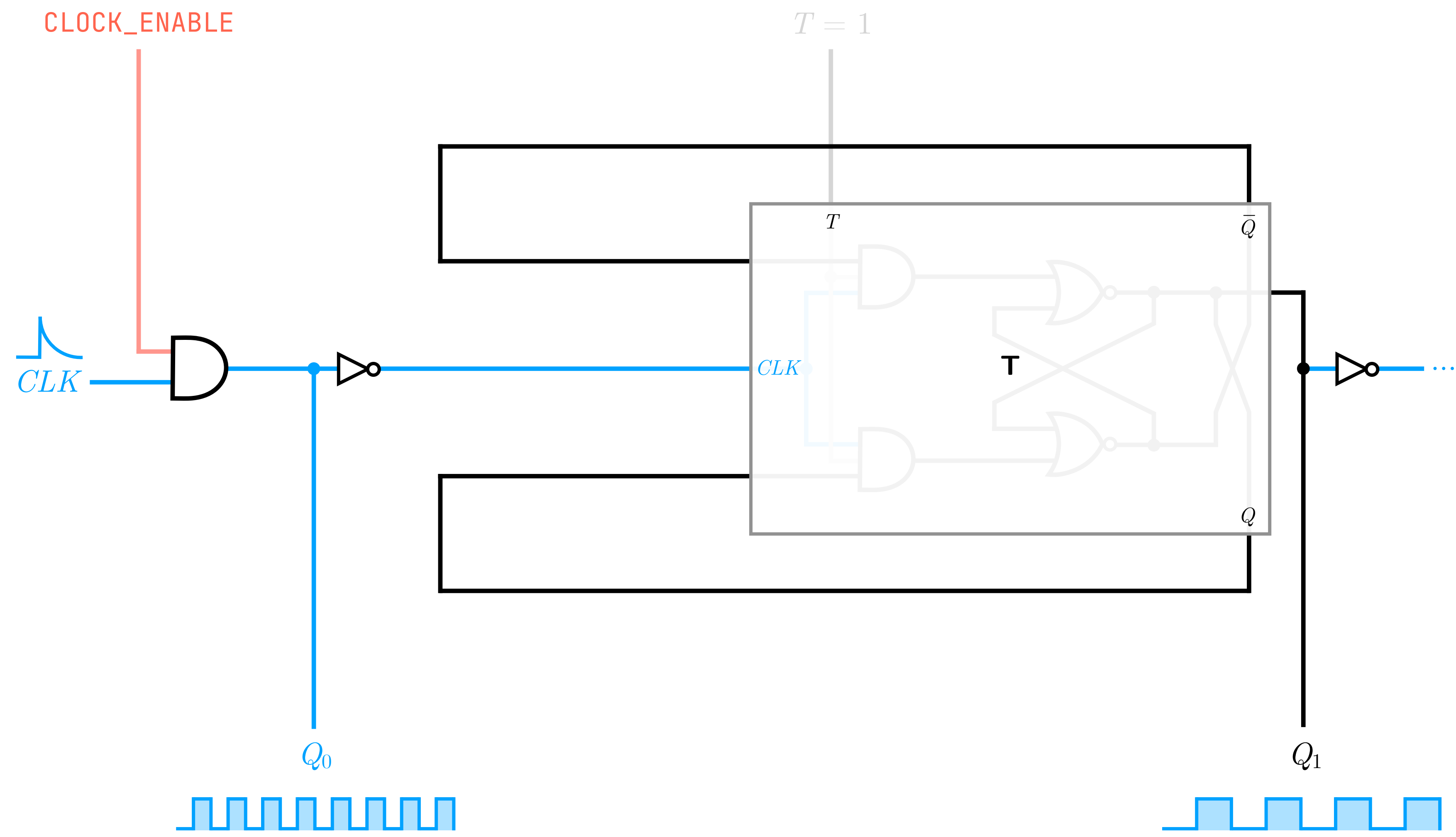Program Counter (aka Instruction Pointer)



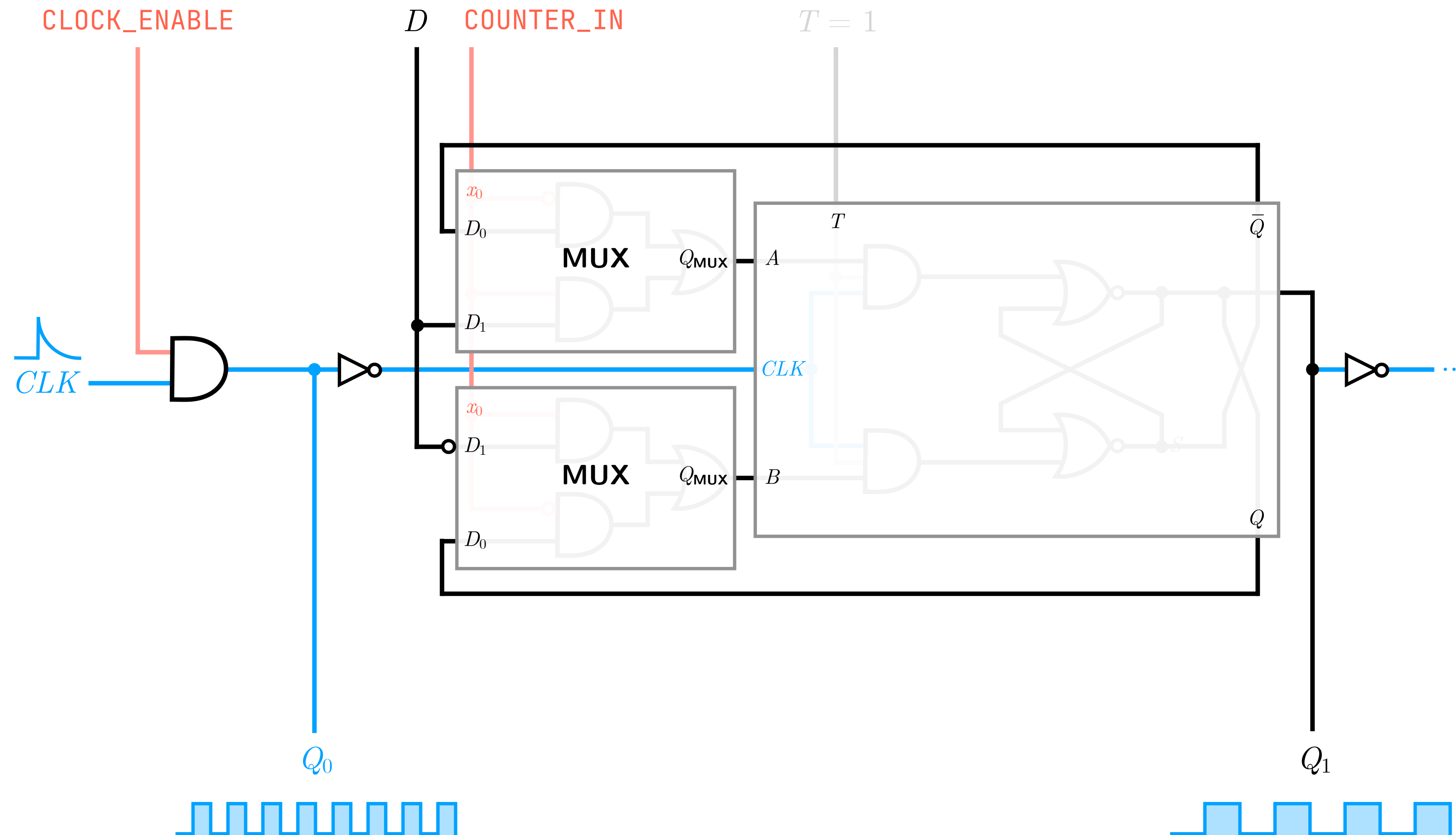
## Program Counter (aka Instruction Pointer)



Same ENABLE logic as before (MUX),  
but we need it for each input separately,  
one using Q and the other notQ.

T flip flop (fixed  $T=J=K=1$ ),  
but instead of just feeding (Q, notQ) back,  
we instead feed (D, D) if COUNTER\_IN  
is active (and only if CLOCK\_ENABLE  
is active and there's a clock pulse)

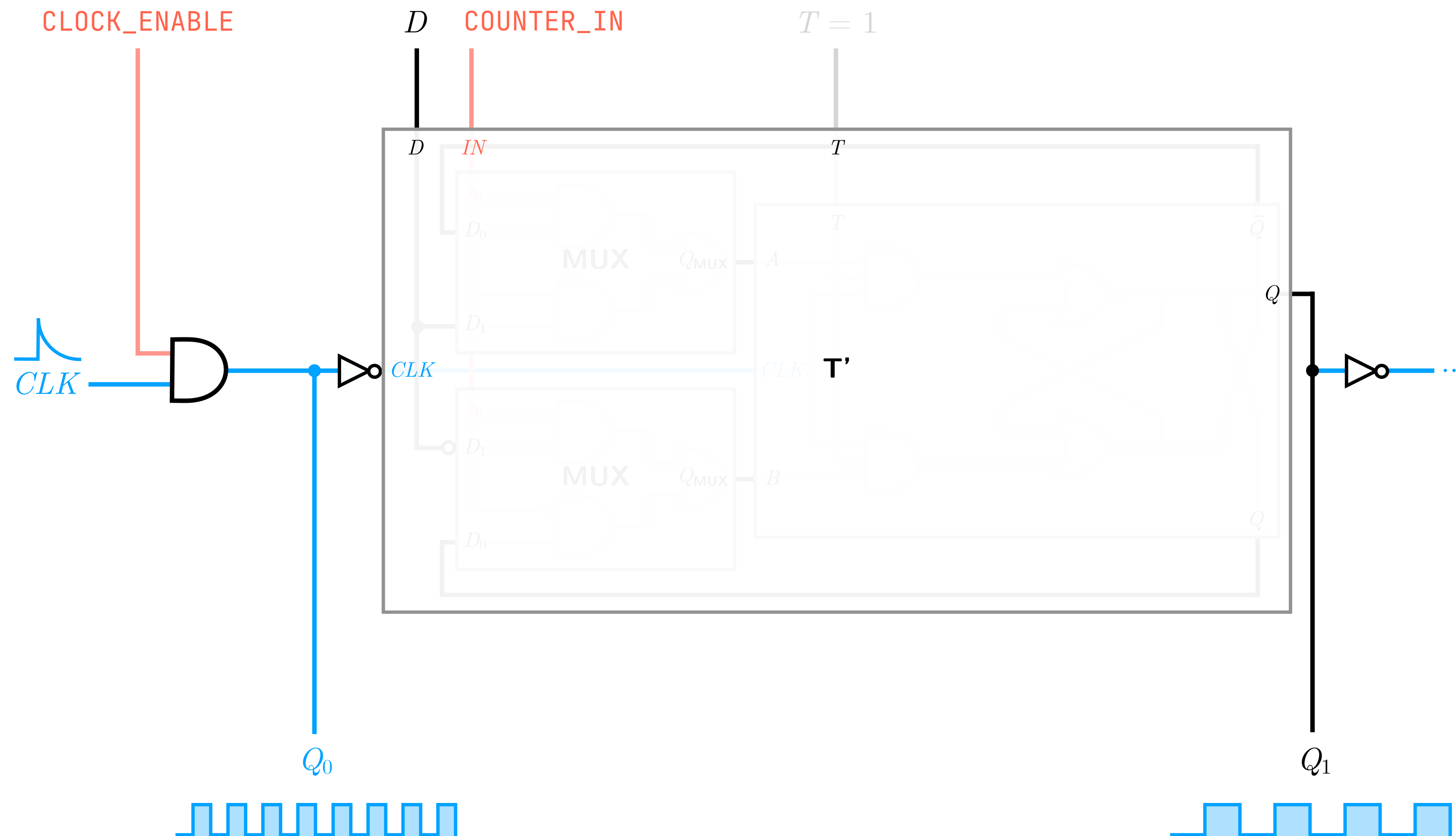
## Program Counter (aka Instruction Pointer)



Same ENABLE logic as before (MUX), but we need it for each input separately, one using  $Q$  and the other  $\bar{Q}$ .


T flip flop (fixed  $T=J=K=1$ ), but instead of just feeding ( $Q$ ,  $\bar{Q}$ ) back, we instead feed ( $D$ ,  $D$ ) if  $COUNTER\_IN$  is active (and only if  $CLOCK\_ENABLE$  is active and there's a clock pulse)

 Program Counter (aka Instruction Pointer)




Program Counter (aka Instruction Pointer)

 We can flip our diagram, so the least significant bit is on the right.



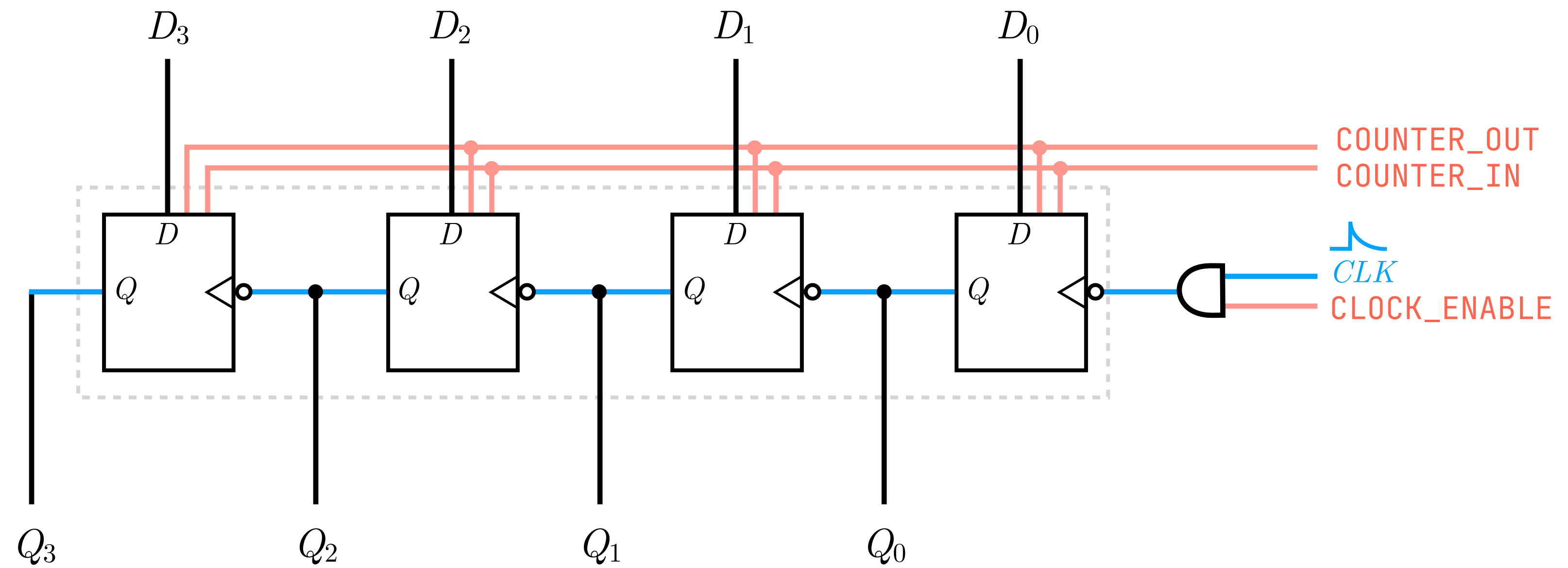
## Program Counter (aka Instruction Pointer)

Same WRITE\_ENABLE  
(COUNTER\_OUT) as before  
using tri-state logic.



 
Program Counter (aka Instruction Pointer)





Program Counter (aka Instruction Pointer)

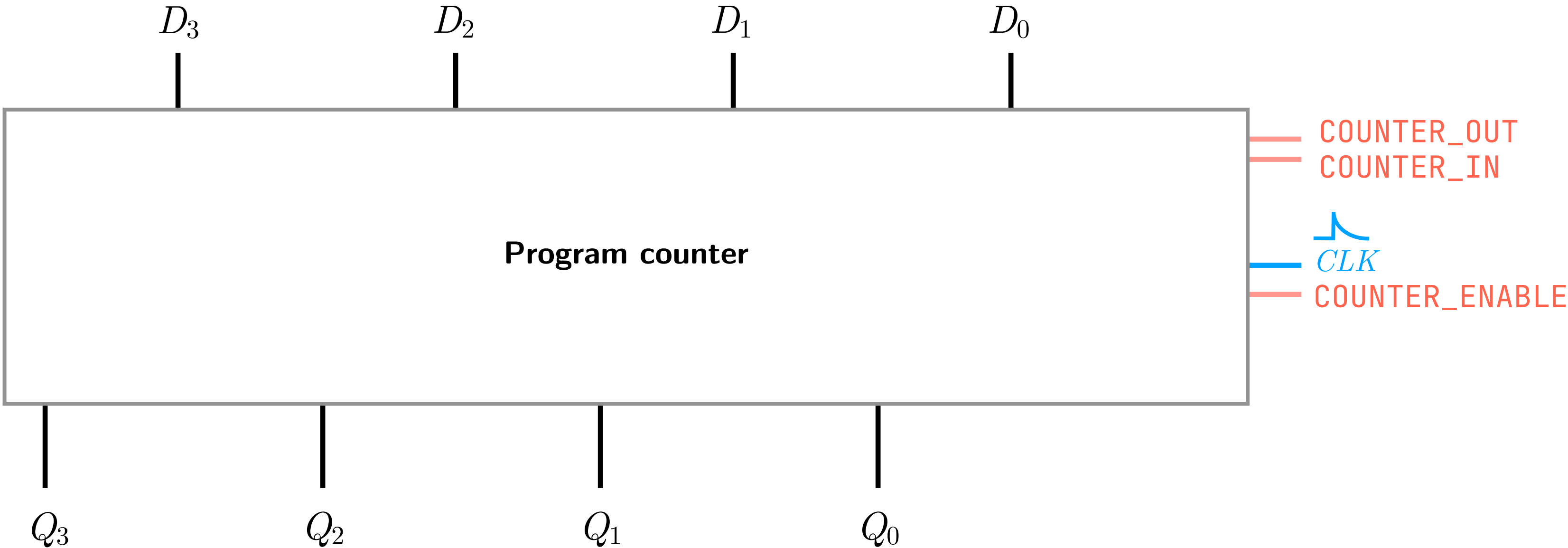
Slightly different variant  
using COUNTER\_ENABLE  
rather than CLOCK\_ENABLE.  
COUNTER\_IN, COUNTER\_OUT  
now also work independently of  
CLOCK\_ENABLE




This is the coolest part  
it's where everything comes together

Inverted clock!

Clock

 

Clock

 

map [opcode, step] to control\_word, where control\_word is simply the string of all control signals and their value in that micro-step, i.e. all are 0 except for the control signals we want to execute, which are 1

ROM is used as “Instruction Decoder”


micro-step counter aka “sequencer”

# Control logic

Coming up with instructions: we can use mnemonics and then come up with instruction codes


For now, imagine we activate the clock manually and in between clock highs we set the control signals

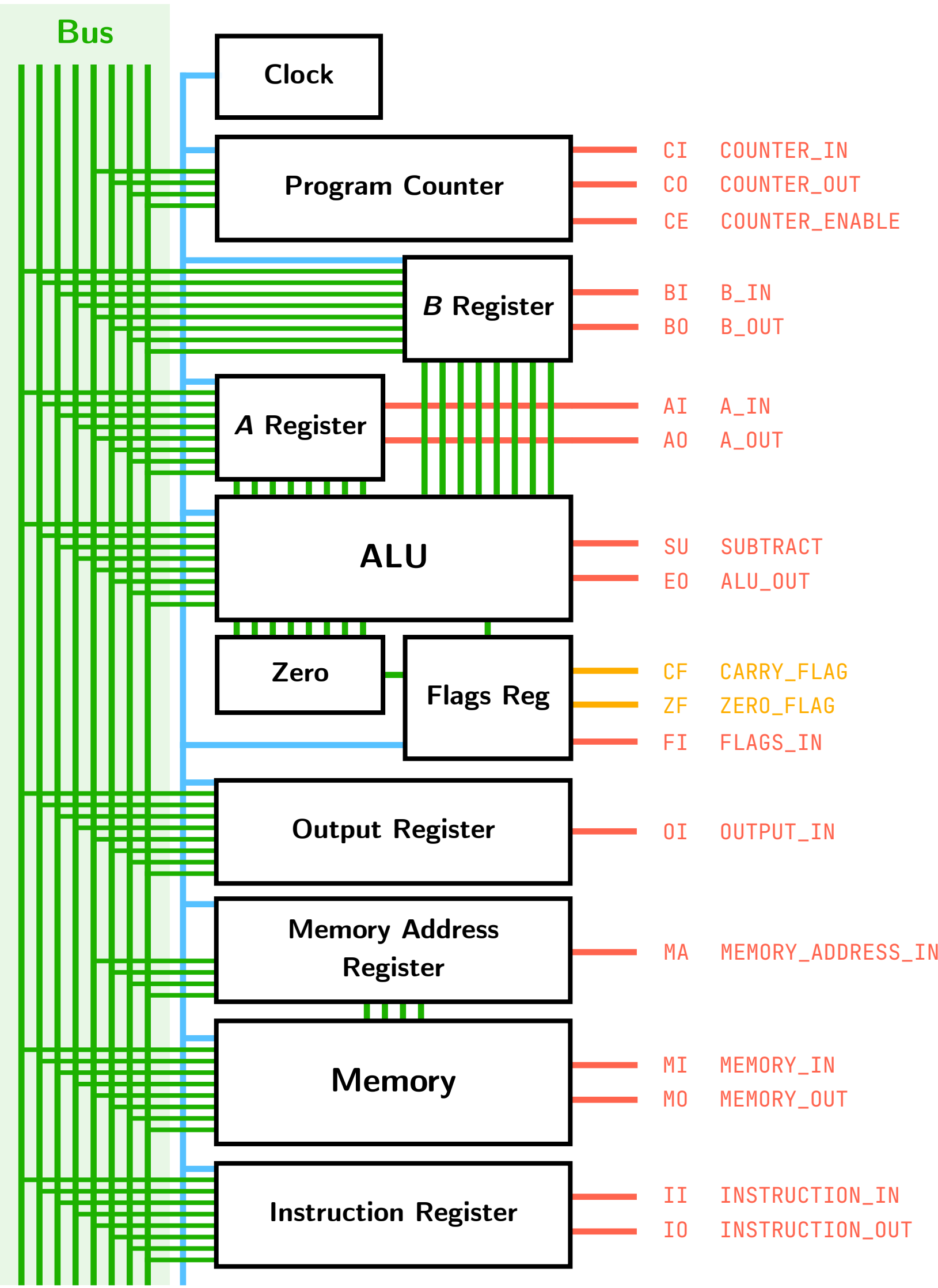Explain that there are steps  
e.g. 6 steps, each takes one clock cycle  
each instruction goes through all 6 steps  
and so each instruction takes 6 clock cycles





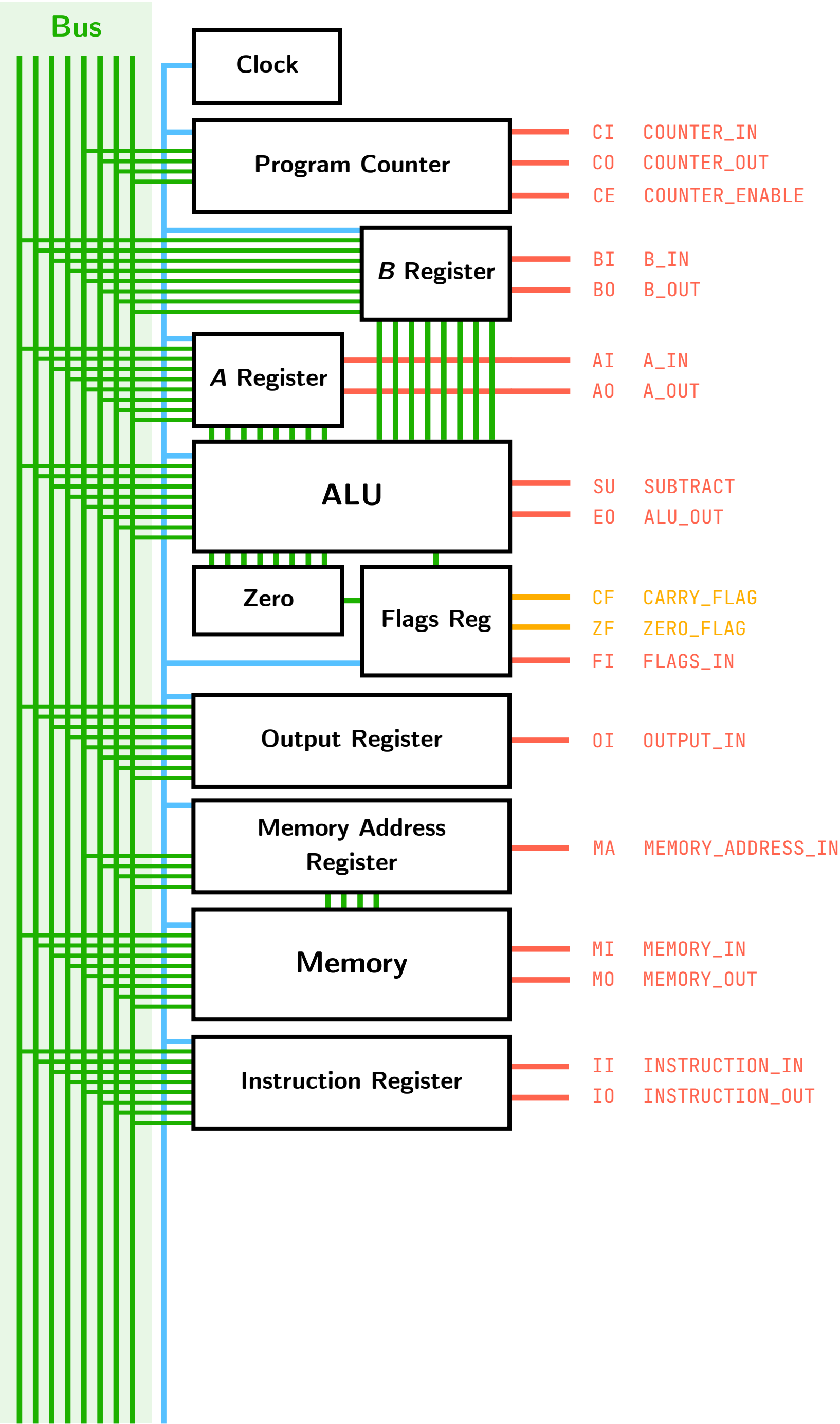At this point, when explaining stuff,  
there's no ROM or step counter yet !!!




Program		
[0]	LOAD	14
[1]	ADD	15
[2]	OUT	
[14]	10	
[15]	20	

Not showing reset circuit

There's also connections like this that we can use instead of the MAR and bus in order to manually program the computer (manually write something to memory)  
We can call this “**programming mode**”, as opposed to the usual “**run mode**”

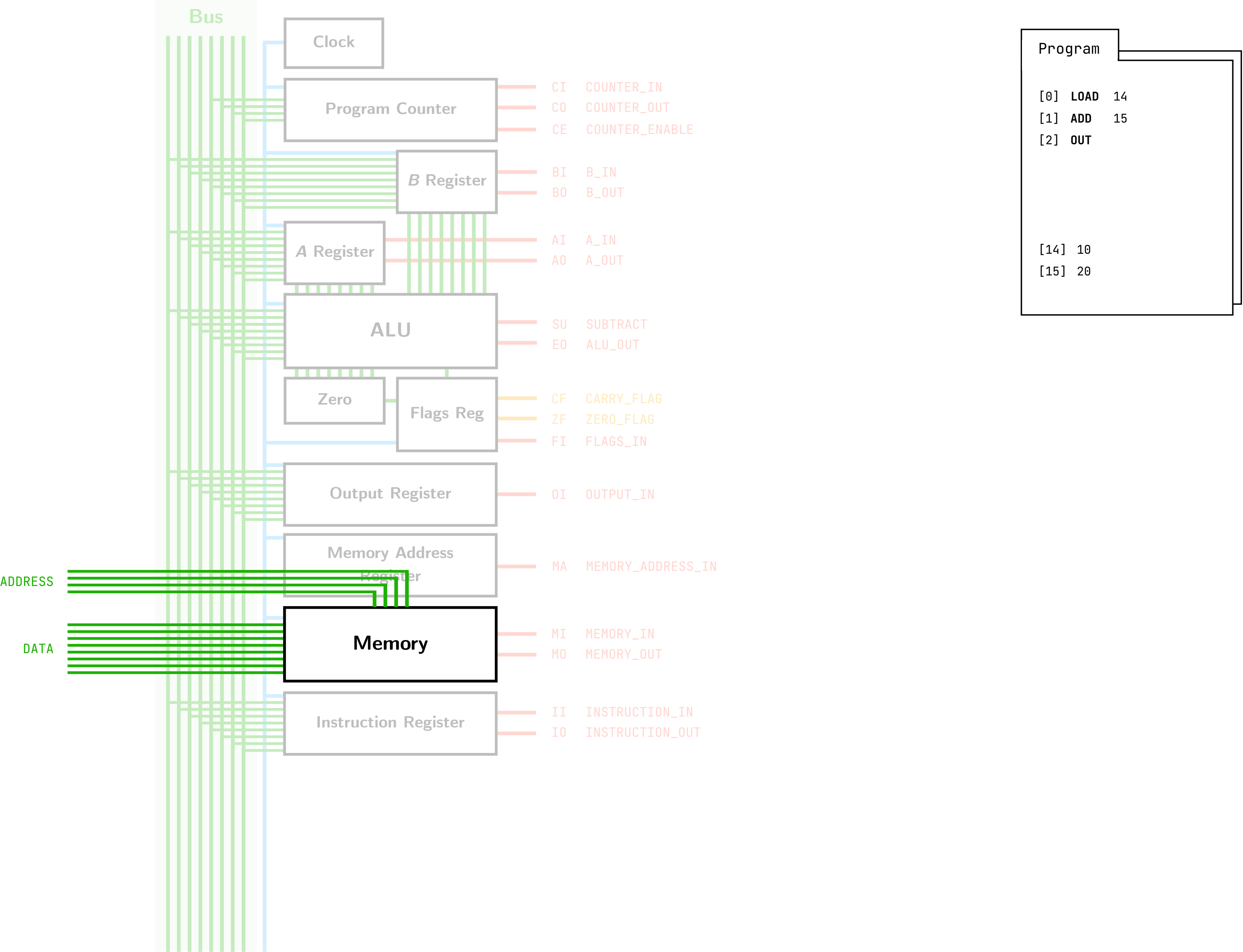
Manually write some data (8 bits) at some memory address (4 bits)







There's also connections like this that we can use instead of the MAR and bus in order to manually program the computer (manually write something to memory)  
We can call this **“programming mode”**, as opposed to the usual **“run mode”**

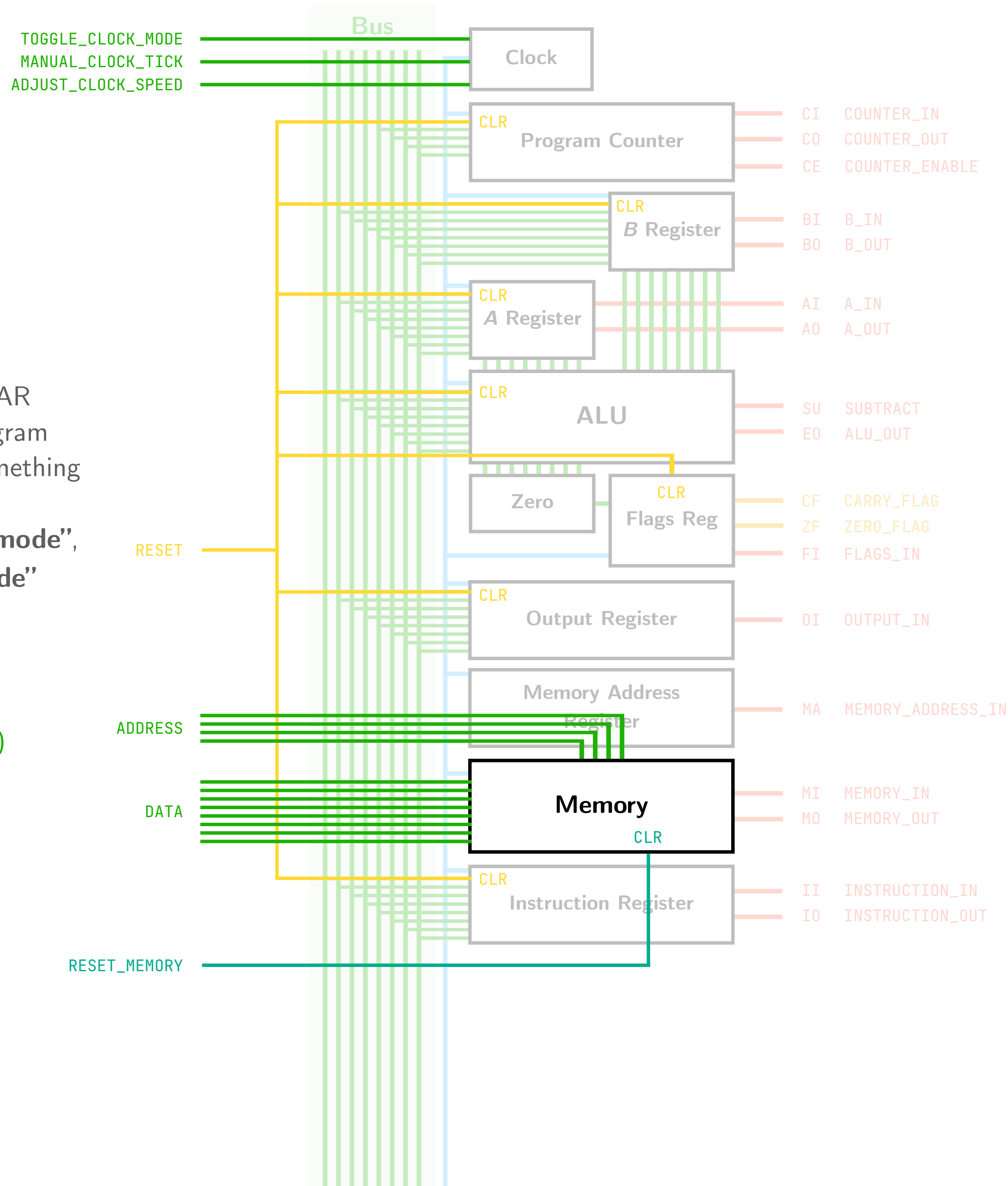
Manually write some data (8 bits) at some memory address (4 bits)





Program		
[0]	LOAD	14
[1]	ADD	15
[2]	OUT	
[14]	10	
[15]	20	

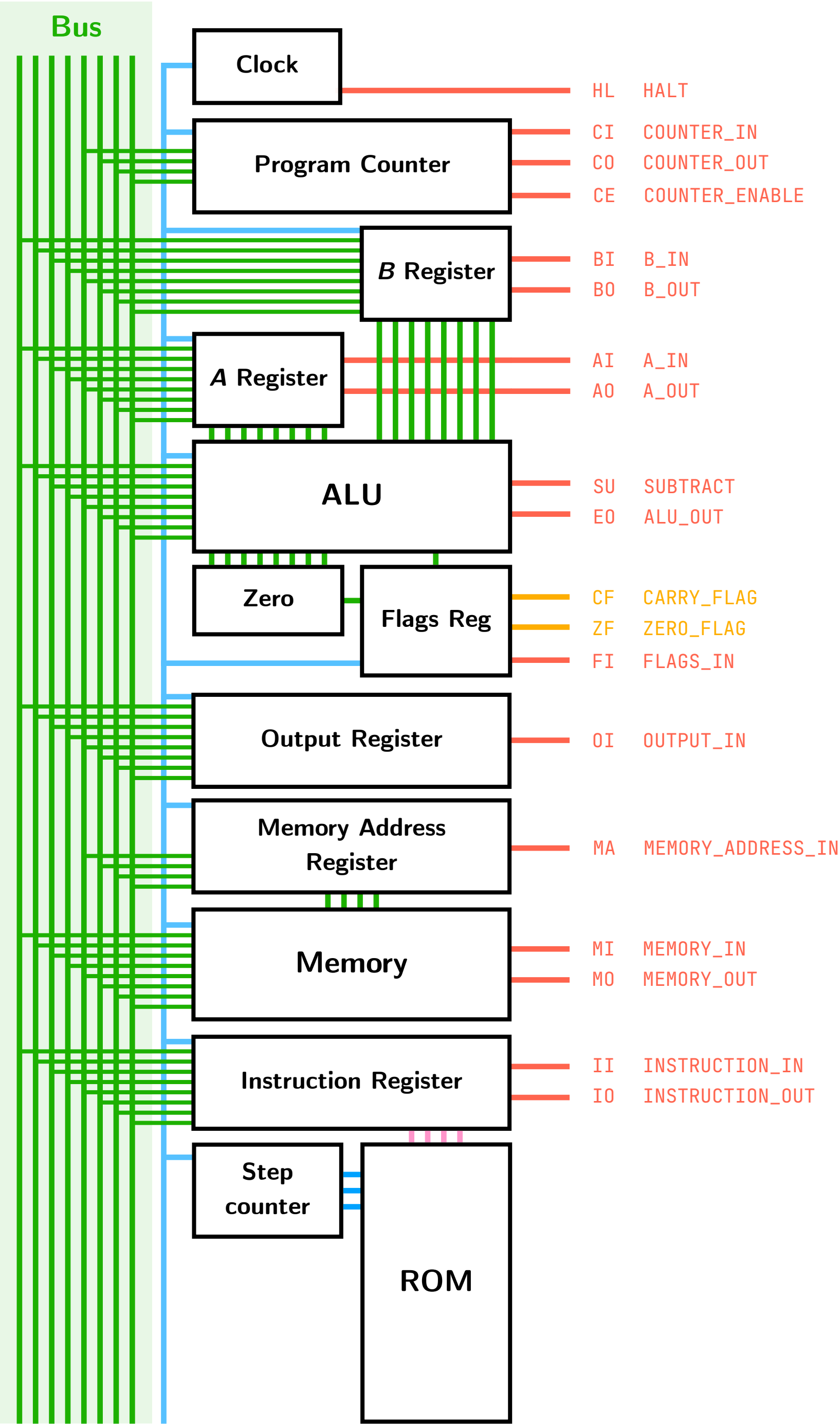


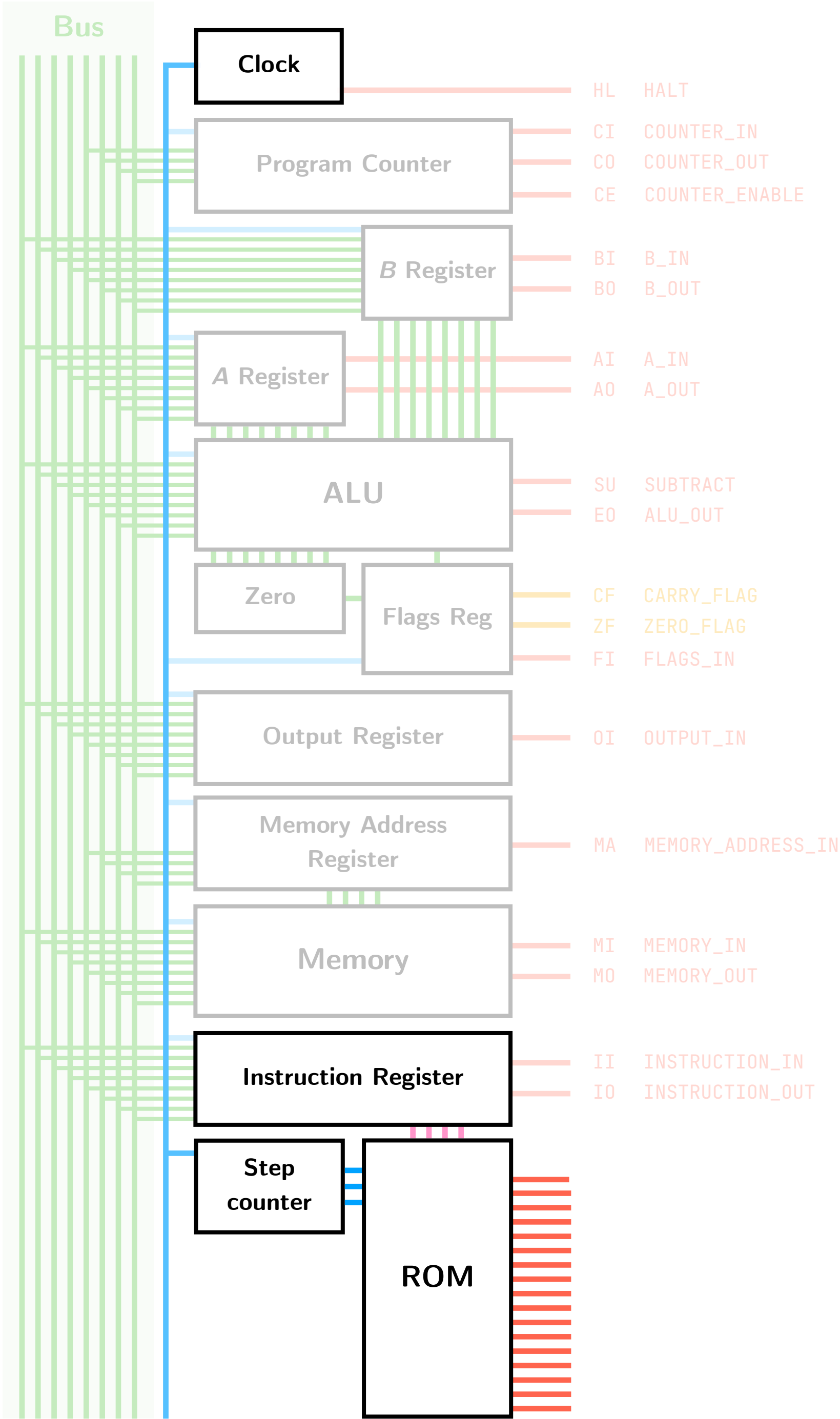


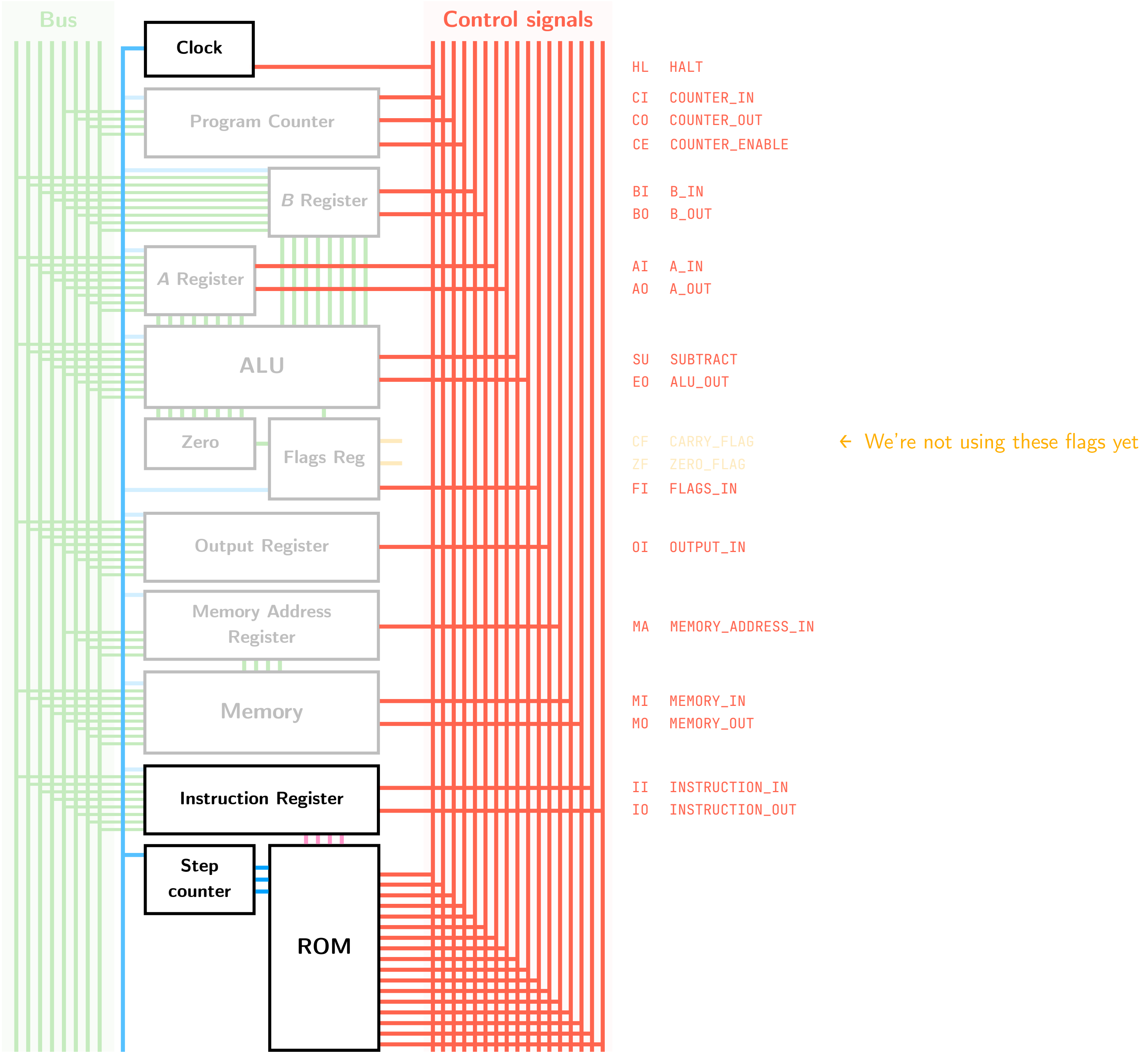

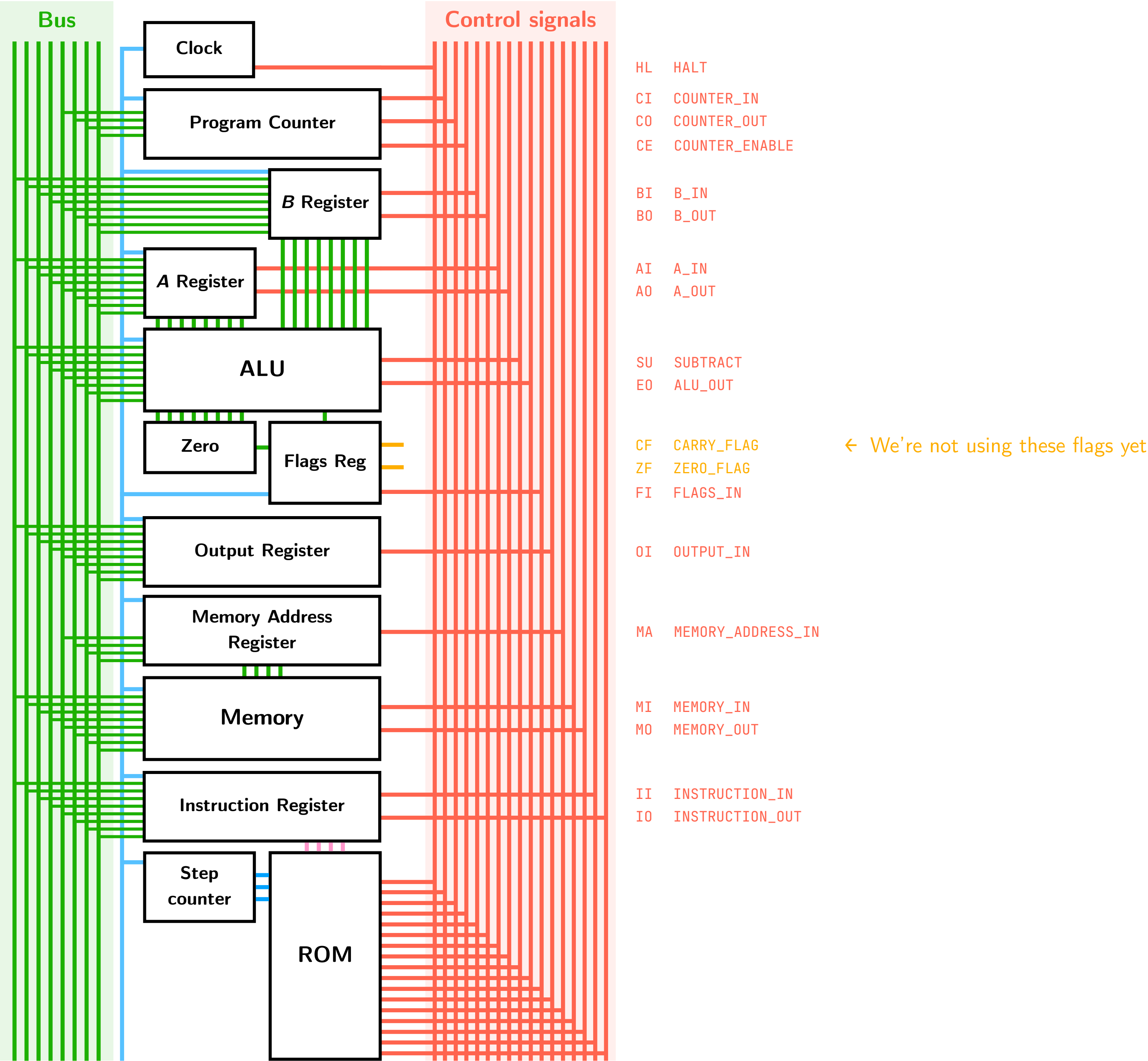


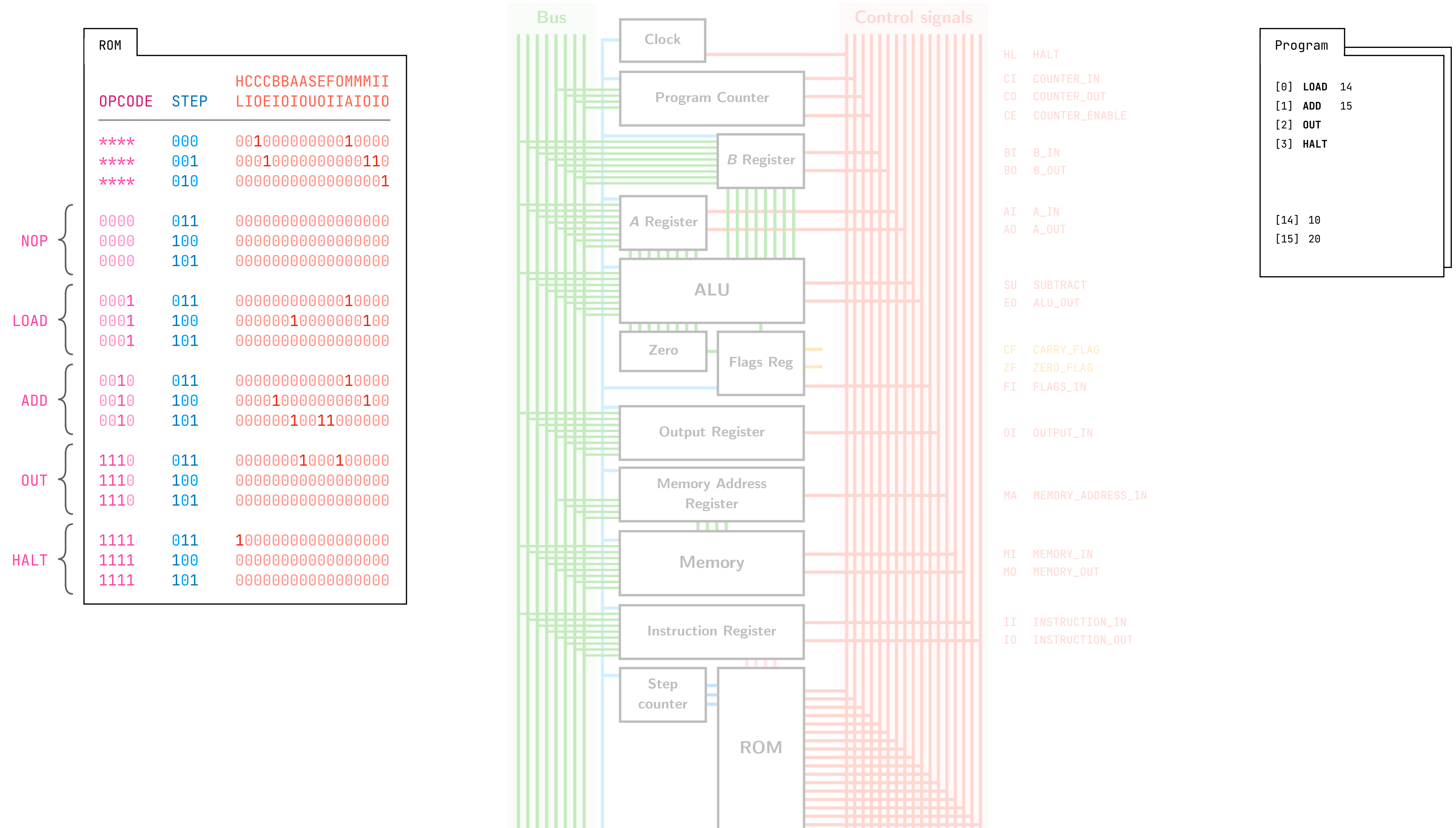


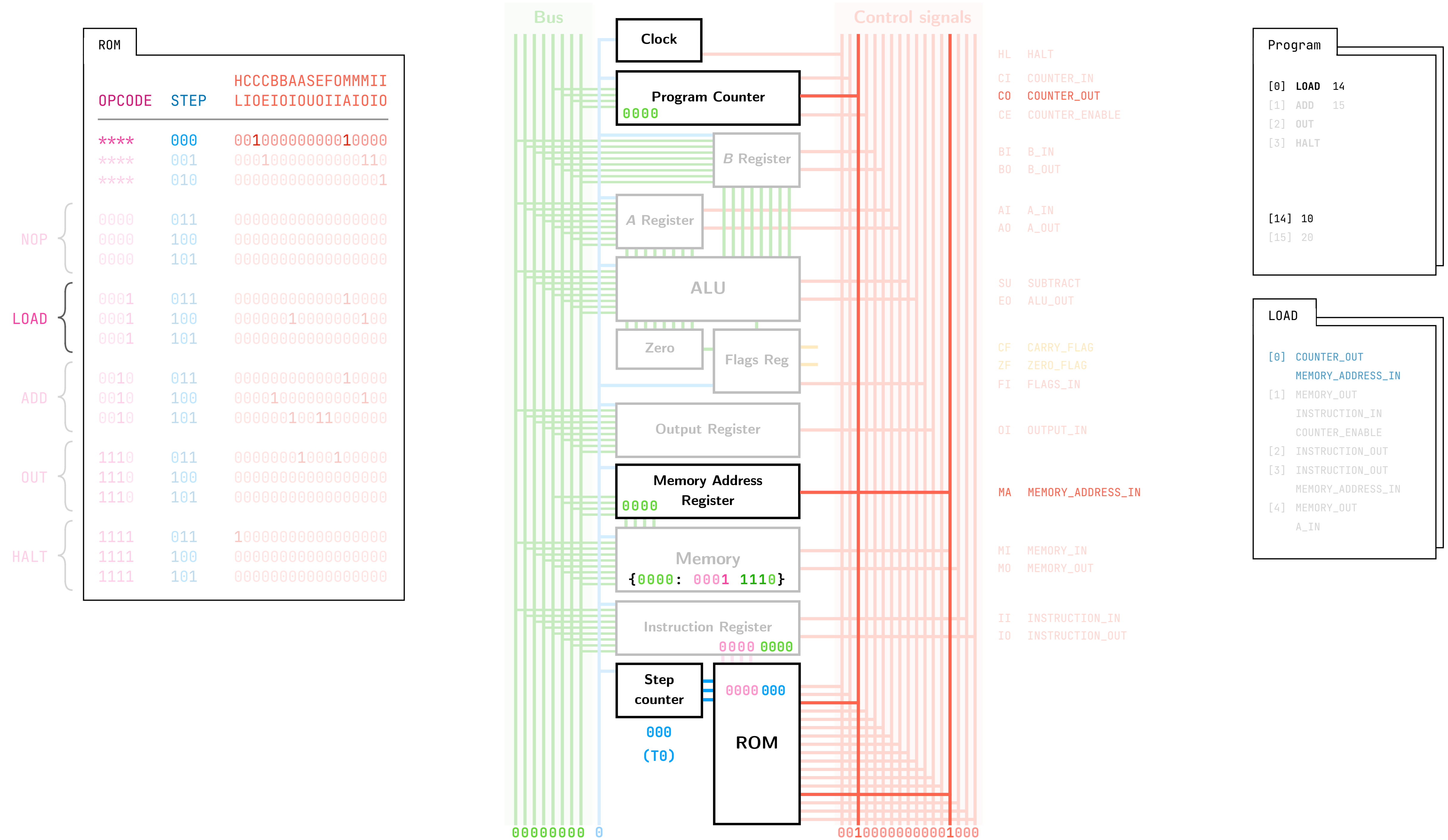


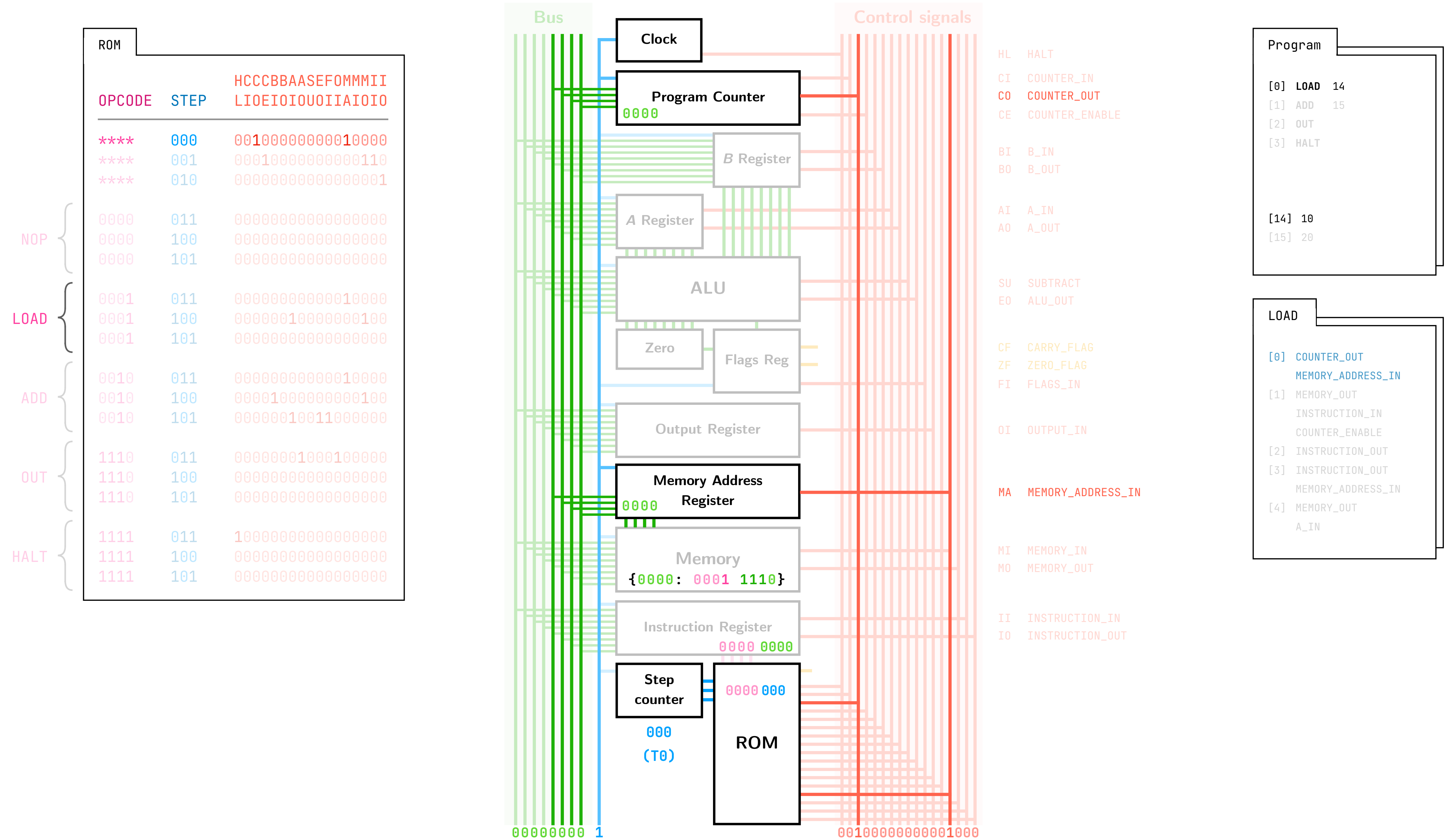




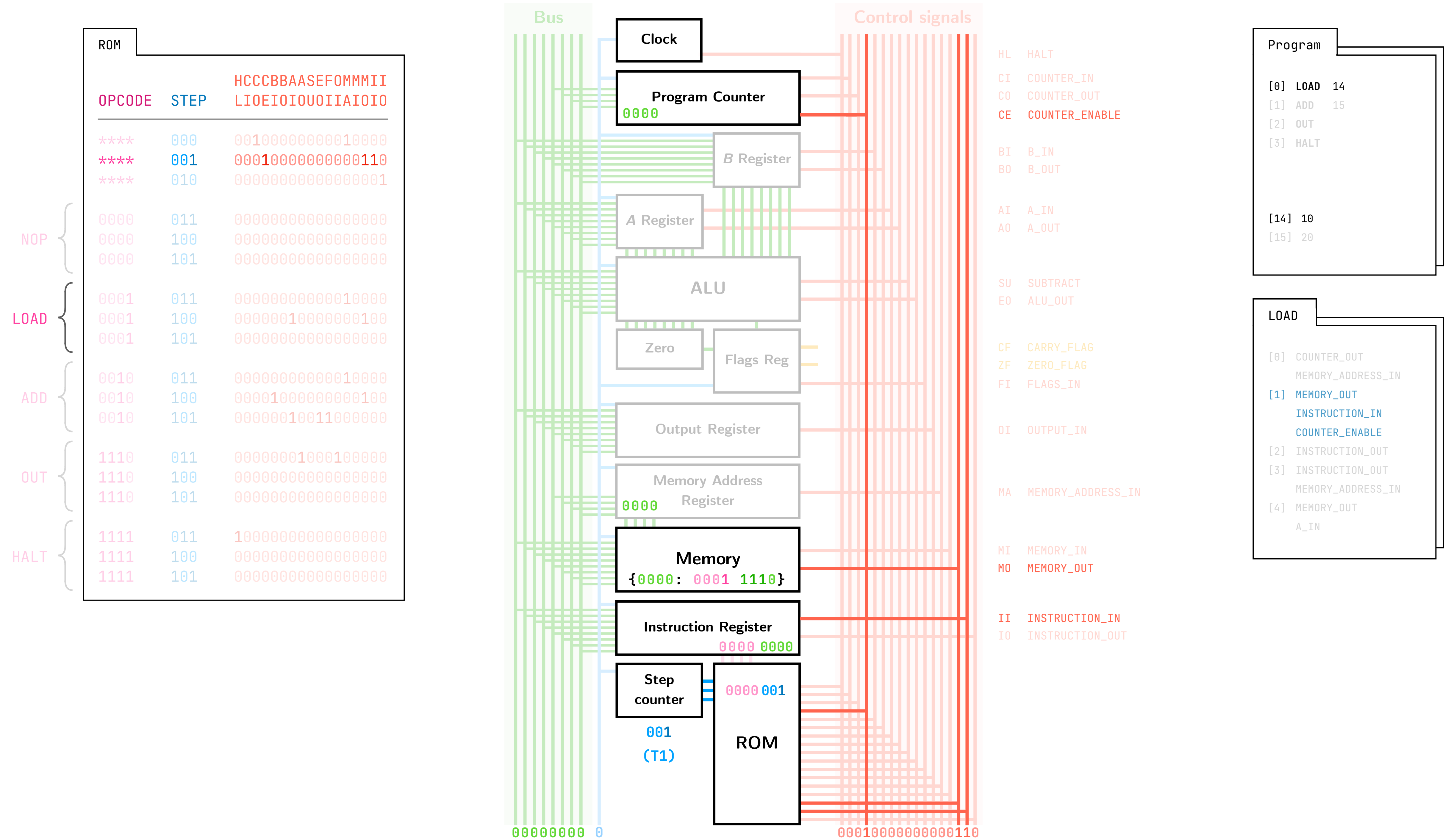

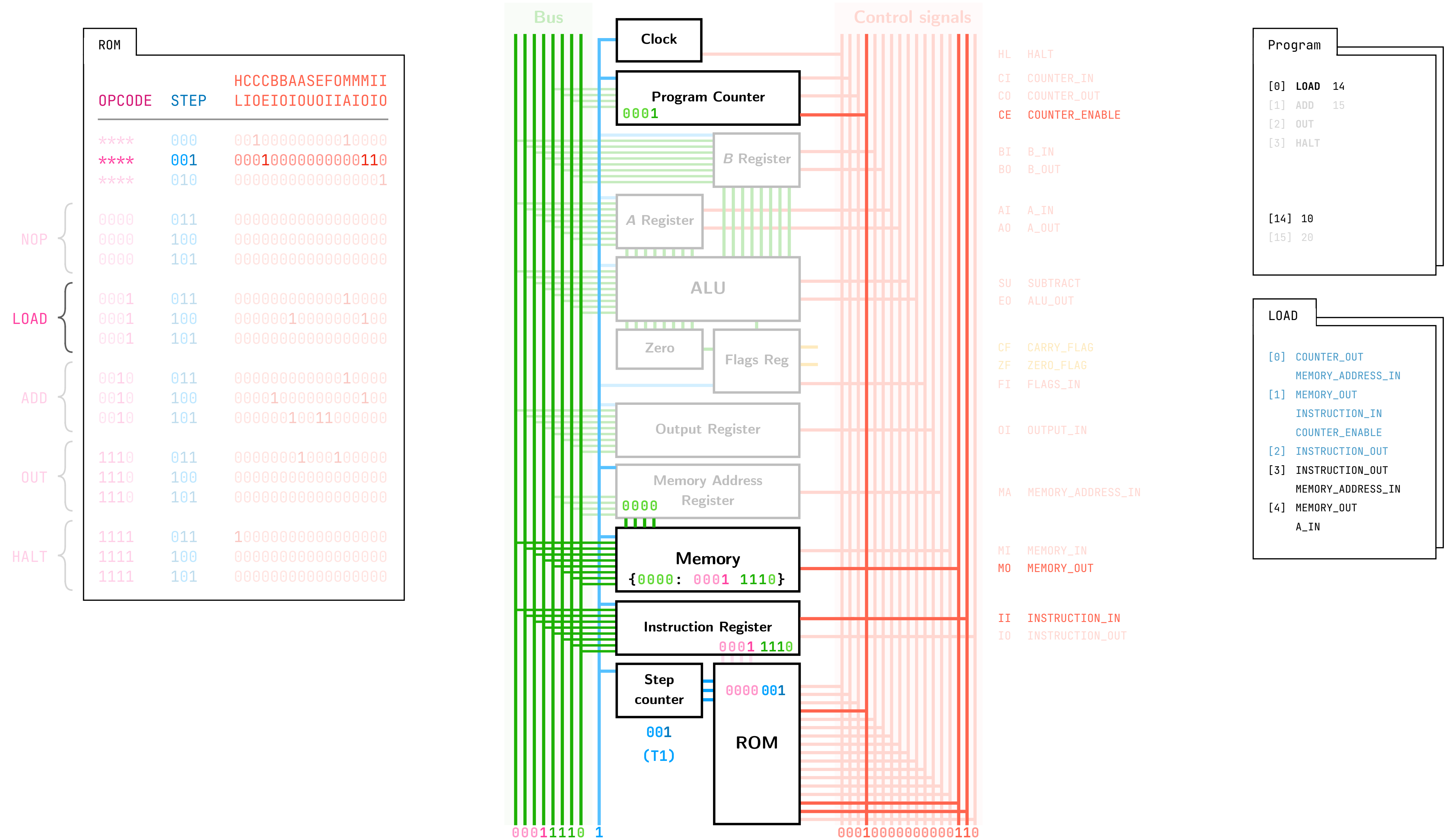

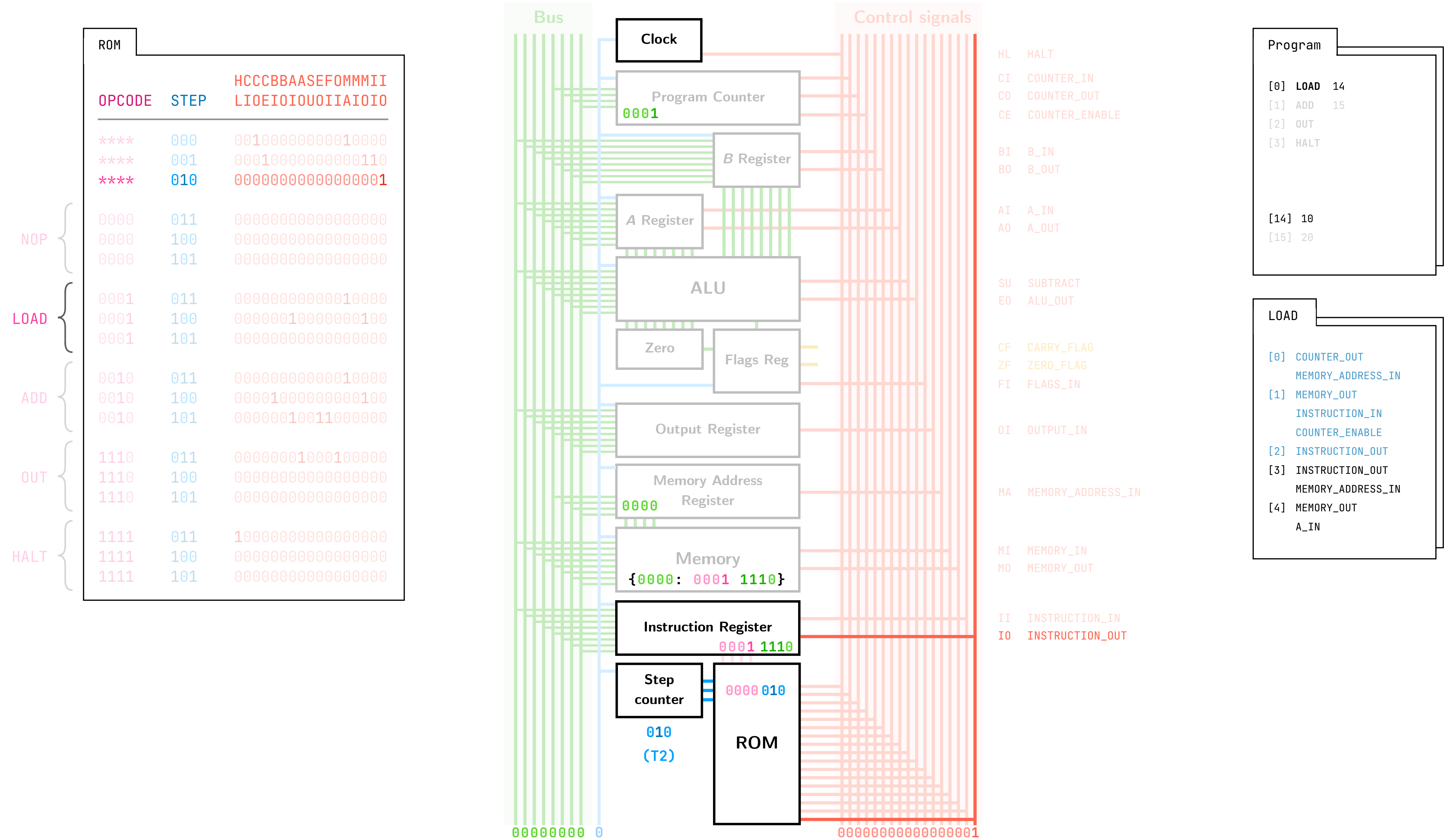

ROM			
OPCODE	STEP		HCCCBBAASEFOMMMII LIOEIOIOUOIIAIOIO
****	000		00100000000010000
****	001		00010000000000110
****	010		00000000000000001
NOP	011		00000000000000000
	100		00000000000000000
	101		00000000000000000
LOAD	011		00000000000010000
	100		00000010000000100
	101		00000000000000000
ADD	011		00000000000010000
	100		00001000000000100
	101		00000010011000000
OUT	011		00000001000100000
	100		00000000000000000
	101		00000000000000000
HALT	011		10000000000000000
	100		00000000000000000
	101		00000000000000000

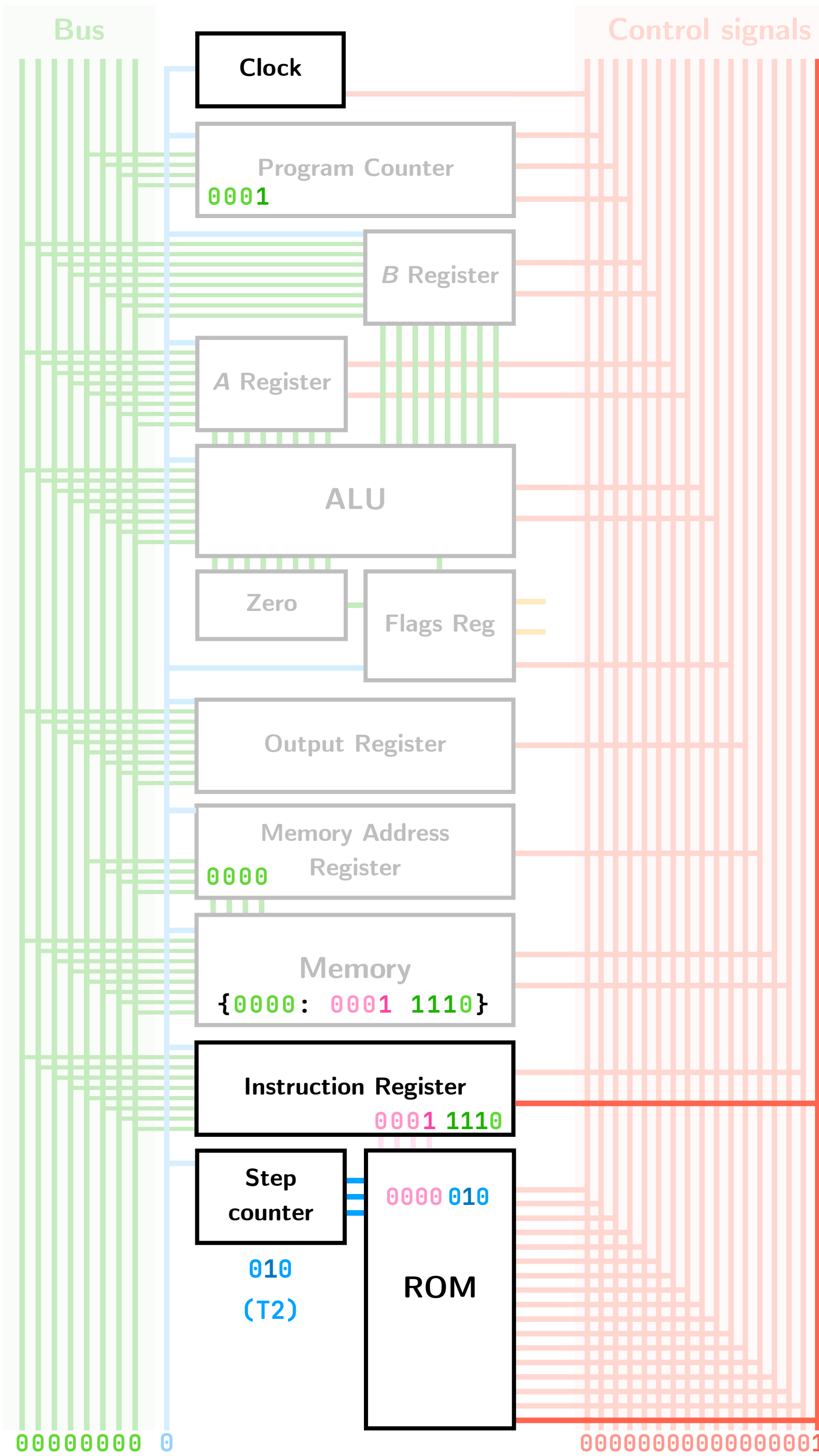


- HL HALT
- CI COUNTER\_IN
- CO COUNTER\_OUT
- CE COUNTER\_ENABLE
- BI B\_IN
- BO B\_OUT
- AI A\_IN
- AO A\_OUT
- SU SUBTRACT
- EO ALU\_OUT
- CF CARRY\_FLAG
- ZF ZERO\_FLAG
- FI FLAGS\_IN
- OI OUTPUT\_IN
- MA MEMORY\_ADDRESS\_IN
- MI MEMORY\_IN
- MO MEMORY\_OUT
- II INSTRUCTION\_IN
- IO INSTRUCTION\_OUT

Program		
[0]	LOAD	14
[1]	ADD	15
[2]	OUT	
[3]	HALT	
[14]	10	
[15]	20	

LOAD		
[0]	COUNTER_OUT	
[1]	MEMORY_OUT	
	INSTRUCTION_IN	
	COUNTER_ENABLE	
[2]	INSTRUCTION_OUT	
[3]	INSTRUCTION_OUT	
	MEMORY_ADDRESS_IN	
[4]	MEMORY_OUT	
	A_IN	

ROM		
OPCODE	STEP	HCCCBBAASEFOMMMII LIOEIOIOUOIIAIOIO
****	000	00100000000010000
****	001	00010000000000110
****	010	00000000000000001
NOP	011	00000000000000000
	100	00000000000000000
	101	00000000000000000
LOAD	011	00000000000010000
	100	00000010000000100
	101	00000000000000000
ADD	011	00000000000010000
	100	00001000000000100
	101	00000010011000000
OUT	011	00000001000100000
	100	00000000000000000
	101	00000000000000000
HALT	011	10000000000000000
	100	00000000000000000
	101	00000000000000000

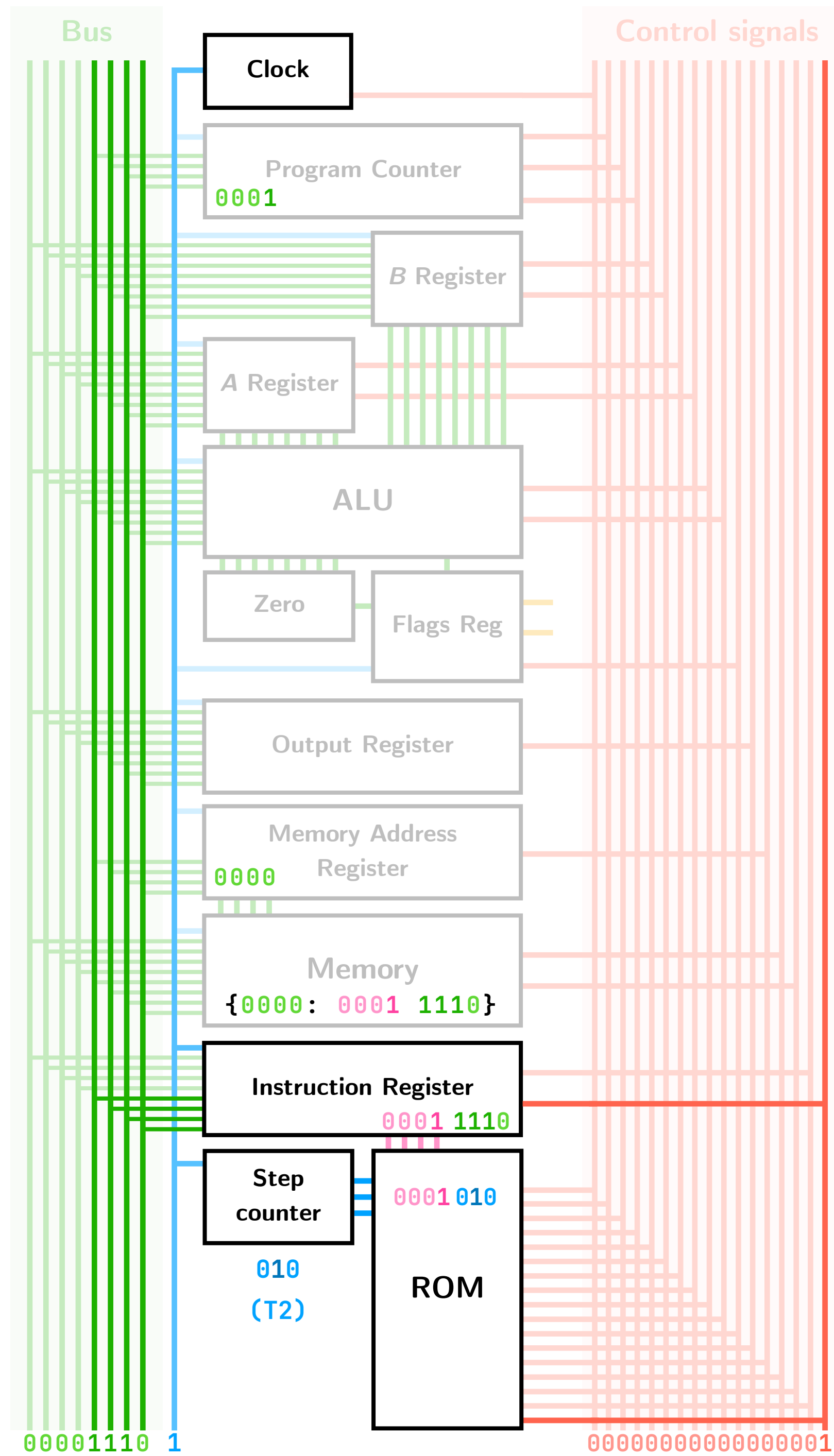


HL	HALT
CI	COUNTER_IN
CO	COUNTER_OUT
CE	COUNTER_ENABLE
BI	B_IN
BO	B_OUT
AI	A_IN
AO	A_OUT
SU	SUBTRACT
EO	ALU_OUT
CF	CARRY_FLAG
ZF	ZERO_FLAG
FI	FLAGS_IN
OI	OUTPUT_IN
MA	MEMORY_ADDRESS_IN
MI	MEMORY_IN
MO	MEMORY_OUT
II	INSTRUCTION_IN
IO	INSTRUCTION_OUT

Program		
[0]	LOAD	14
[1]	ADD	15
[2]	OUT	
[3]	HALT	
[14]	10	
[15]	20	


LOAD		
[0]	COUNTER_OUT	
[1]	MEMORY_OUT	
[2]	INSTRUCTION_IN	
[3]	COUNTER_ENABLE	
[4]	INSTRUCTION_OUT	
[5]	MEMORY_ADDRESS_IN	
[6]	MEMORY_OUT	
[7]	A_IN	

← ROM is continuously addressed  
Address changes mid-cycle  
But it's the same control word


IR can only write last 4 bits to bus →

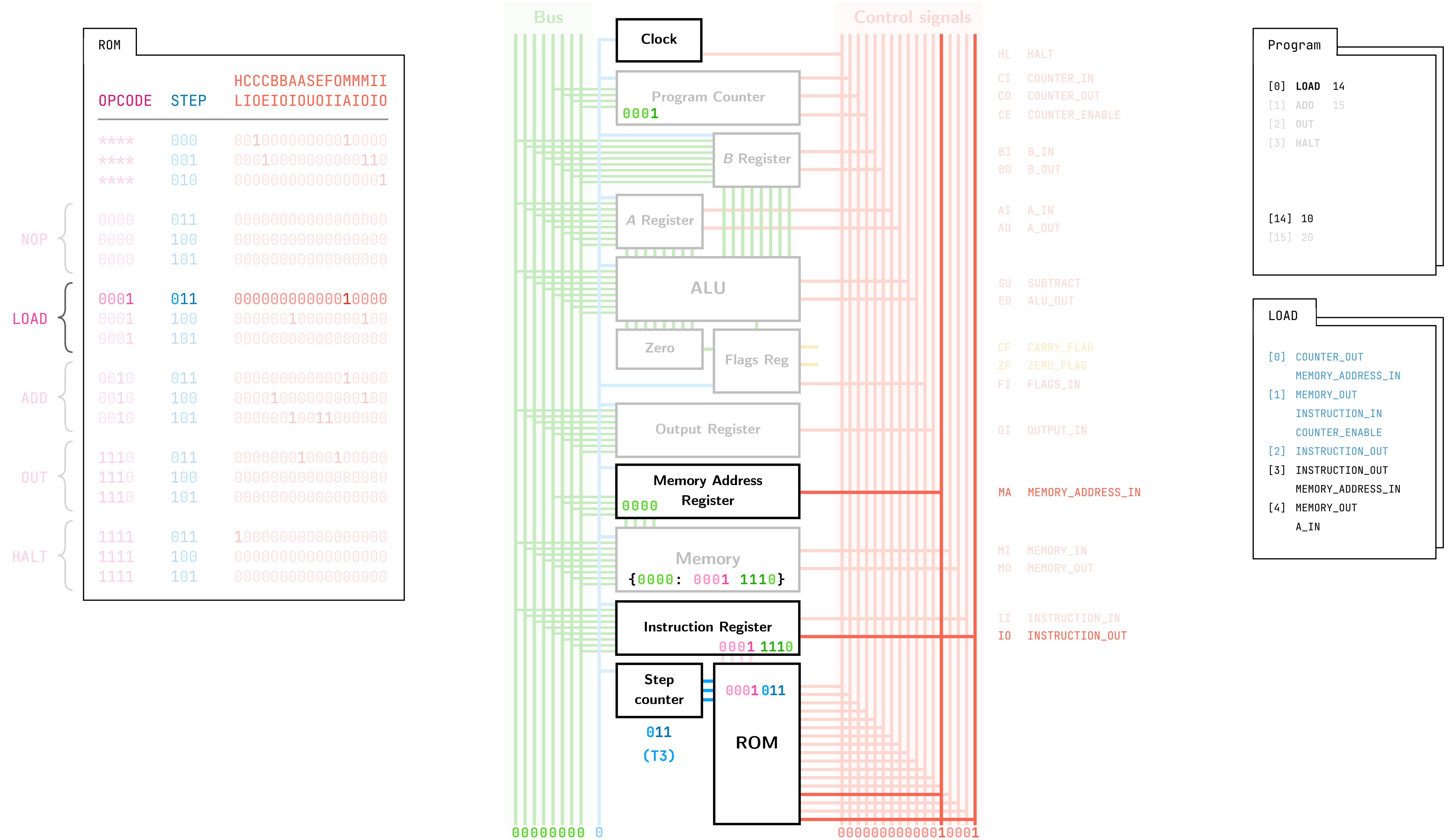




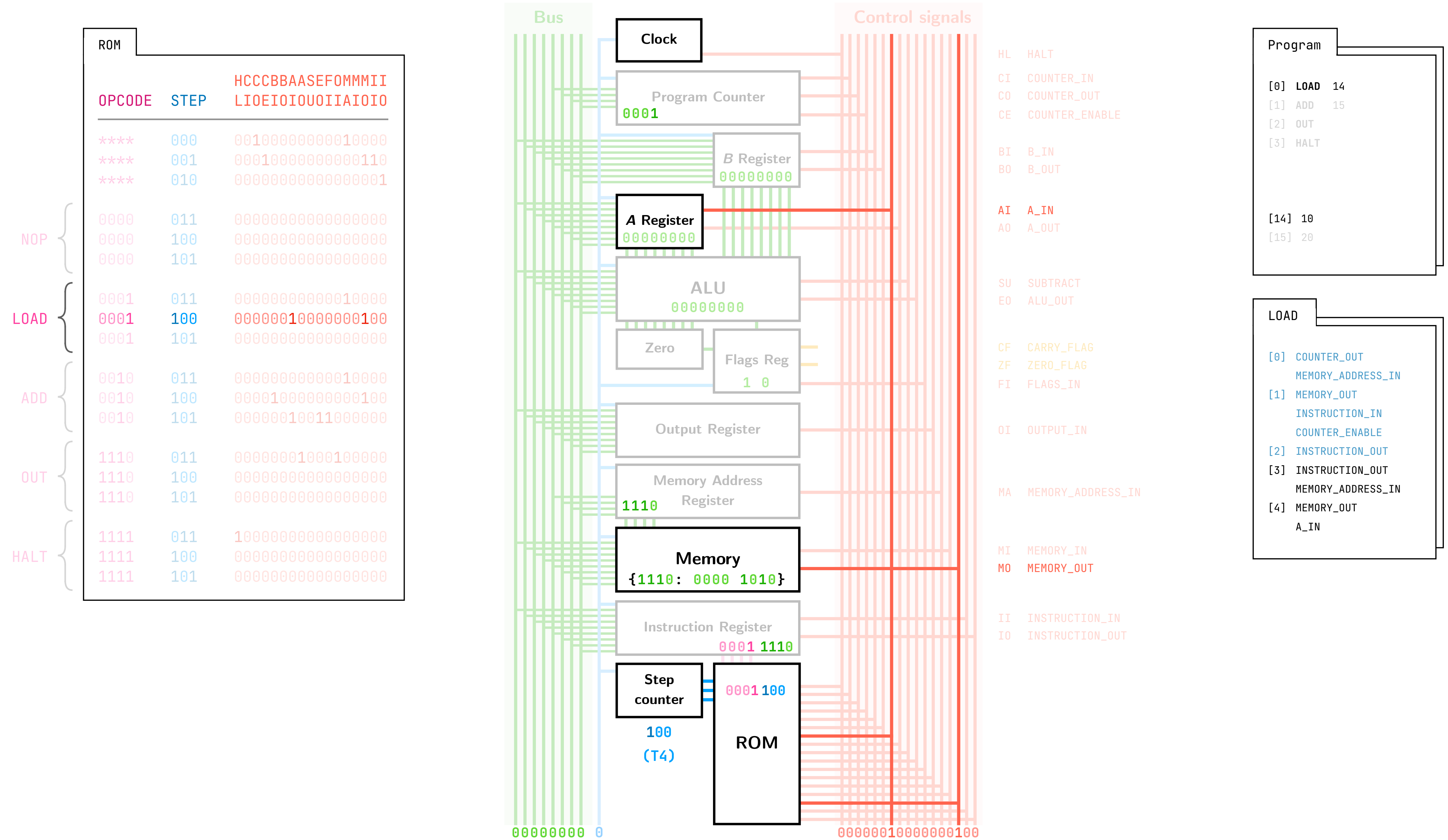




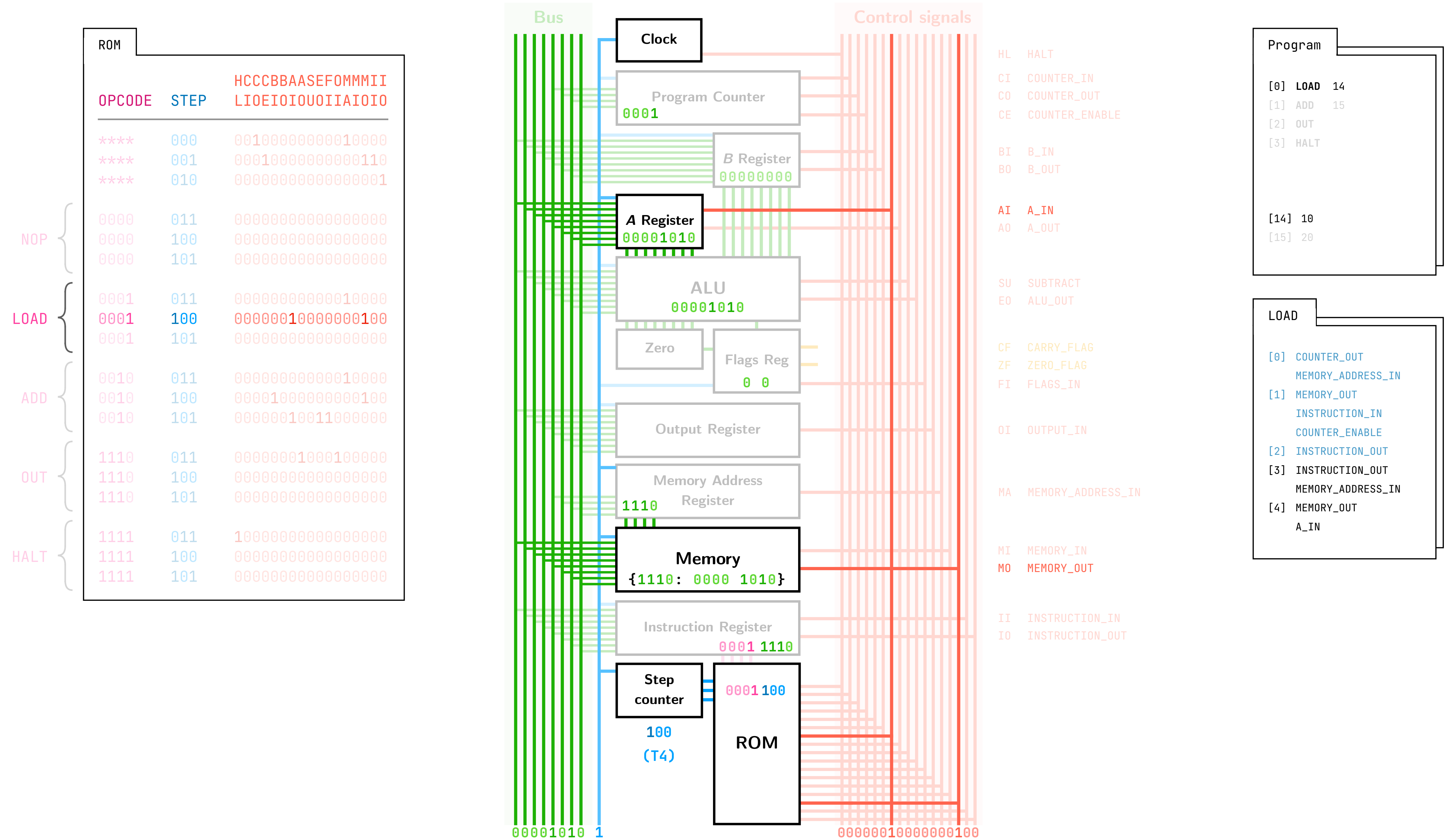



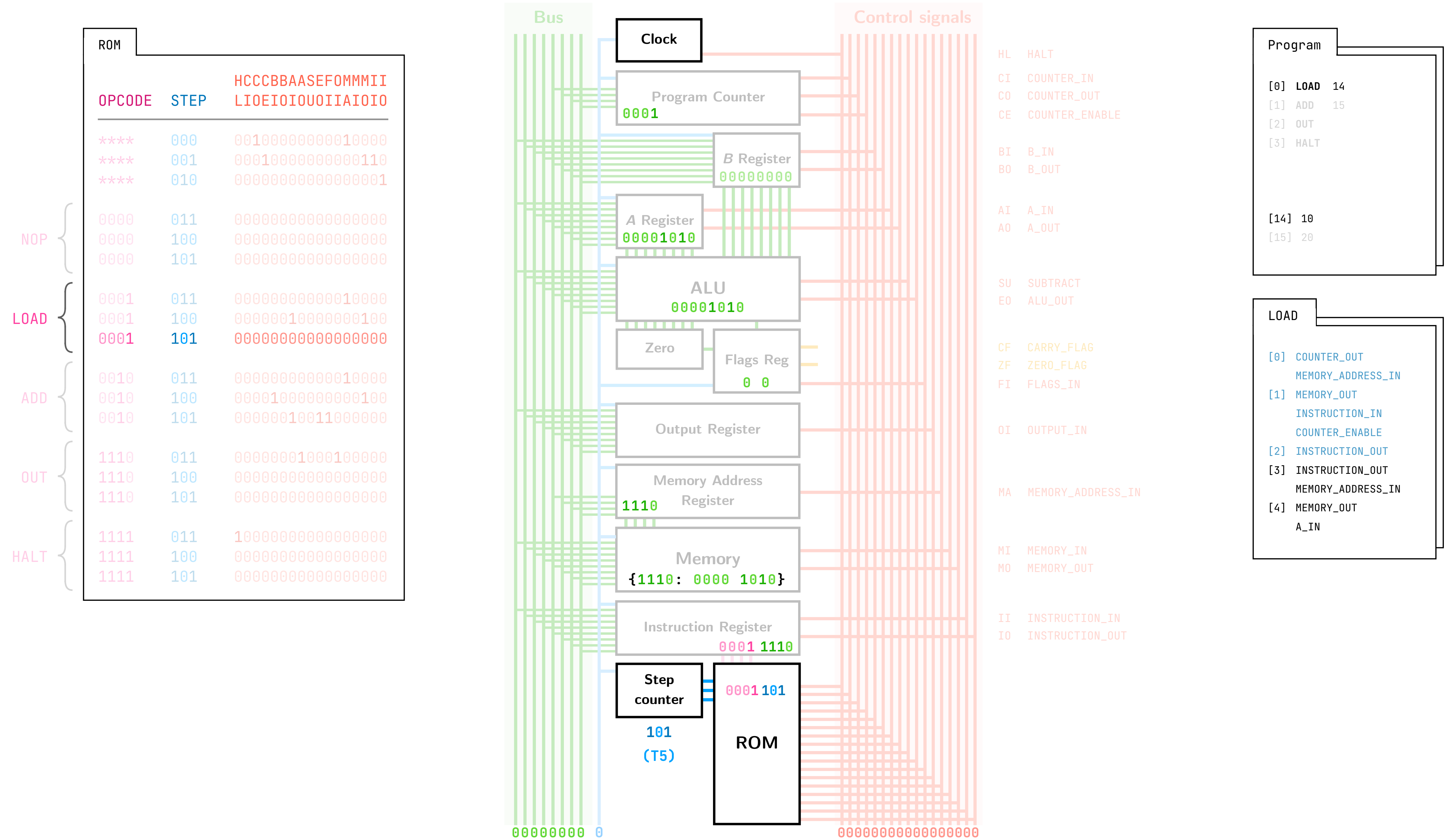


ROM		
		HCCCBBAASEFOMMMII LIOEIOIOUOIIAIOIO
OPCODE	STEP	
****	000	001000000000010000
****	001	00010000000000110
****	010	00000000000000001
0000	011	00000000000000000
0000	100	00000000000000000
0000	101	00000000000000000
0001	011	000000000000010000
0001	100	000000100000000100
0001	101	00000000000000000
0010	011	000000000000010000
0010	100	000010000000000100
0010	101	00000010011000000
1110	011	00000001000100000
1110	100	00000000000000000
1110	101	00000000000000000
1111	011	10000000000000000
1111	100	00000000000000000
1111	101	00000000000000000

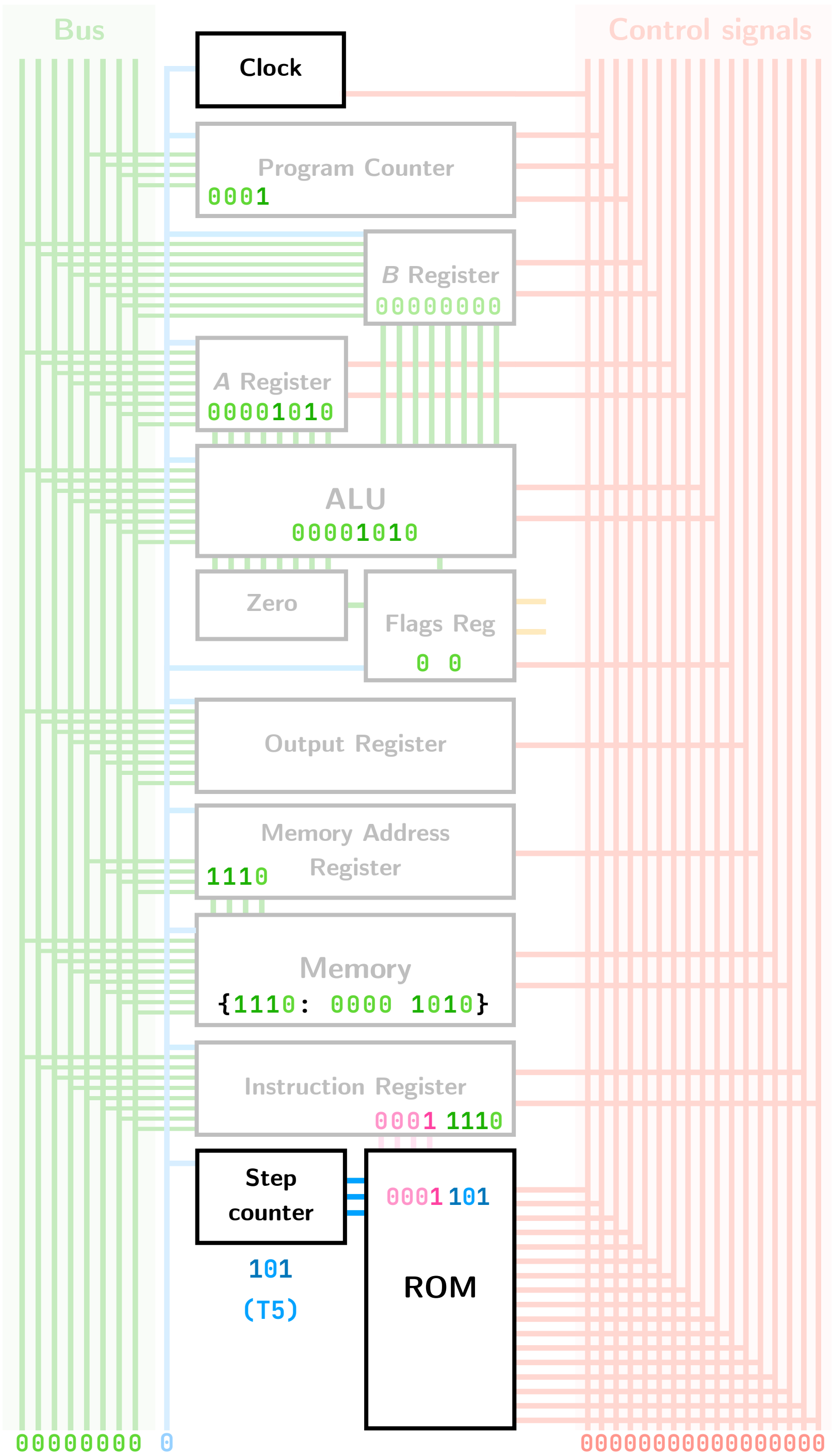



- Control signals
- HL HALT
  - CI COUNTER\_IN
  - CO COUNTER\_OUT
  - CE COUNTER\_ENABLE
  - BI B\_IN
  - BO B\_OUT
  - AI A\_IN
  - AO A\_OUT
  - SU SUBTRACT
  - EO ALU\_OUT
  - CF CARRY\_FLAG
  - ZF ZERO\_FLAG
  - FI FLAGS\_IN
  - OI OUTPUT\_IN
  - MA MEMORY\_ADDRESS\_IN
  - MI MEMORY\_IN
  - MO MEMORY\_OUT
  - II INSTRUCTION\_IN
  - IO INSTRUCTION\_OUT


Program		
[0]	LOAD	14
[1]	ADD	15
[2]	OUT	
[3]	HALT	
[14]	10	
[15]	20	


LOAD		
[0]	COUNTER_OUT	
	MEMORY_ADDRESS_IN	
[1]	MEMORY_OUT	
	INSTRUCTION_IN	
	COUNTER_ENABLE	
[2]	INSTRUCTION_OUT	
[3]	INSTRUCTION_OUT	
	MEMORY_ADDRESS_IN	
[4]	MEMORY_OUT	
	A_IN	

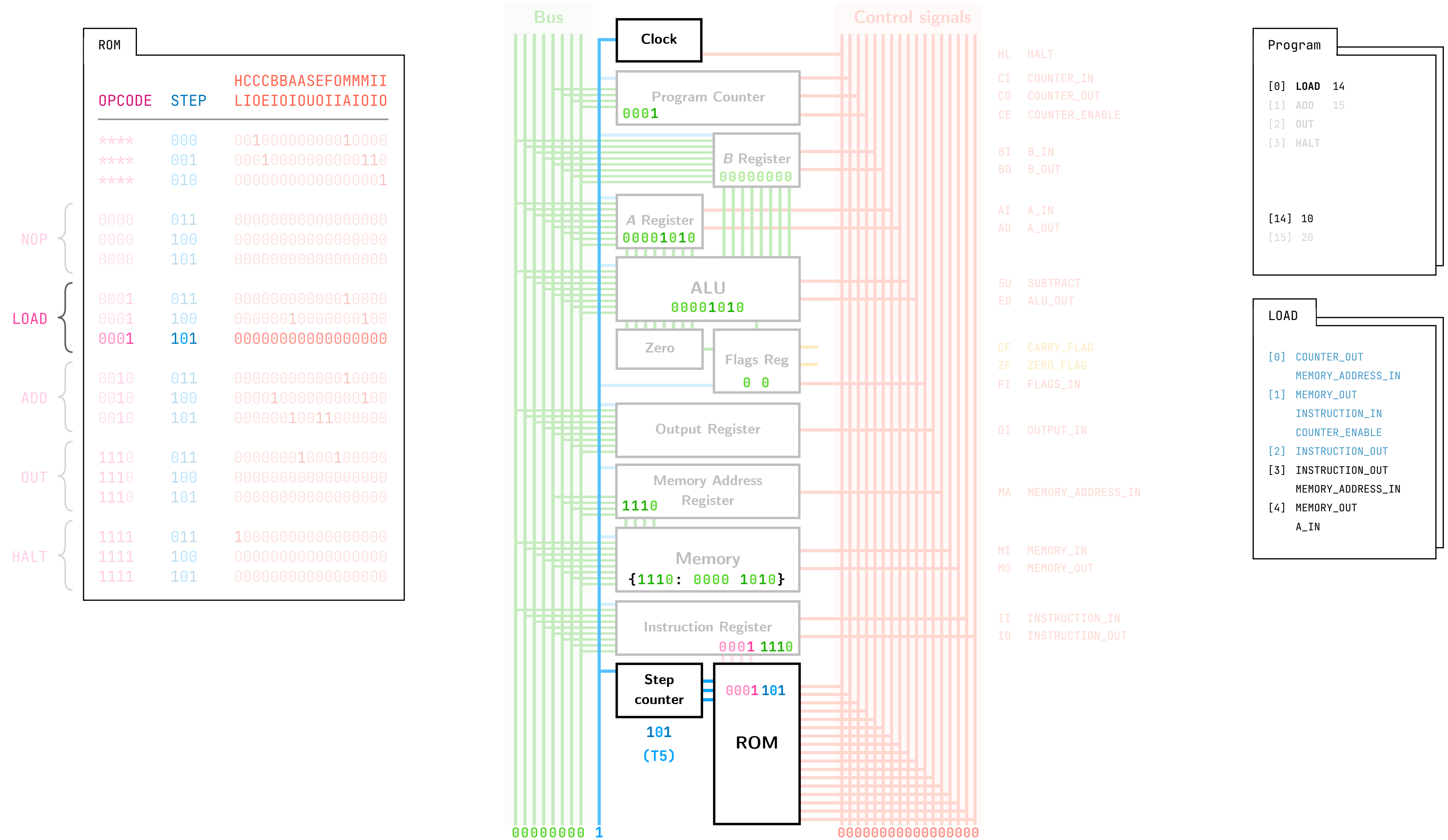


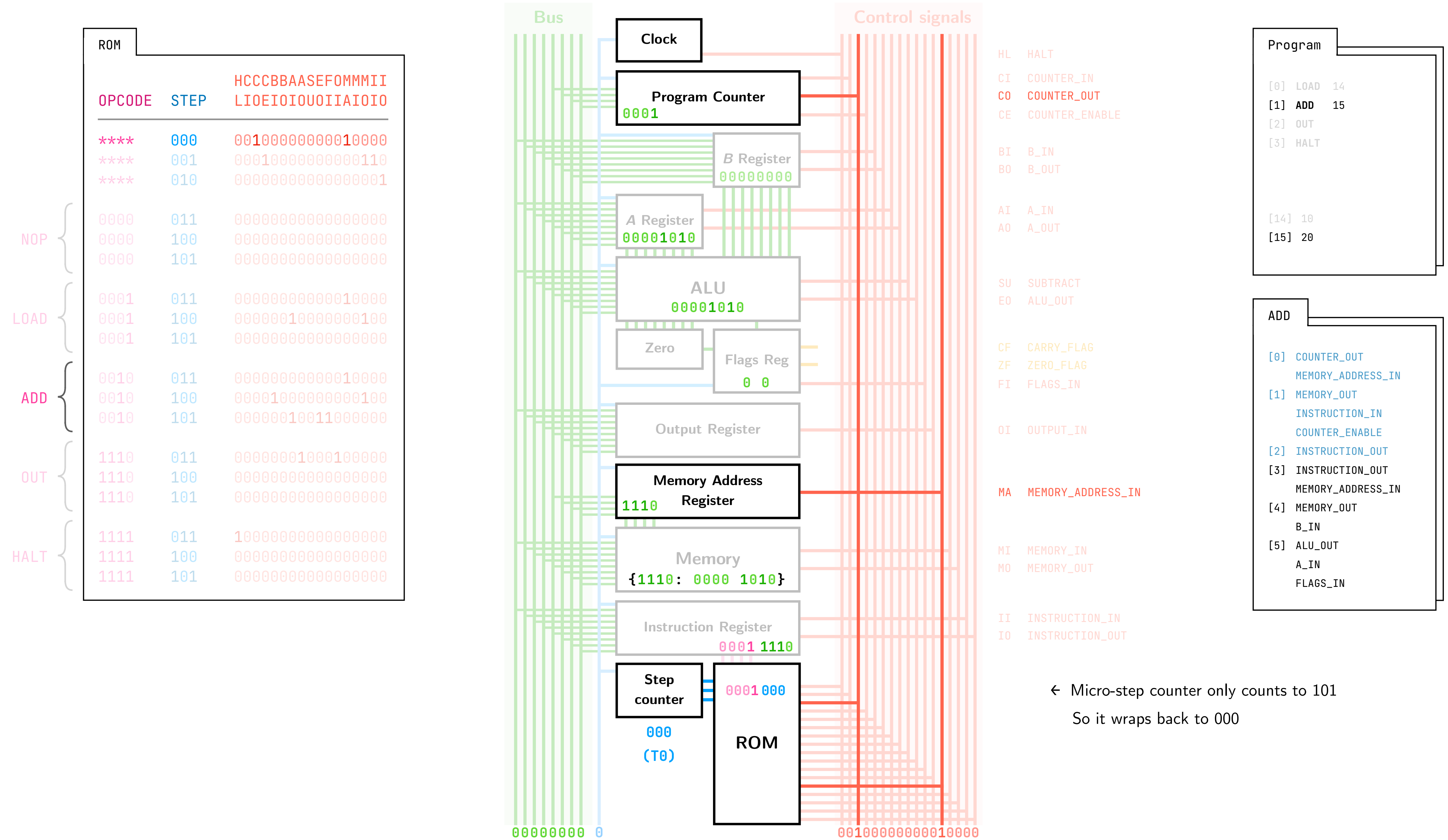

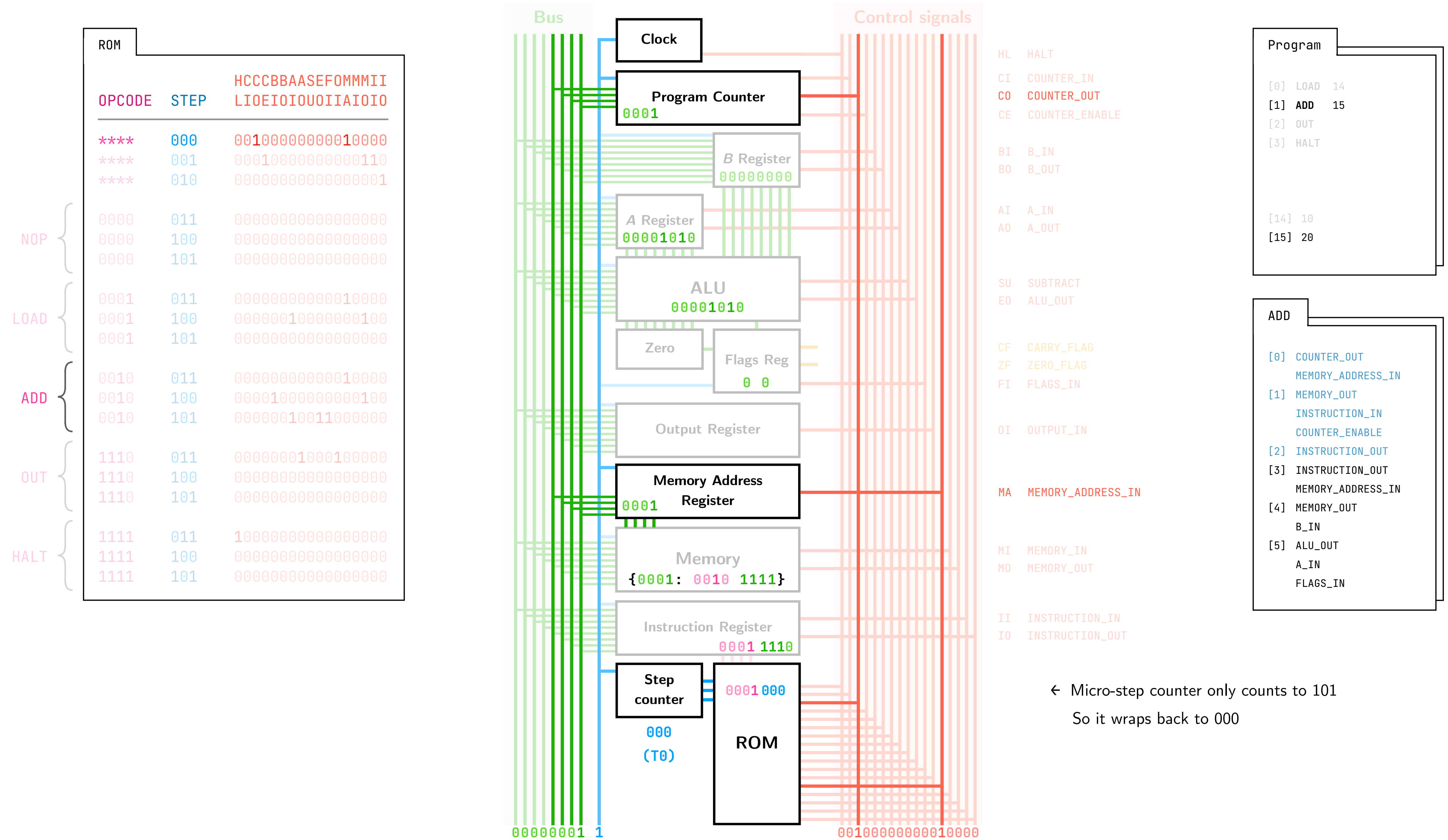

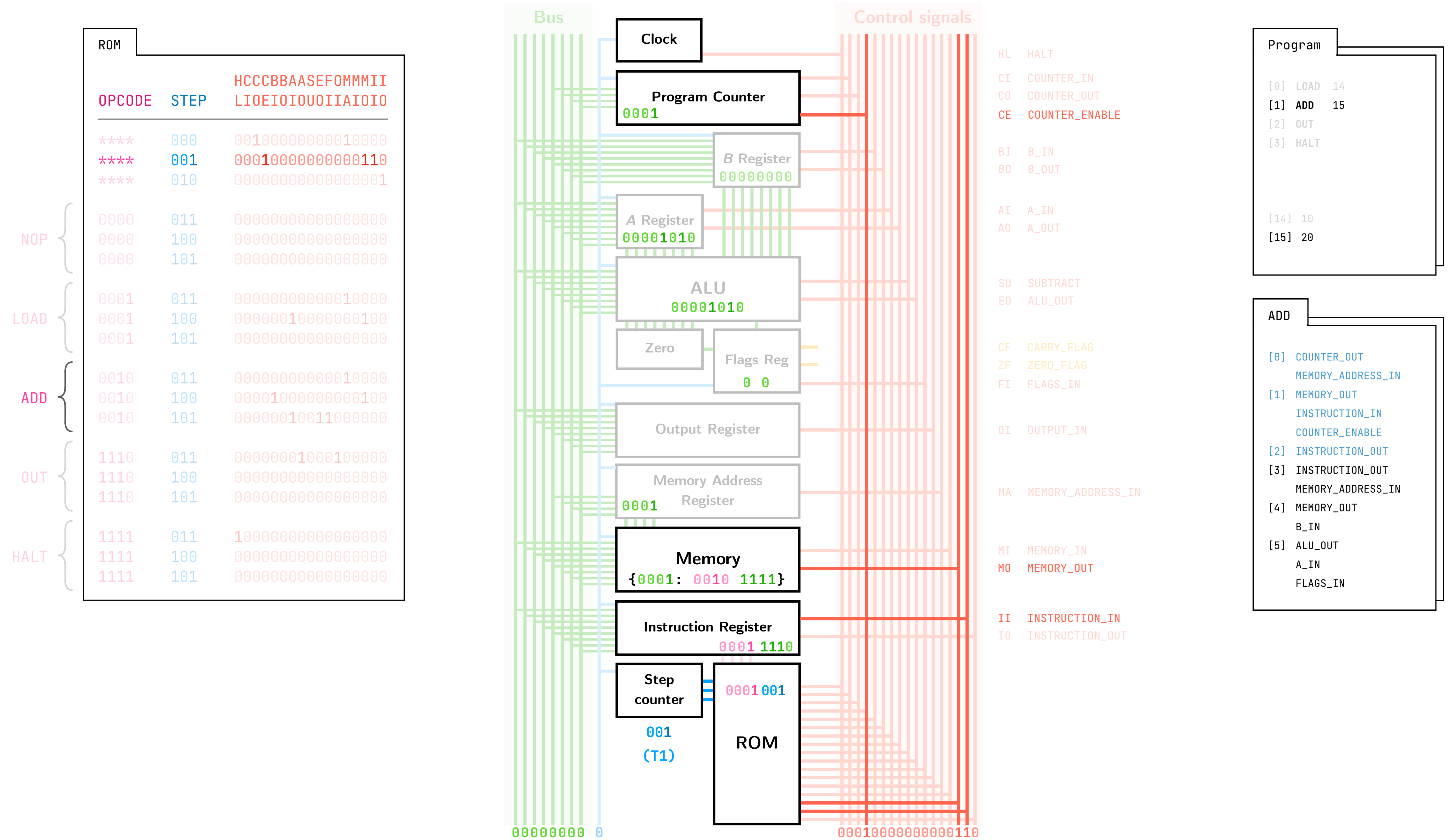


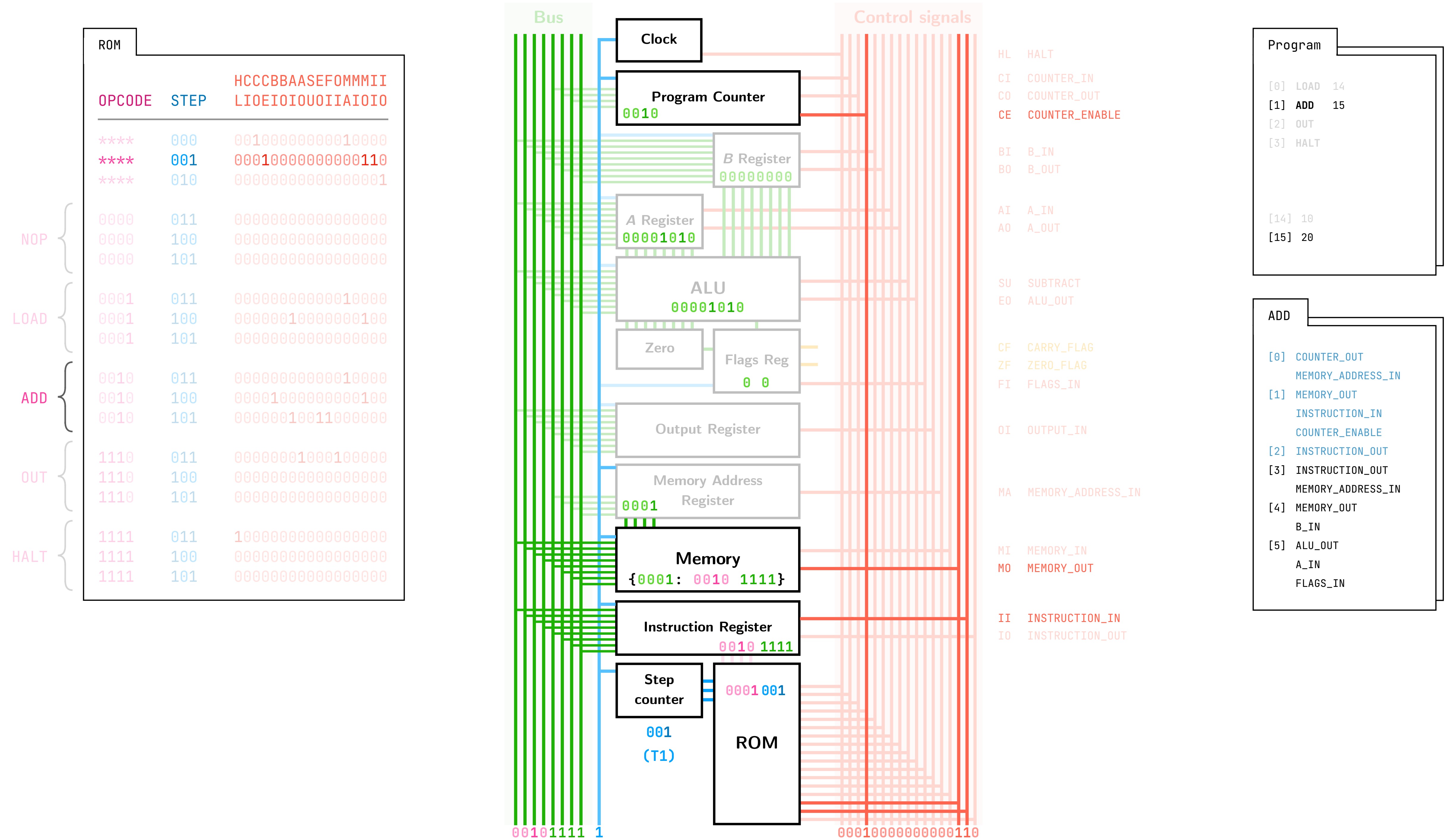

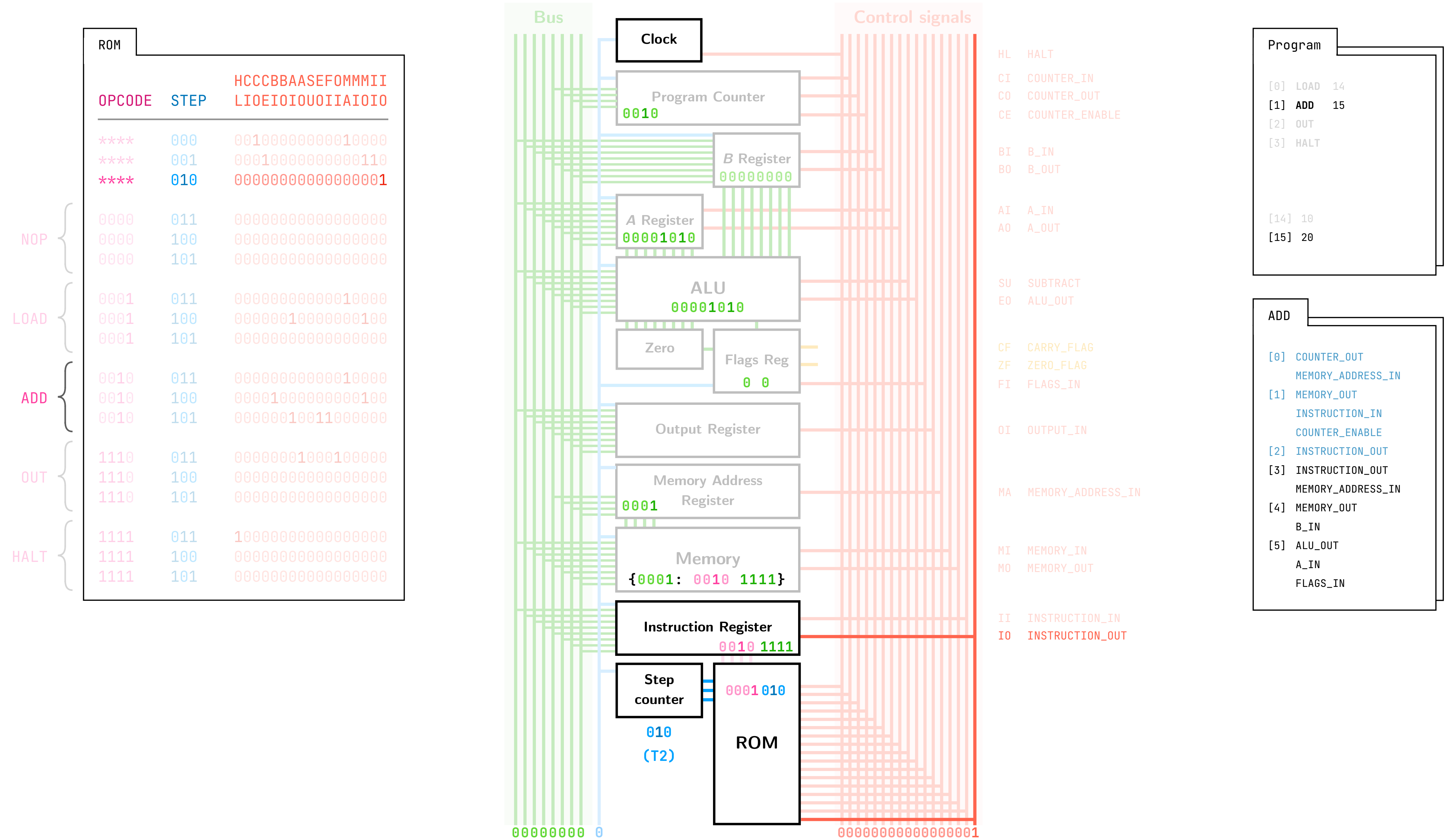



ROM		
OPCODE	STEP	HCCCBBAASEFOMMMII LIOEIOIOUOIIAIOIO
****	000	00100000000010000
****	001	00010000000000110
****	010	00000000000000001
NOP	011	00000000000000000
	100	00000000000000000
	101	00000000000000000
LOAD	011	00000000000010000
	100	00000010000000100
	101	00000000000000000
ADD	011	00000000000010000
	100	00001000000000100
	101	00000010011000000
OUT	011	00000001000100000
	100	00000000000000000
	101	00000000000000000
HALT	011	10000000000000000
	100	00000000000000000
	101	00000000000000000

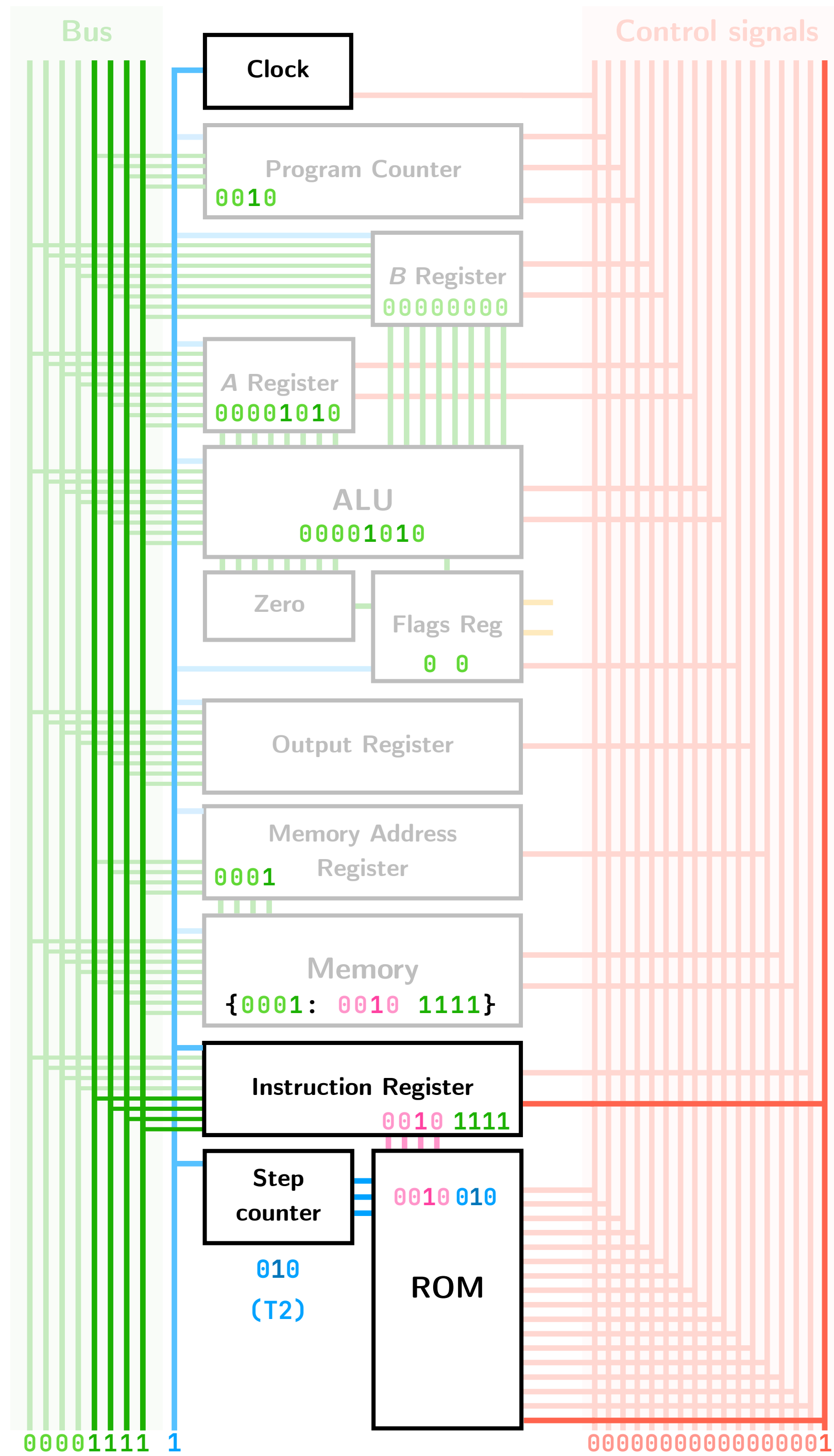


HL	HALT
CI	COUNTER_IN
CO	COUNTER_OUT
CE	COUNTER_ENABLE
BI	B_IN
BO	B_OUT
AI	A_IN
AO	A_OUT
SU	SUBTRACT
EO	ALU_OUT
CF	CARRY_FLAG
ZF	ZERO_FLAG
FI	FLAGS_IN
OI	OUTPUT_IN
MA	MEMORY_ADDRESS_IN
MI	MEMORY_IN
MO	MEMORY_OUT
II	INSTRUCTION_IN
IO	INSTRUCTION_OUT


Program		
[0]	LOAD	14
[1]	ADD	15
[2]	OUT	
[3]	HALT	
[14]	10	
[15]	20	


ADD		
[0]	COUNTER_OUT	
[1]	MEMORY_OUT	
[2]	INSTRUCTION_OUT	
[3]	INSTRUCTION_OUT	
[4]	MEMORY_OUT	
[5]	B_IN	
[5]	ALU_OUT	
	A_IN	
	FLAGS_IN	

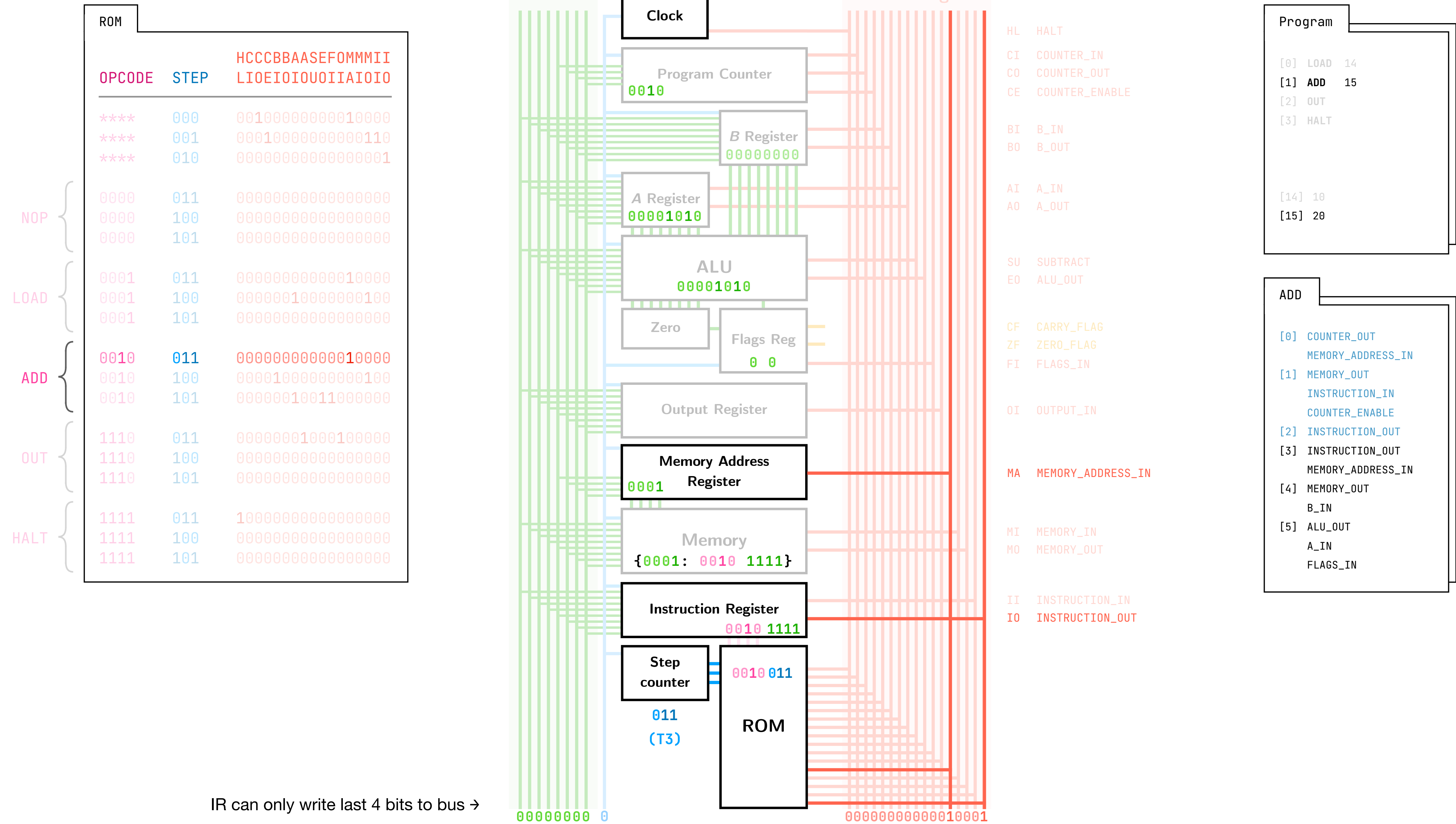← ROM is continuously addressed  
Address changes mid-cycle  
But it's the same control word







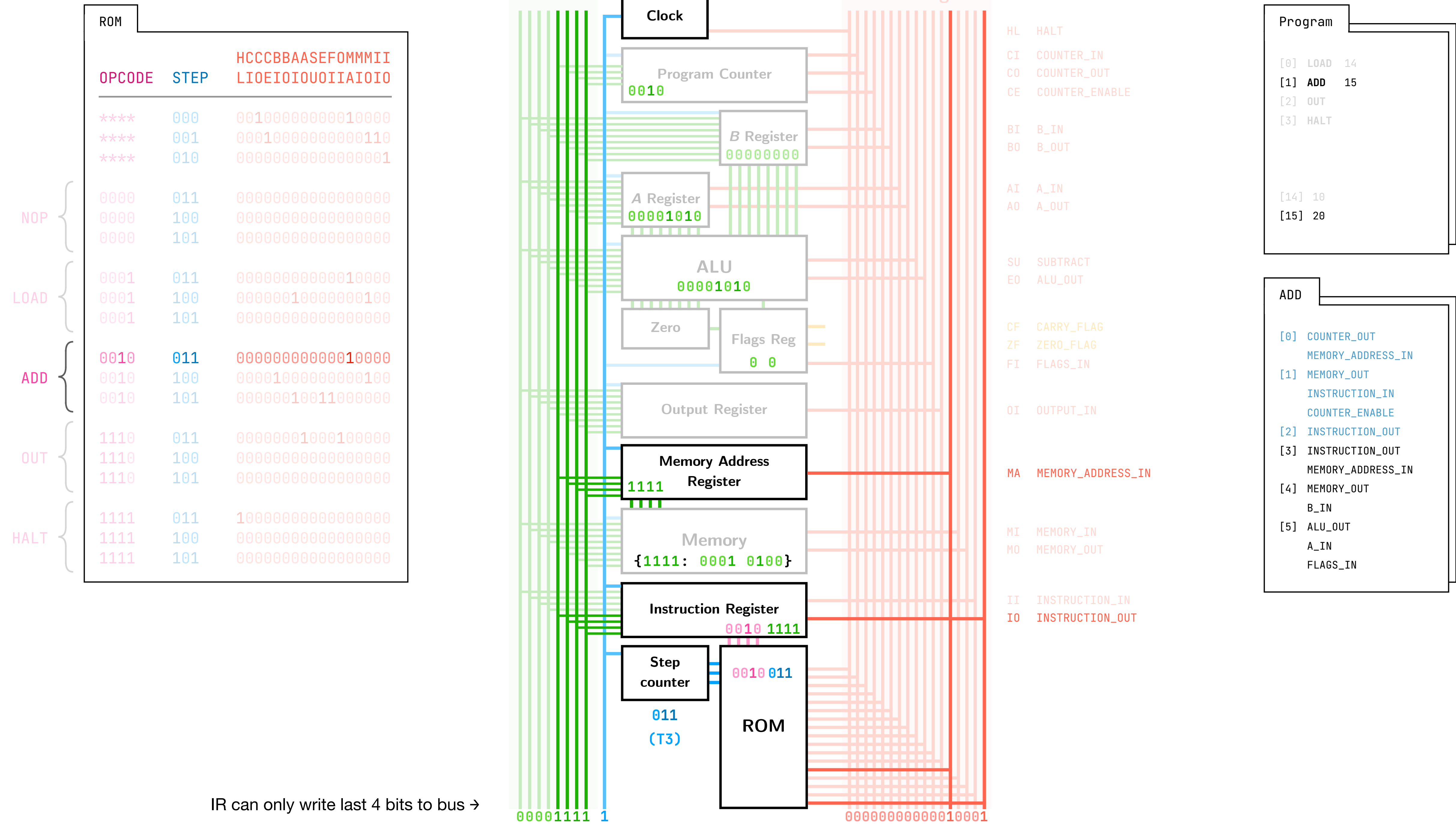


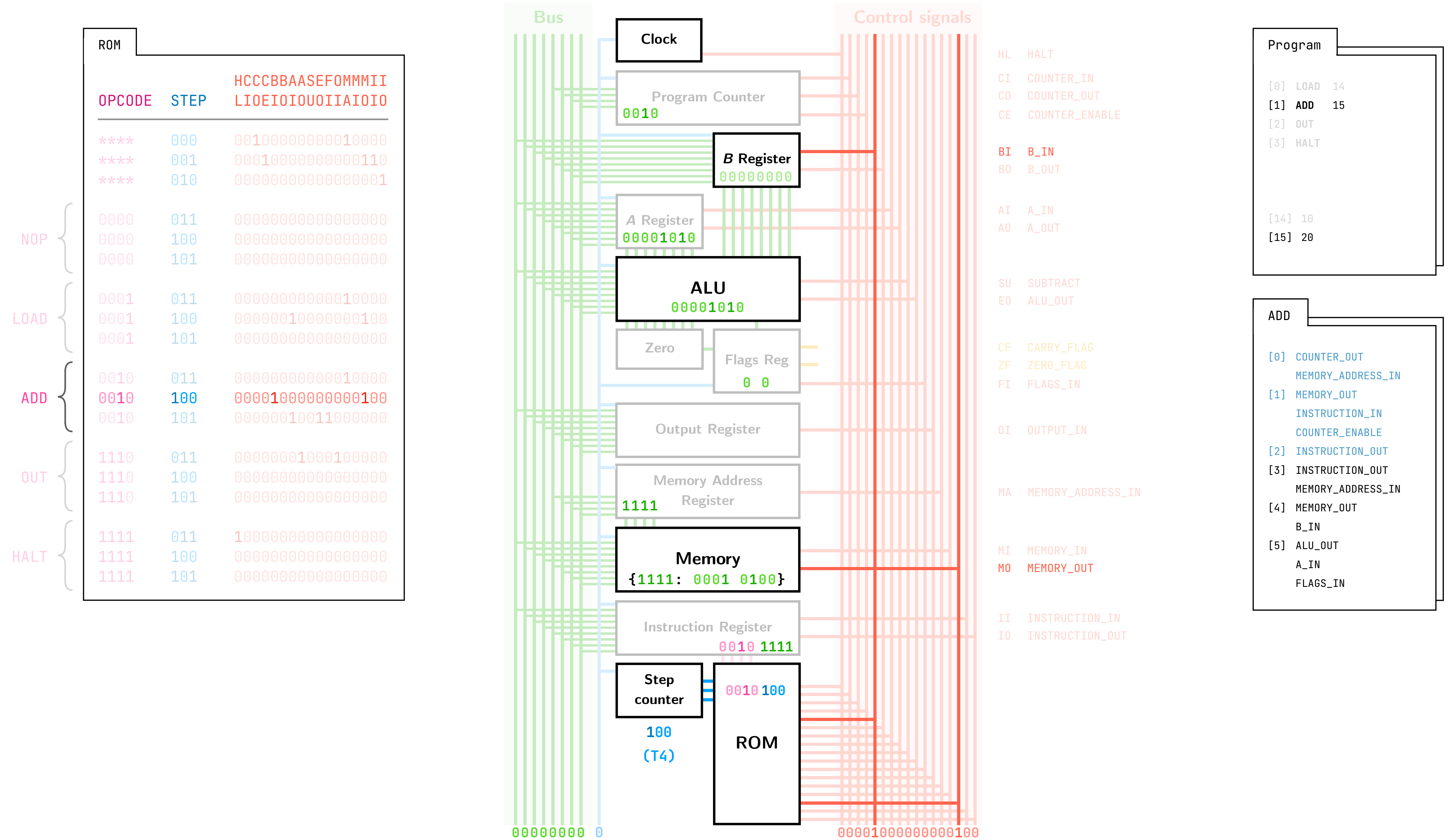




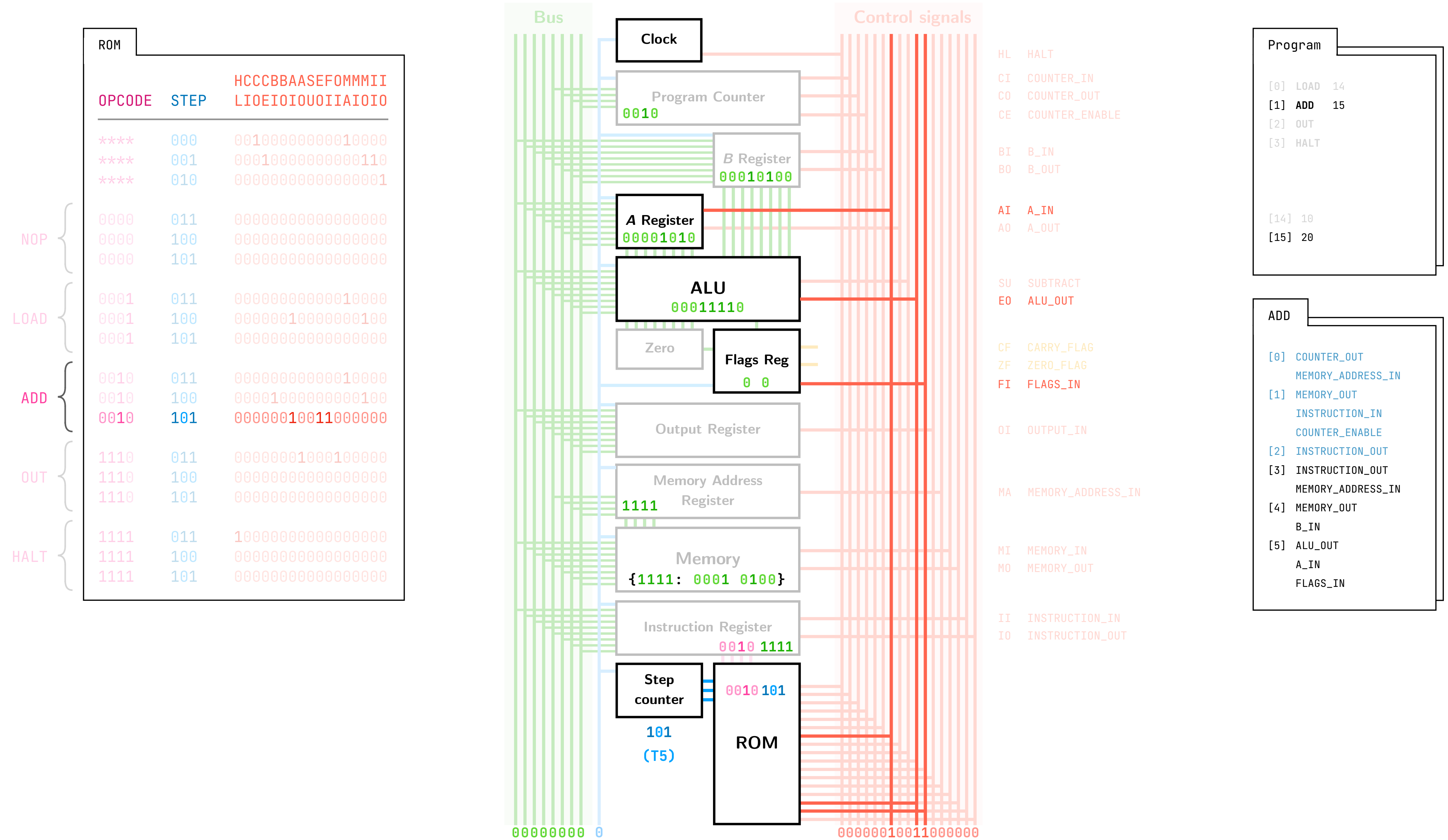

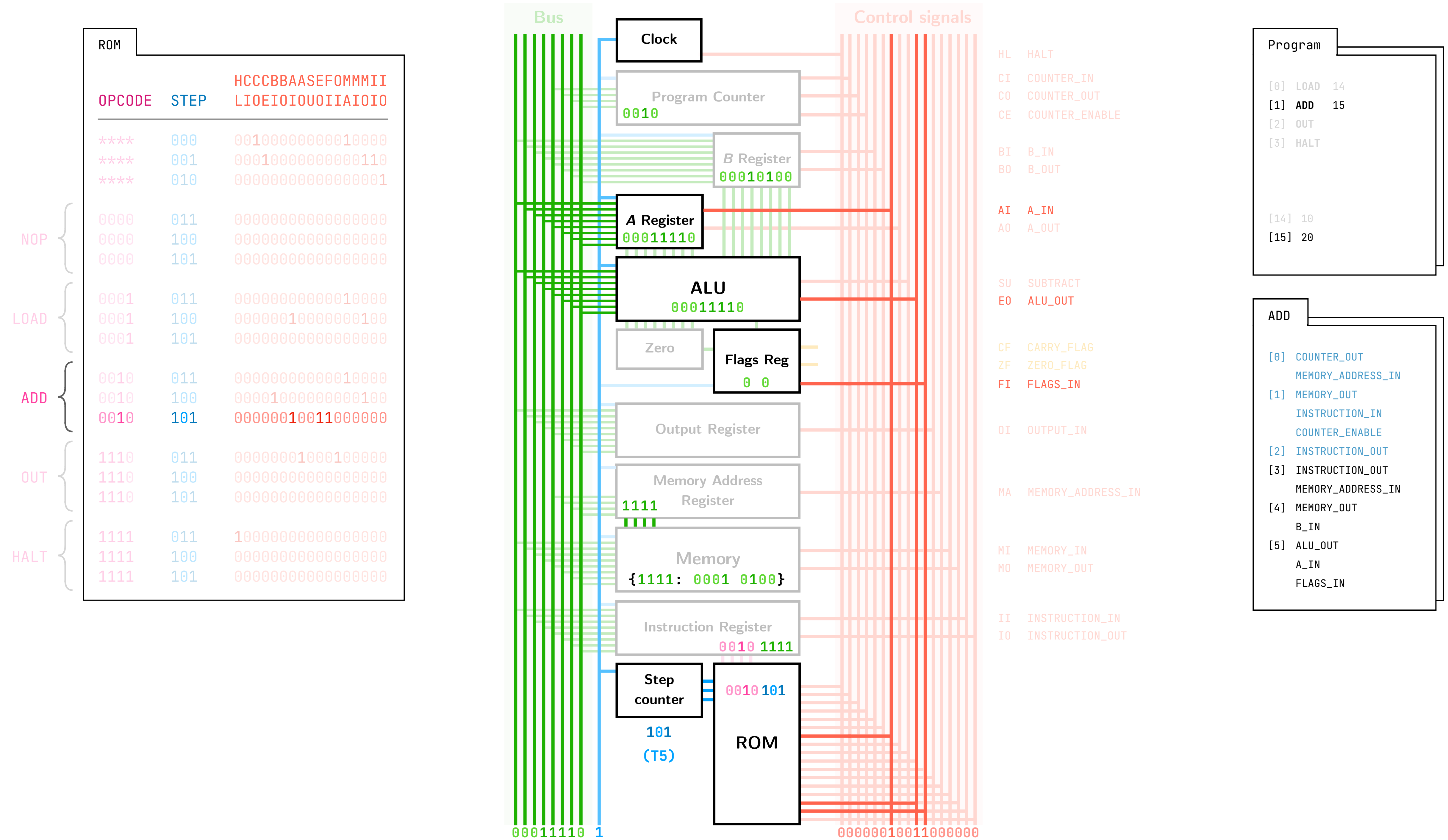


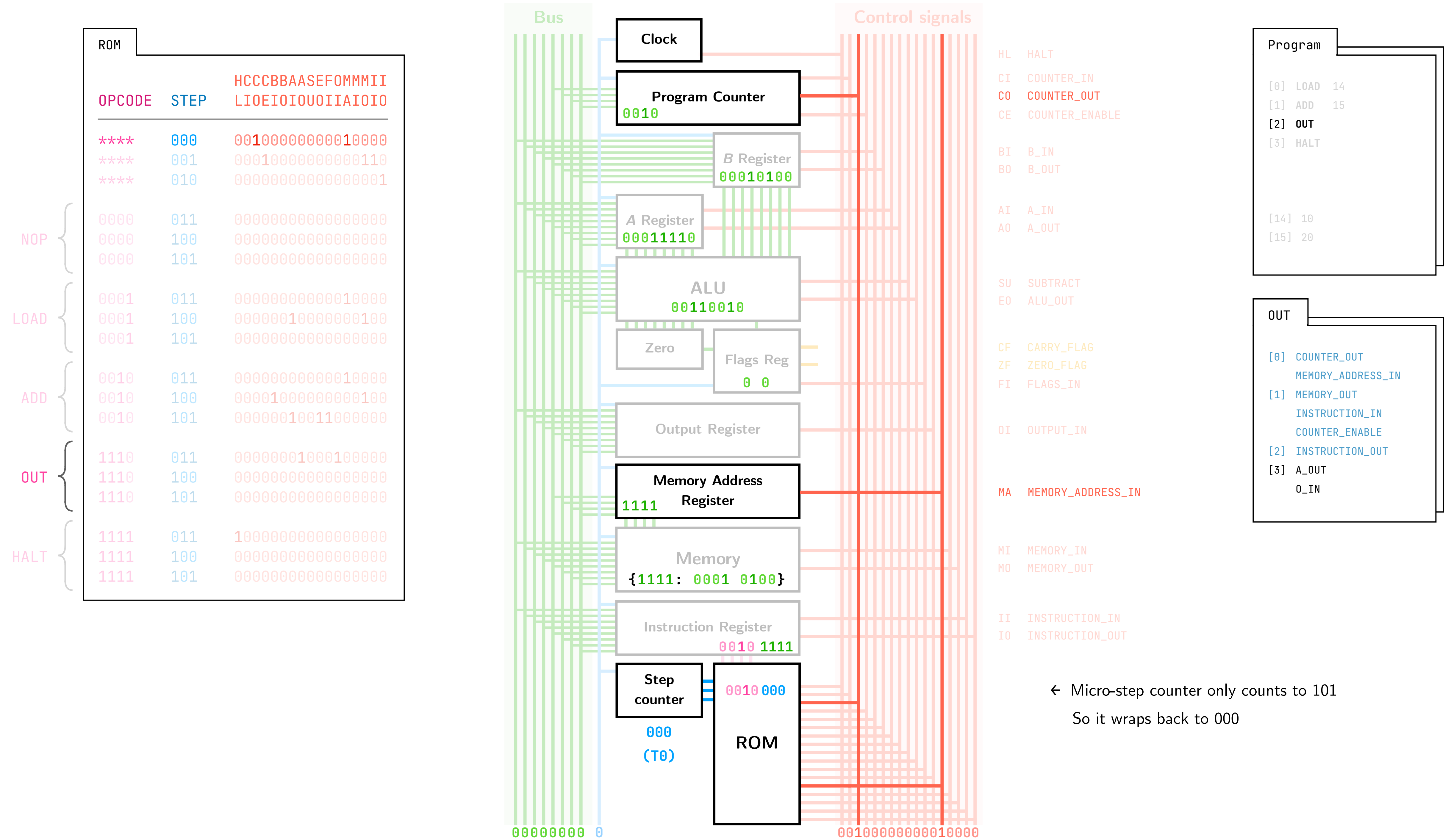





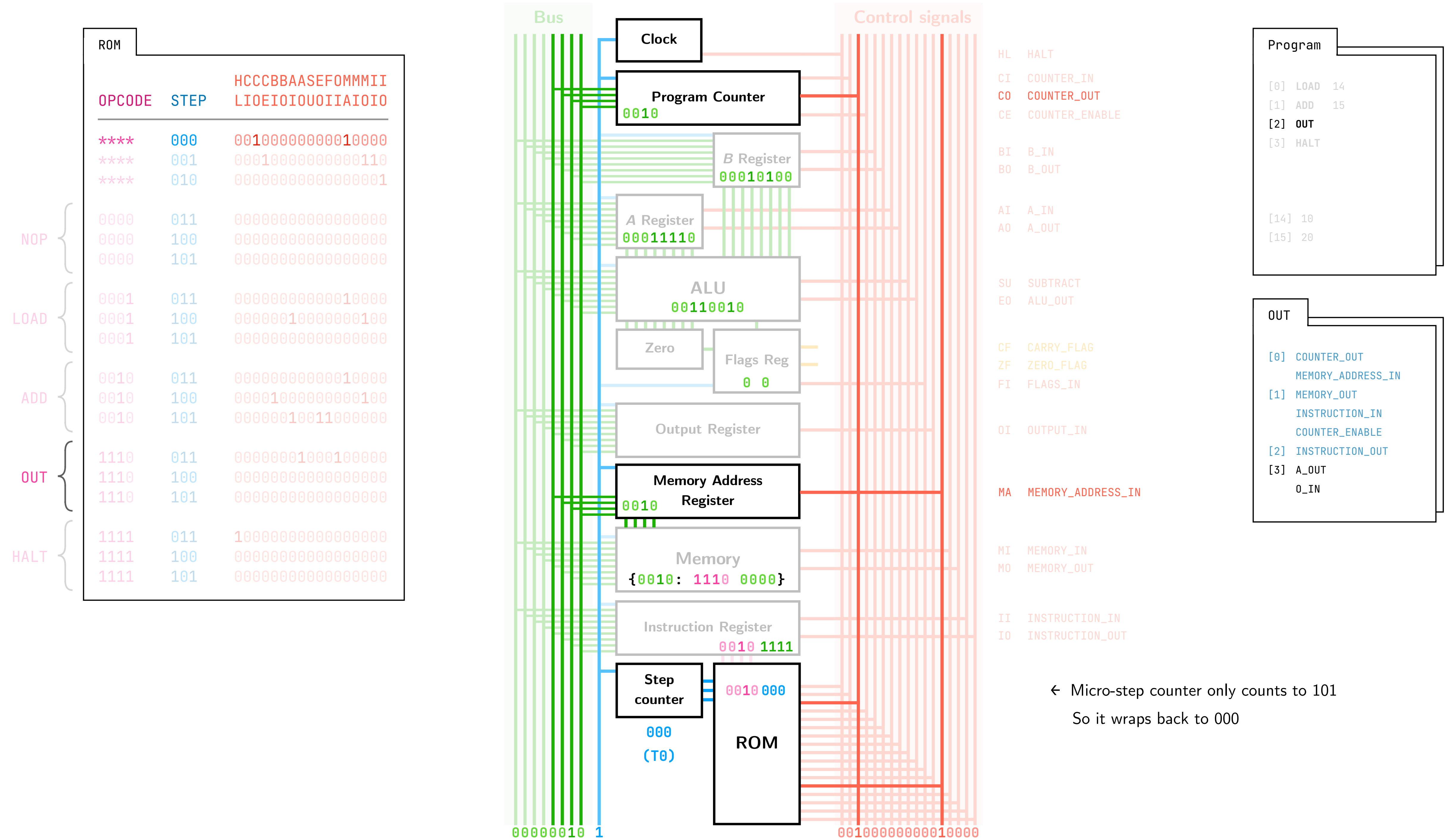




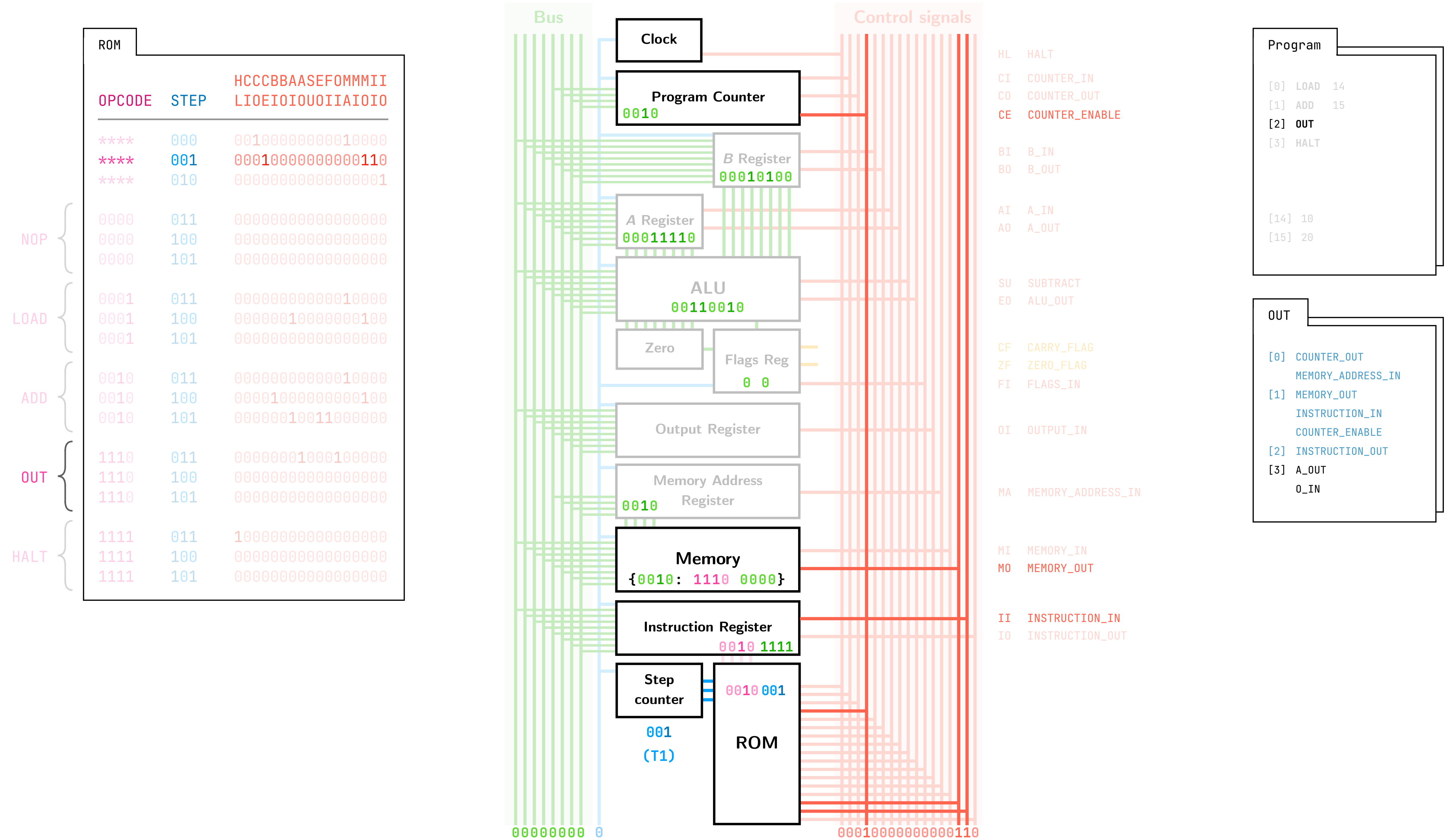


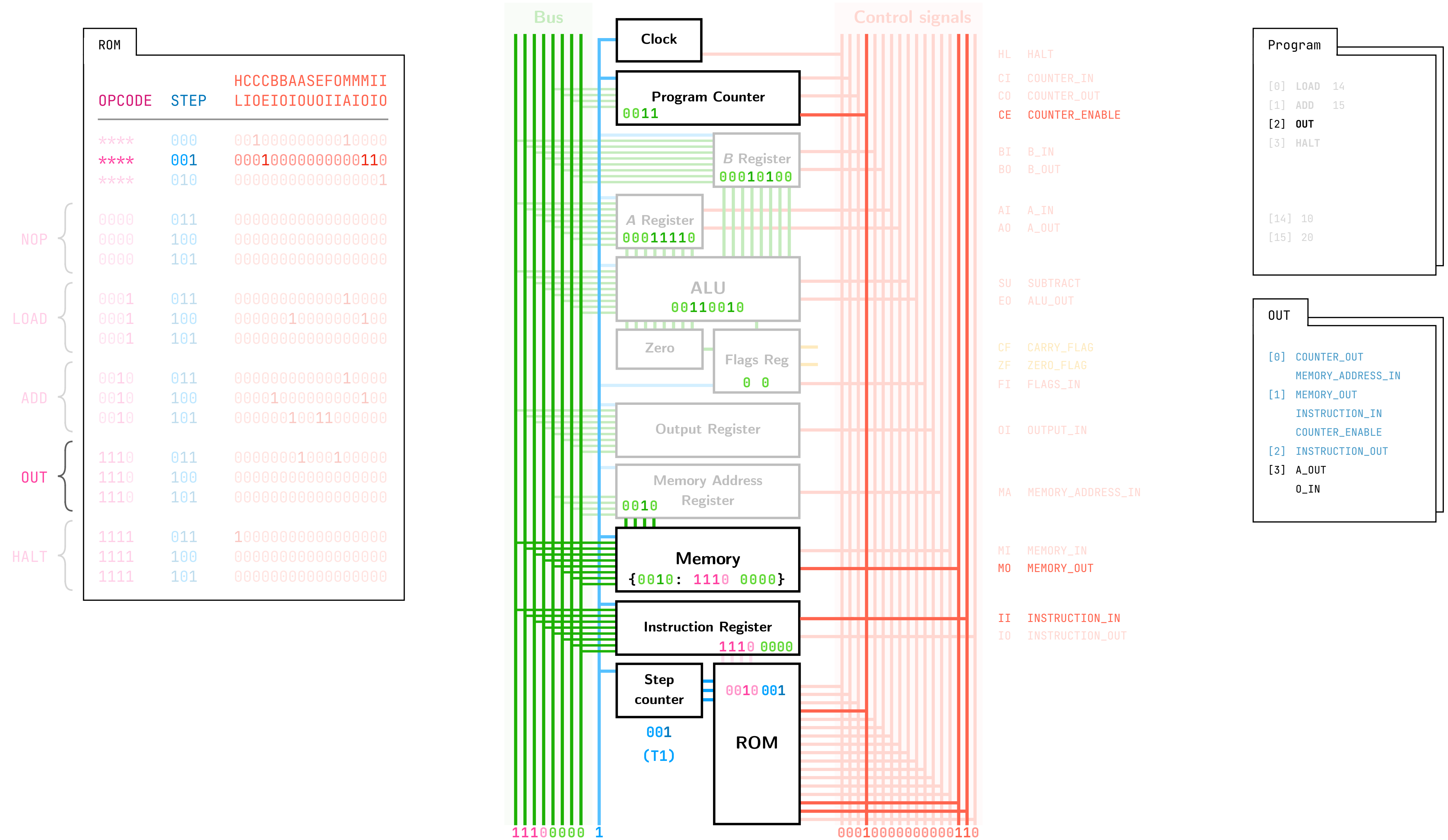


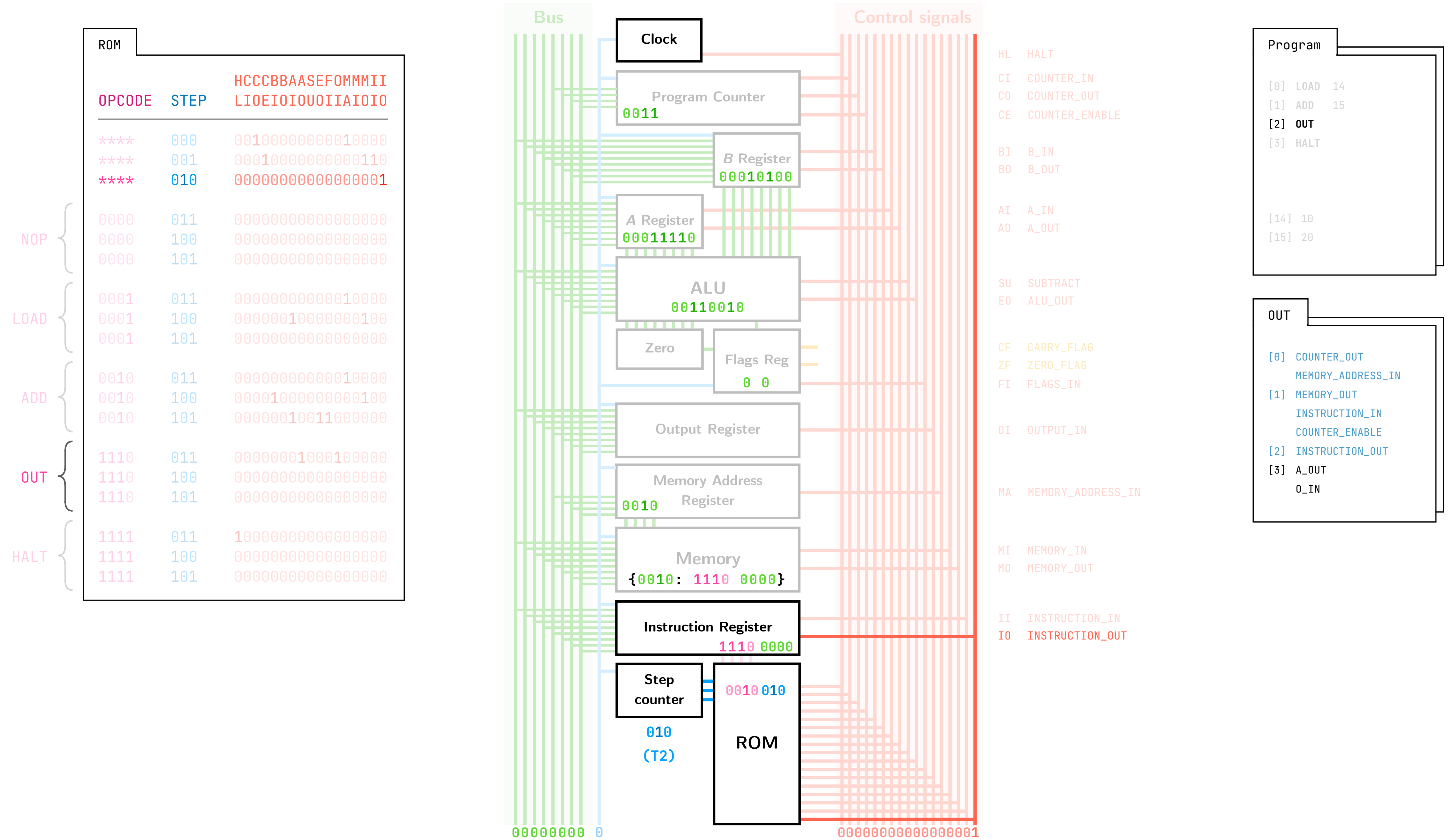


ROM		
OPCODE	STEP	HCCCBBAASEFOMMMII LIOEIOIOUOIIAIOIO
****	000	00100000000010000
****	001	00010000000000110
****	010	00000000000000001
NOP	011	00000000000000000
	100	00000000000000000
	101	00000000000000000
LOAD	011	00000000000010000
	100	00000010000000100
	101	00000000000000000
ADD	011	00000000000010000
	100	00001000000000100
	101	00000010011000000
OUT	011	00000001000100000
	100	00000000000000000
	101	00000000000000000
HALT	011	10000000000000000
	100	00000000000000000
	101	00000000000000000

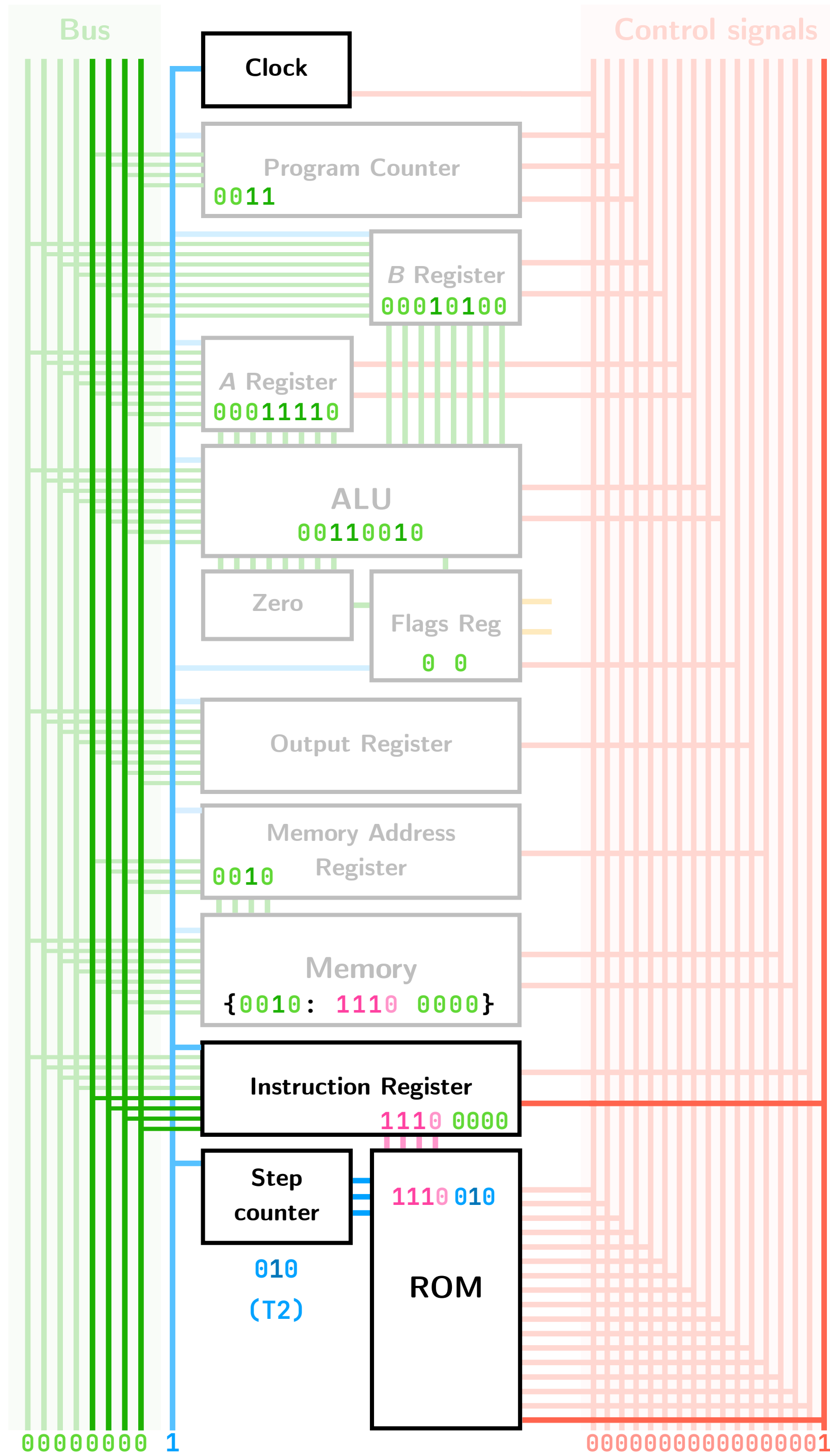


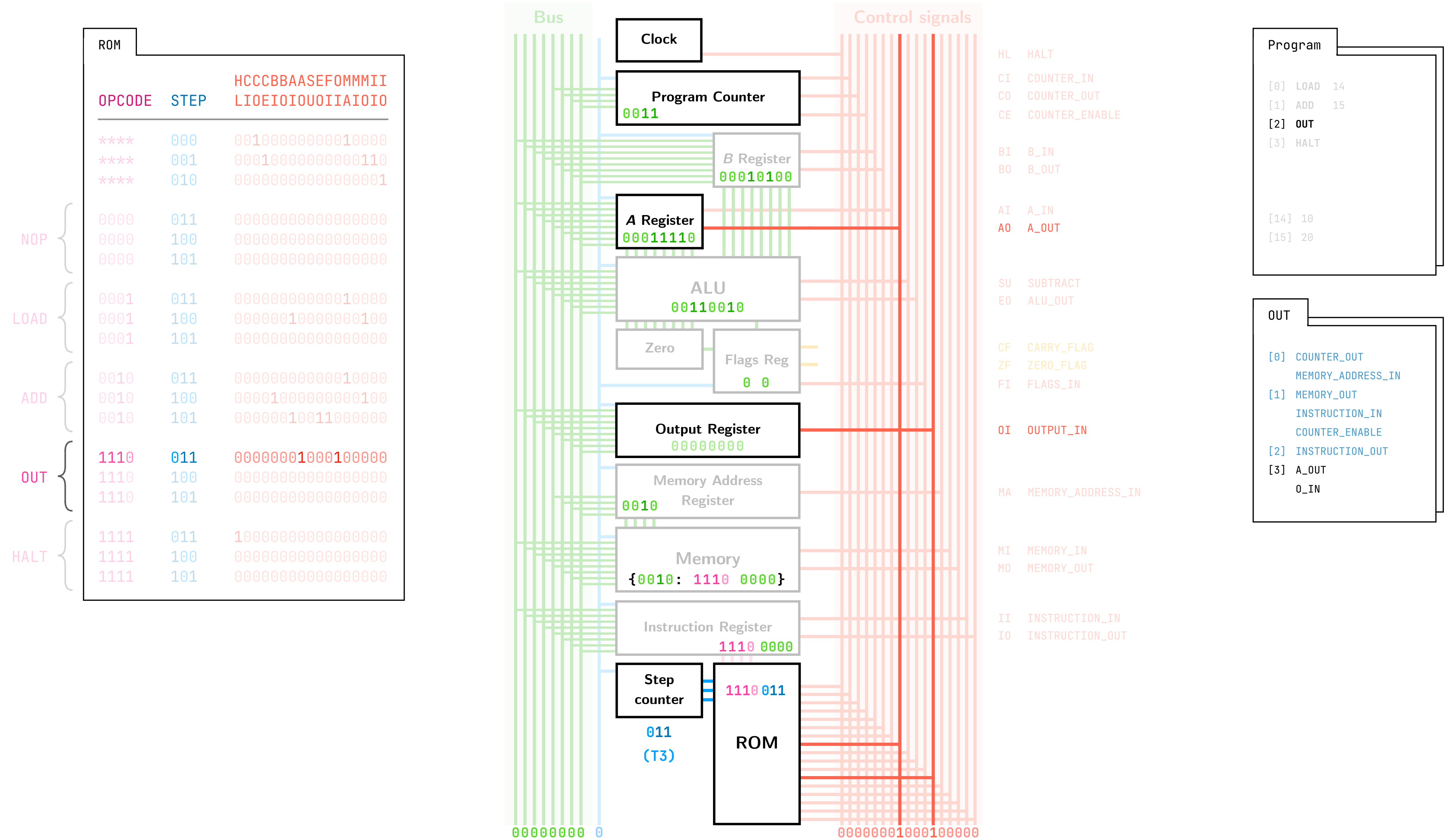

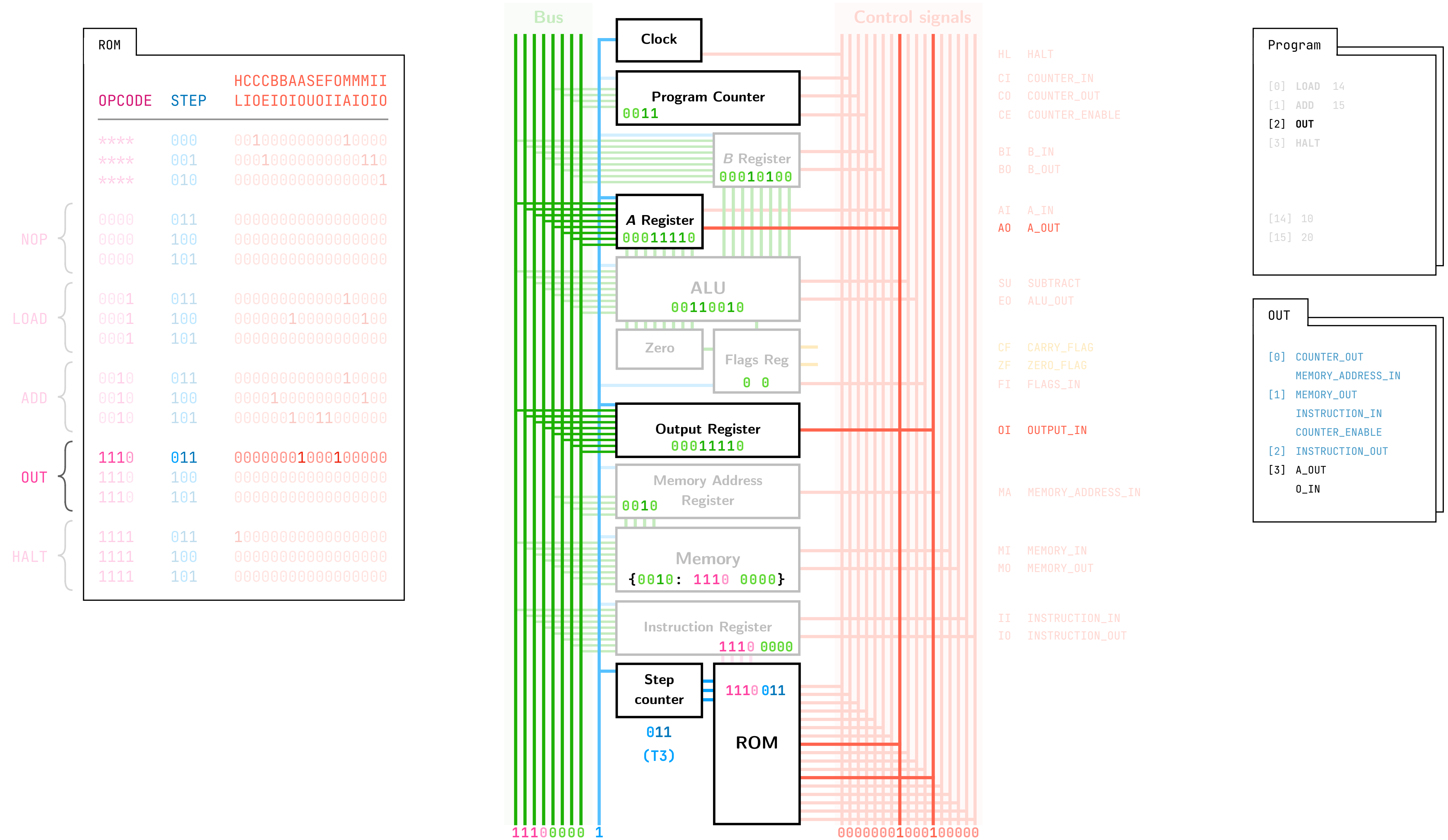


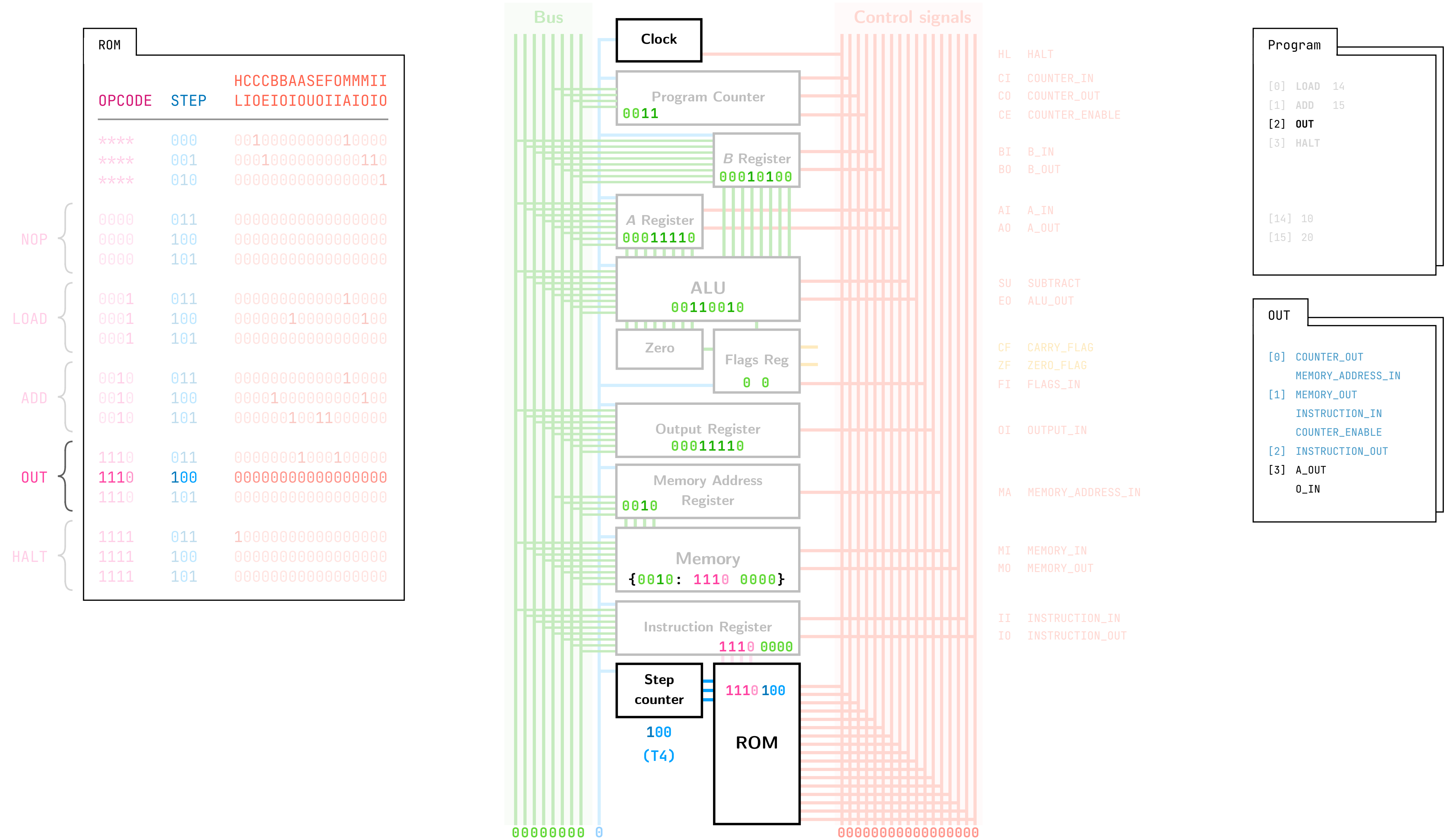





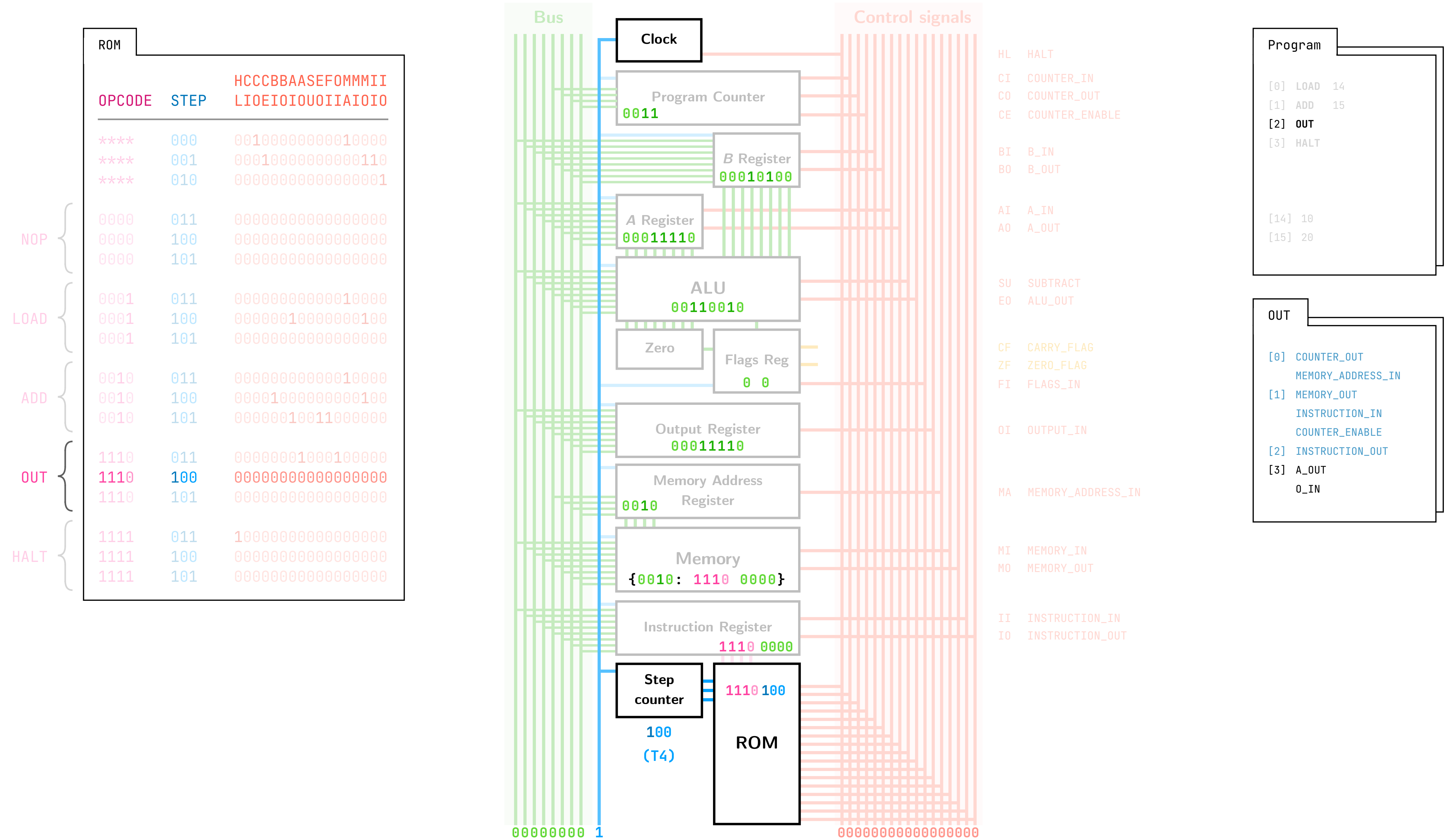





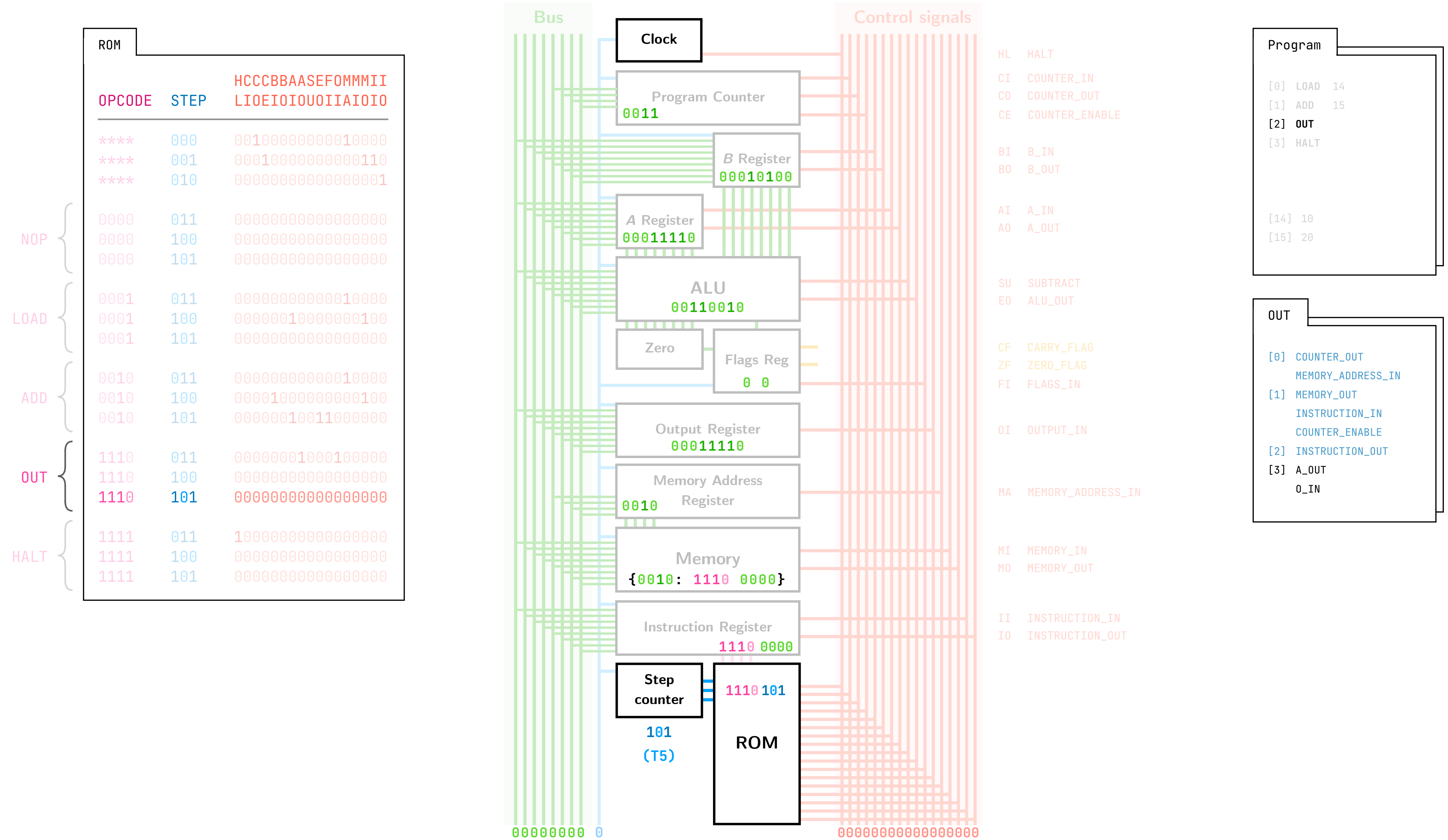


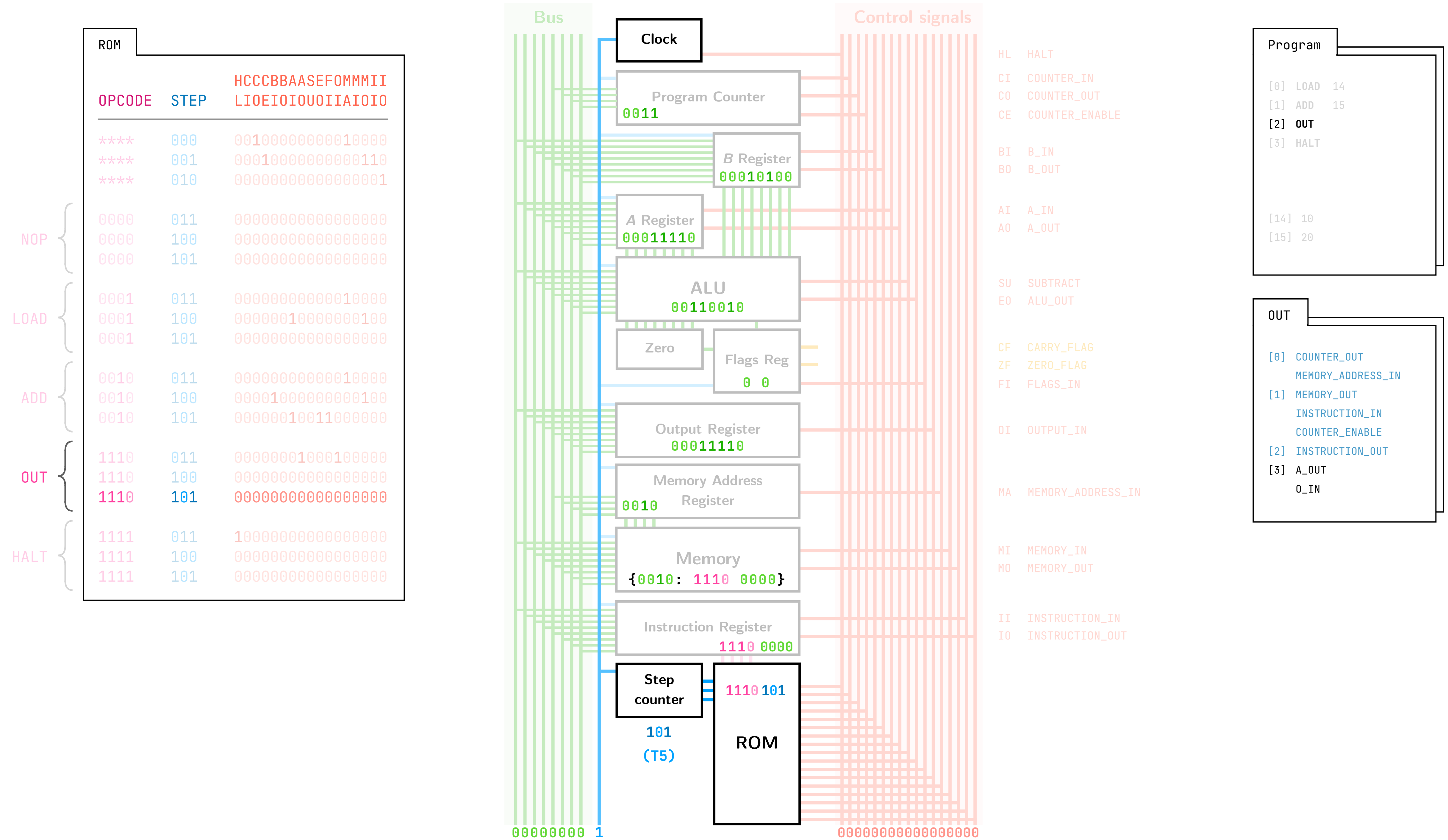


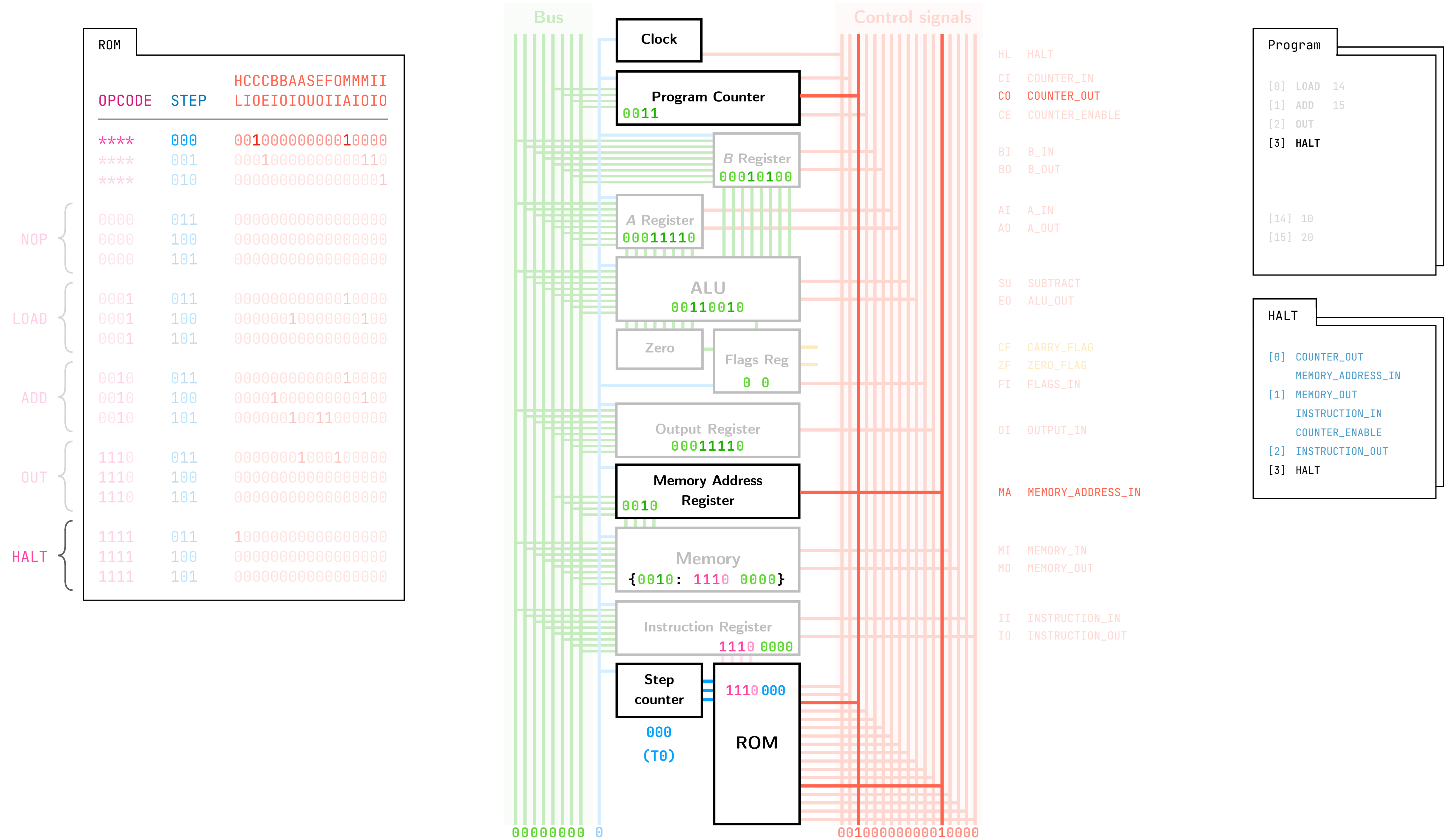

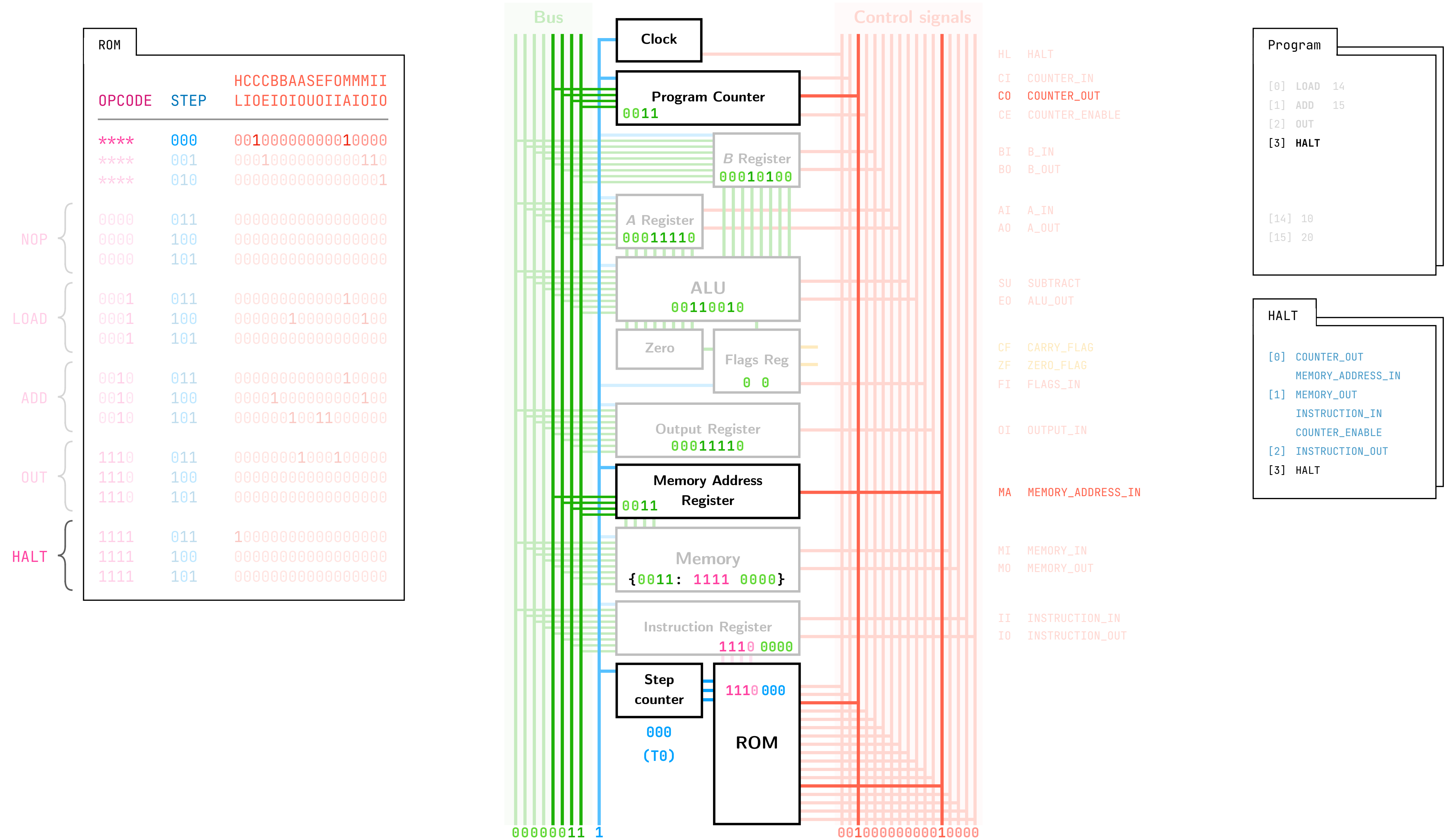


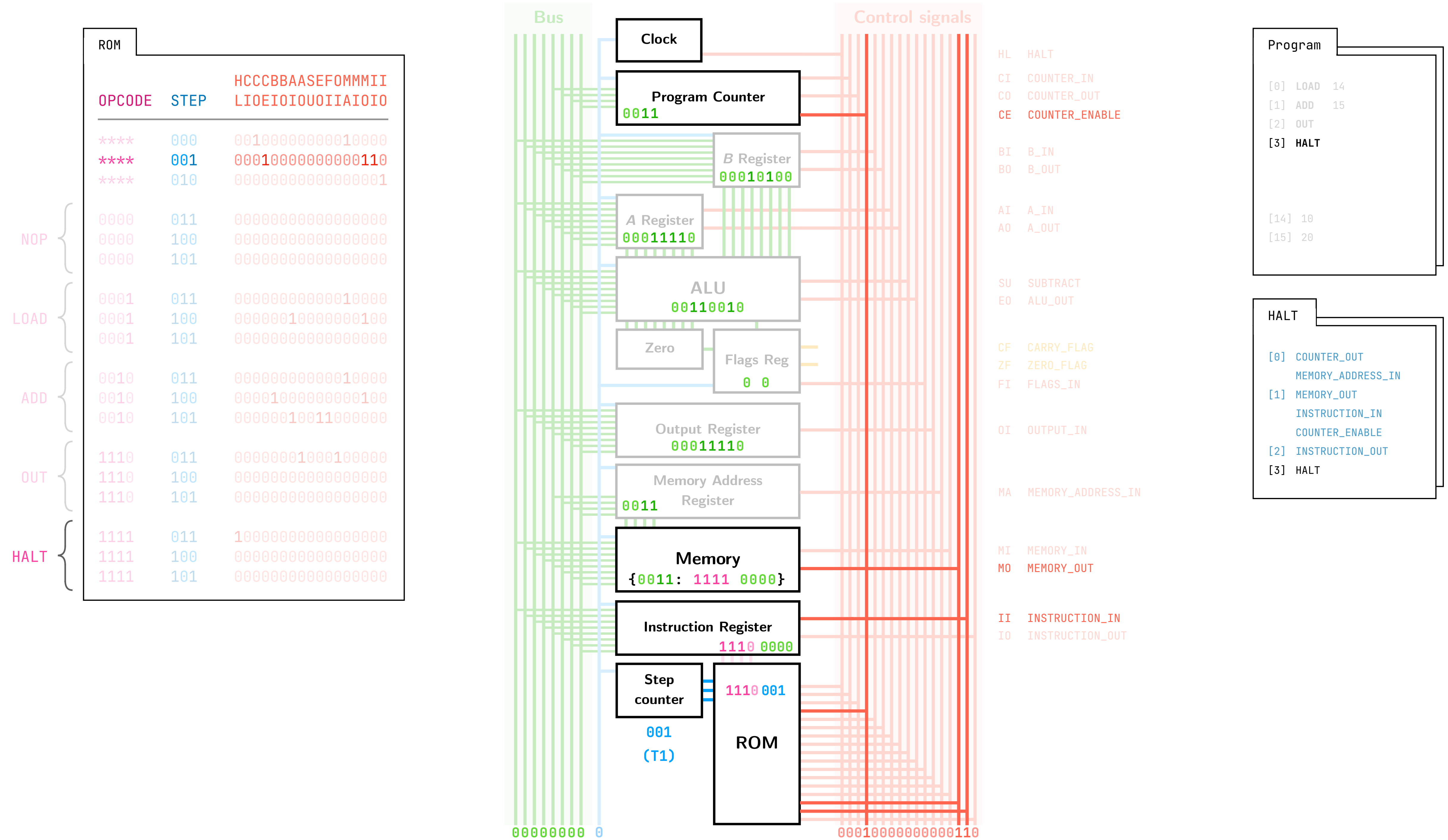

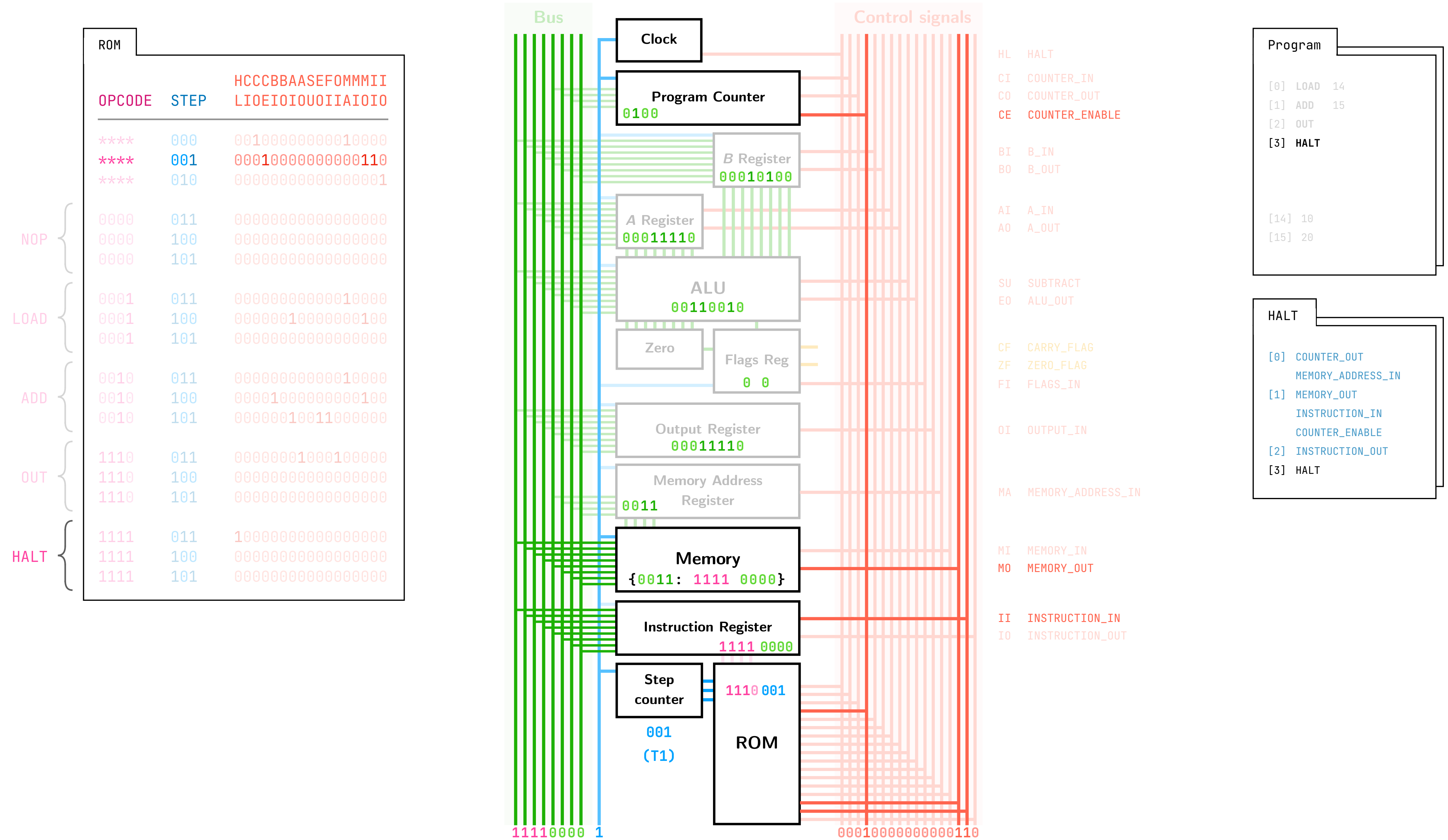

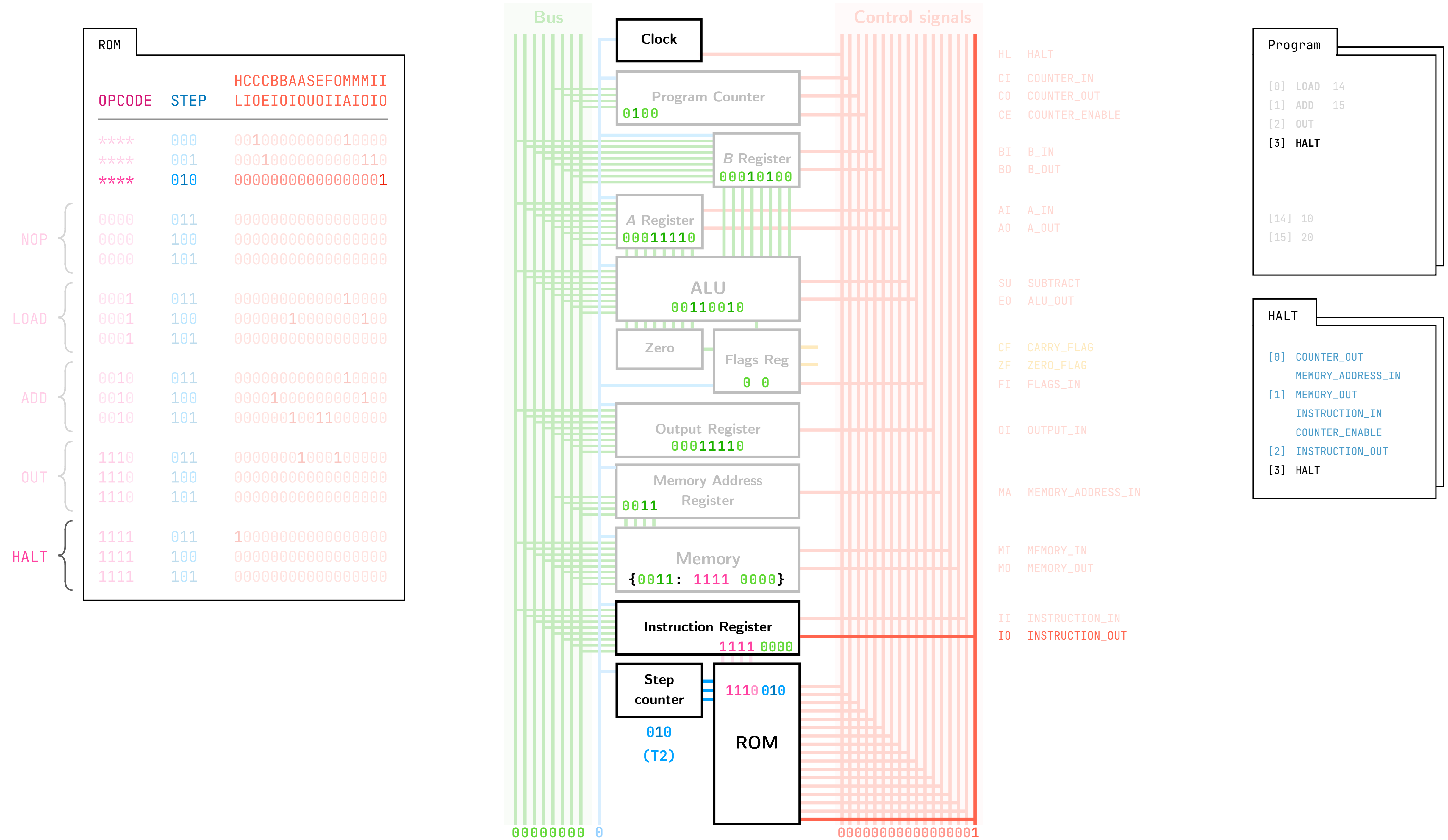

ROM		
OPCODE	STEP	HCCCBBAASEFOMMMII LIOEIOIOUOIIAIOIO
****	000	00100000000010000
****	001	00010000000000110
****	010	00000000000000001
NOP	011	00000000000000000
	100	00000000000000000
	101	00000000000000000
LOAD	011	00000000000010000
	100	00000010000000100
	101	00000000000000000
ADD	011	00000000000010000
	100	00001000000000100
	101	00000010011000000
OUT	011	00000001000100000
	100	00000000000000000
	101	00000000000000000
HALT	011	10000000000000000
	100	00000000000000000
	101	00000000000000000

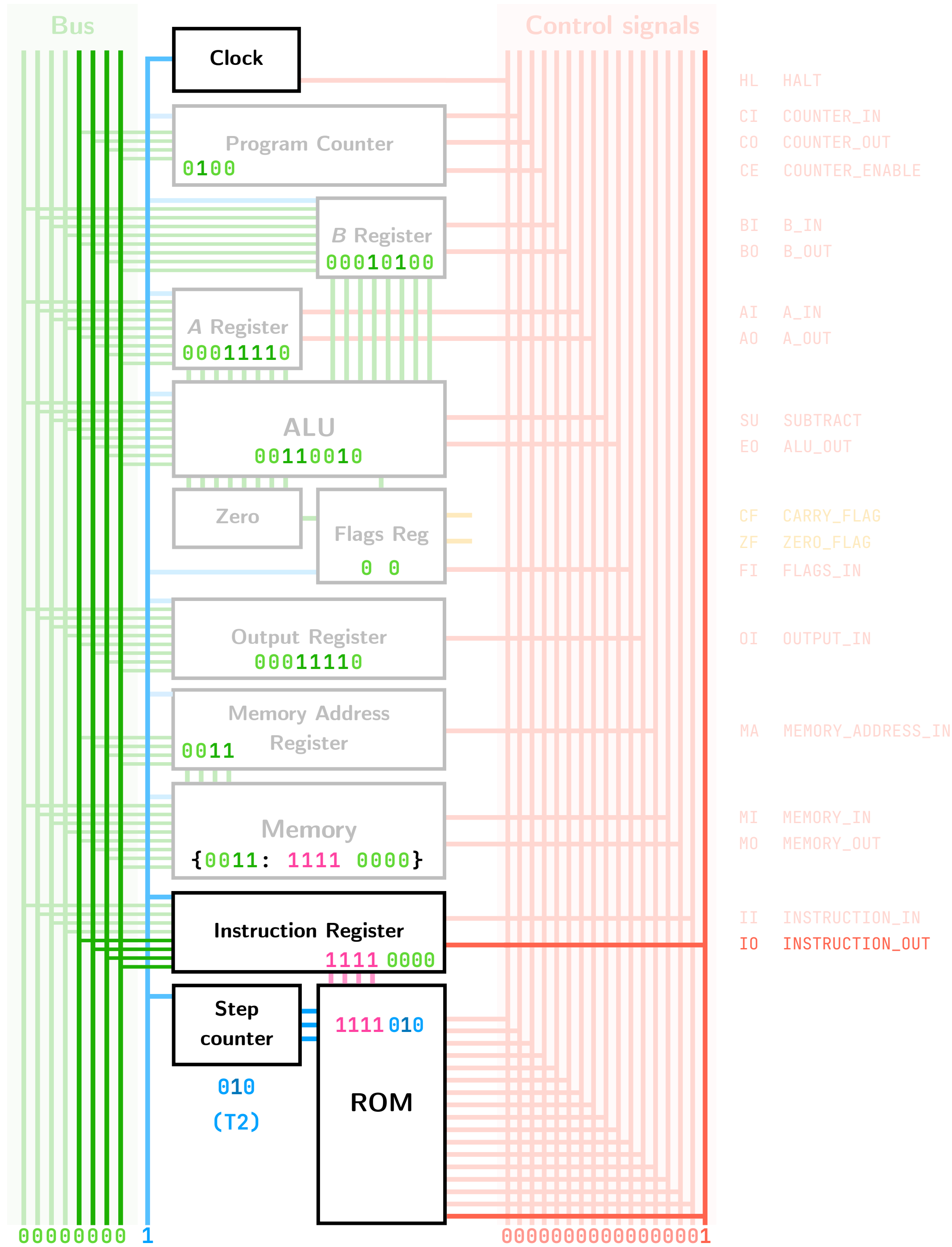


Program		
[0]	LOAD	14
[1]	ADD	15
[2]	OUT	
[3]	HALT	
[14]	10	
[15]	20	

HALT		
[0]	COUNTER_OUT	MEMORY_ADDRESS_IN
[1]	MEMORY_OUT	INSTRUCTION_IN
[2]	INSTRUCTION_OUT	COUNTER_ENABLE
[3]	HALT	


IR can only write last 4 bits to bus →



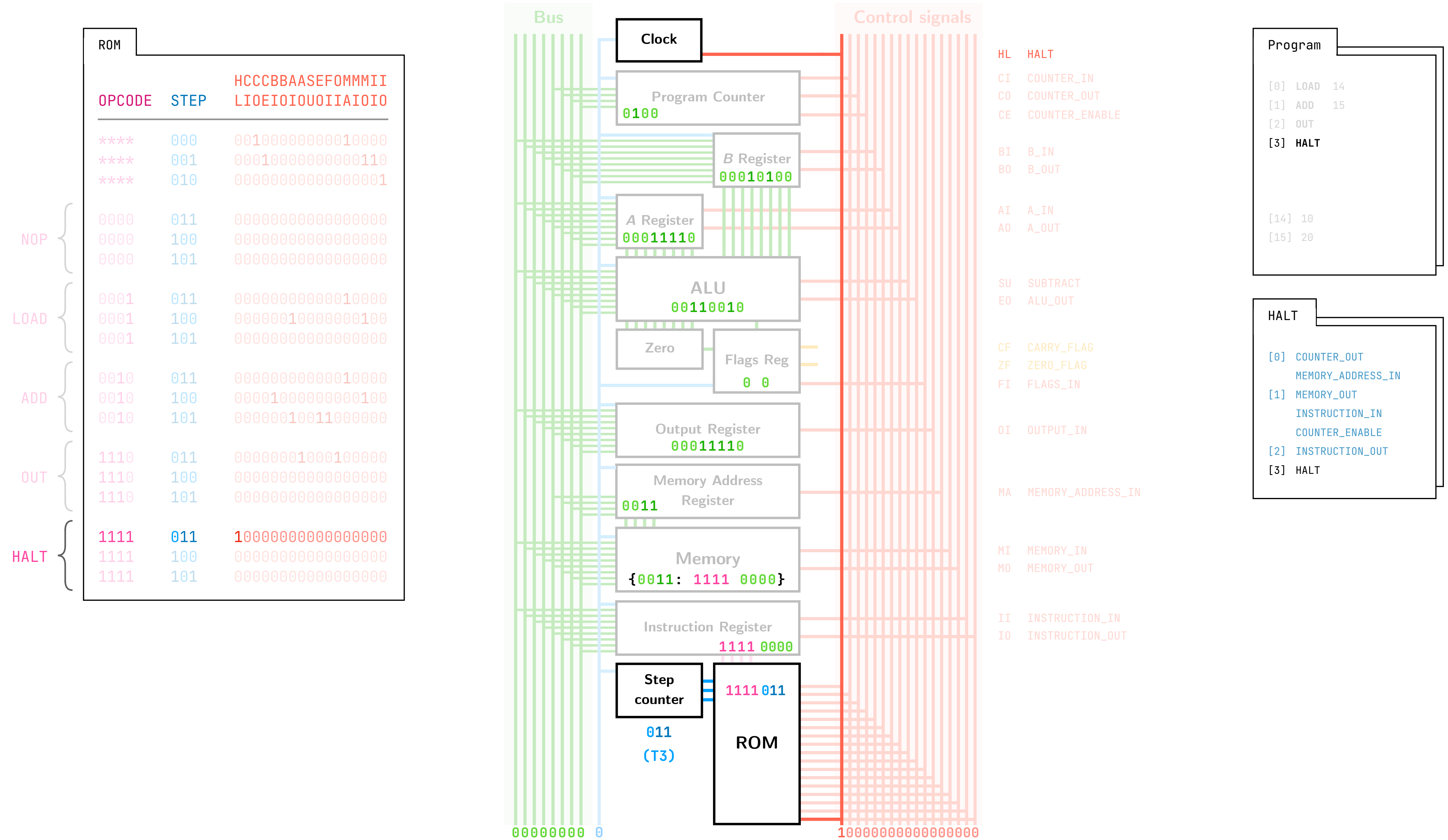

ROM		
OPCODE	STEP	HCCCBBAASEFOMMMII LIOEIOIOUOIIAIOIO
****	000	00100000000010000
	001	00010000000000110
	010	00000000000000001
NOP	011	00000000000000000
	100	00000000000000000
	101	00000000000000000
LOAD	011	00000000000010000
	100	00000010000000100
	101	00000000000000000
ADD	011	00000000000010000
	100	00001000000000100
	101	00000010011000000
OUT	011	00000001000100000
	100	00000000000000000
	101	00000000000000000
HALT	011	10000000000000000
	100	00000000000000000
	101	00000000000000000

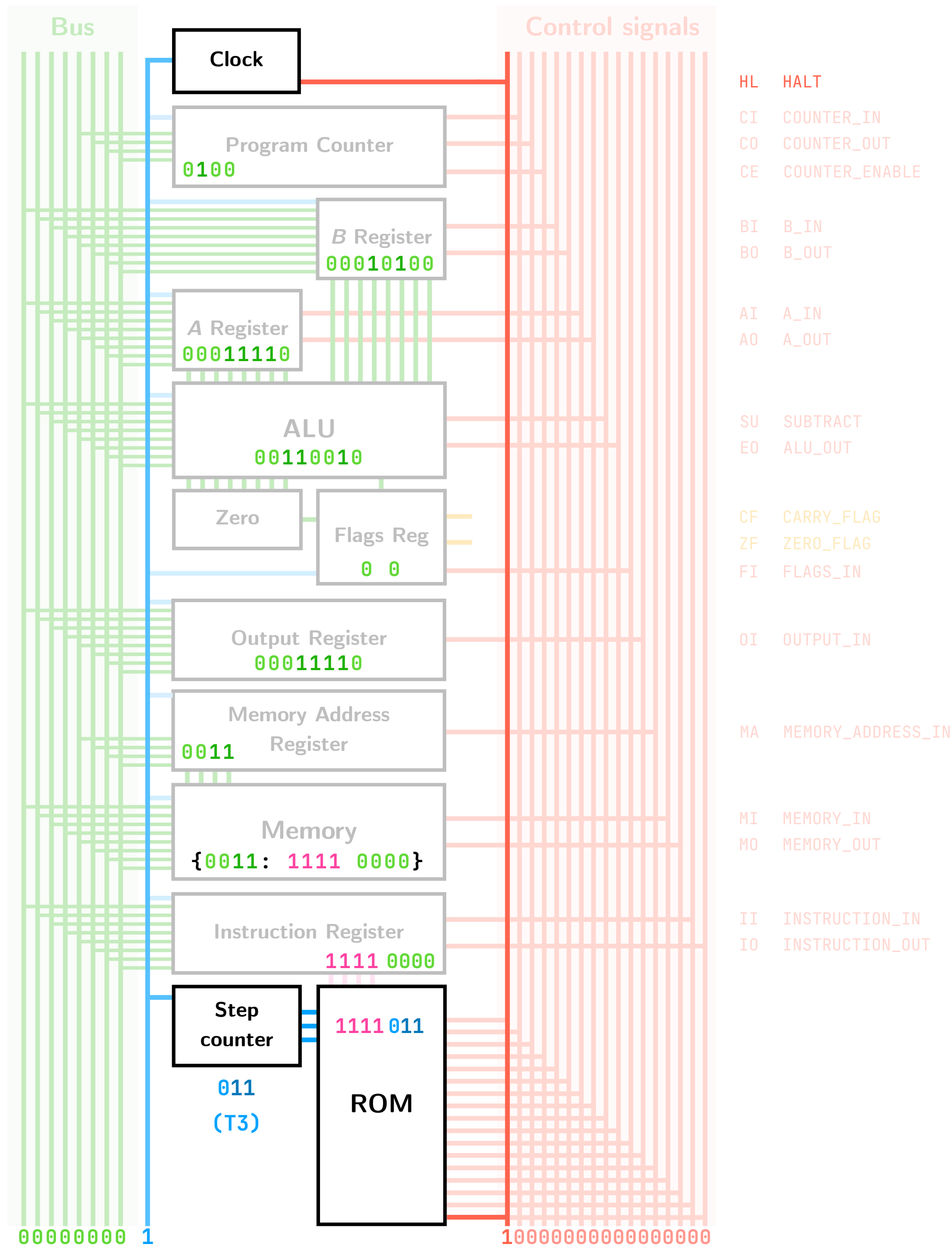Next steps won't happen  
because there is no clock signal  
unless the clock is unhalted



Program		
[0]	LOAD	14
[1]	ADD	15
[2]	OUT	
[3]	HALT	
[14]	10	
[15]	20	

HALT		
[0]	COUNTER_OUT	
[1]	MEMORY_OUT	
[2]	INSTRUCTION_OUT	
[3]	HALT	

**Turing-completeness, conditional jumps and call/return**  
(SAP-2 and SAP-3)

## Conditional jumps

Input to ROM will now be not just [opcode, step] but [**flags**, opcode, step]

so that the control word of a particular instruction at a given step also depends on the flags (e.g. CARRY\_FLAG, ZERO\_FLAG)

most control words will look the same, no matter the flags

but, importantly, not our new instructions:

JZ (jump-if-zero)

JC (jump-if-carry)

you can also add more flags to the control word, e.g. OVERFLOW\_FLAG, NEGATIVE\_FLAG, PARITY\_FLAG,

and define more conditional jump instructions, e.g. other common ones are:

JNZ (jump-if-not-zero)

JNC (jump-if-no-carry)

JE (jump-if-equal)

JNE (jump-if-not-equal)

JG (jump-if-greater)

JGE (jump-if-greater-or-equal)

JL (jump-if-less)

JLE (jump-if-less-or-equal)


JG (jump-if-parity)


conditional jumps are often used right after a CMP (comparison) instruction, in order to set the flag value based on the result of the comparison

the CMP is simply a subtraction without storing the result anywhere, but crucially—like an ordinary subtraction—setting the flags

the result of a subtraction tells us if the first argument is less than, equal to or greater than the second argument

Flags are now connected to ROM!

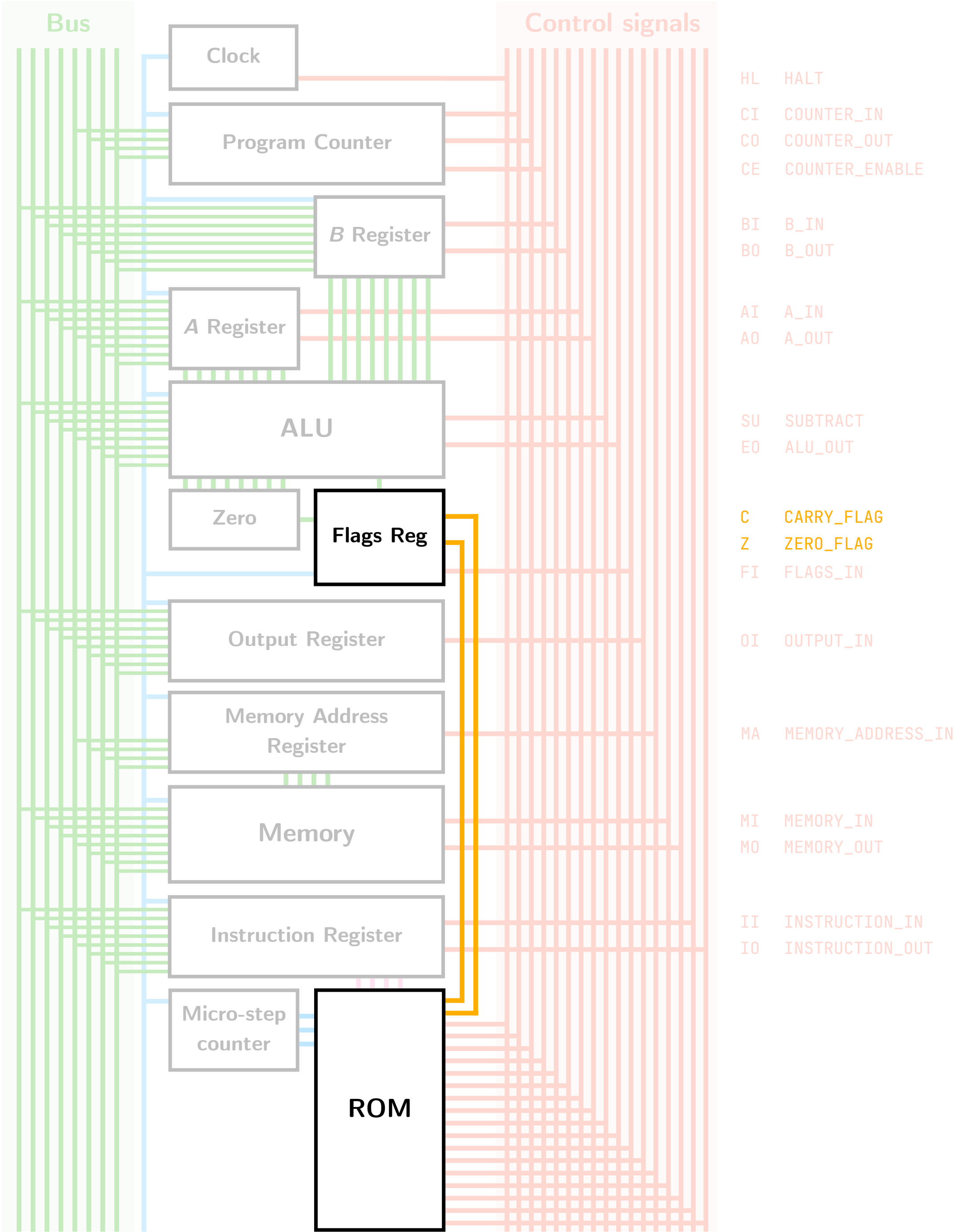

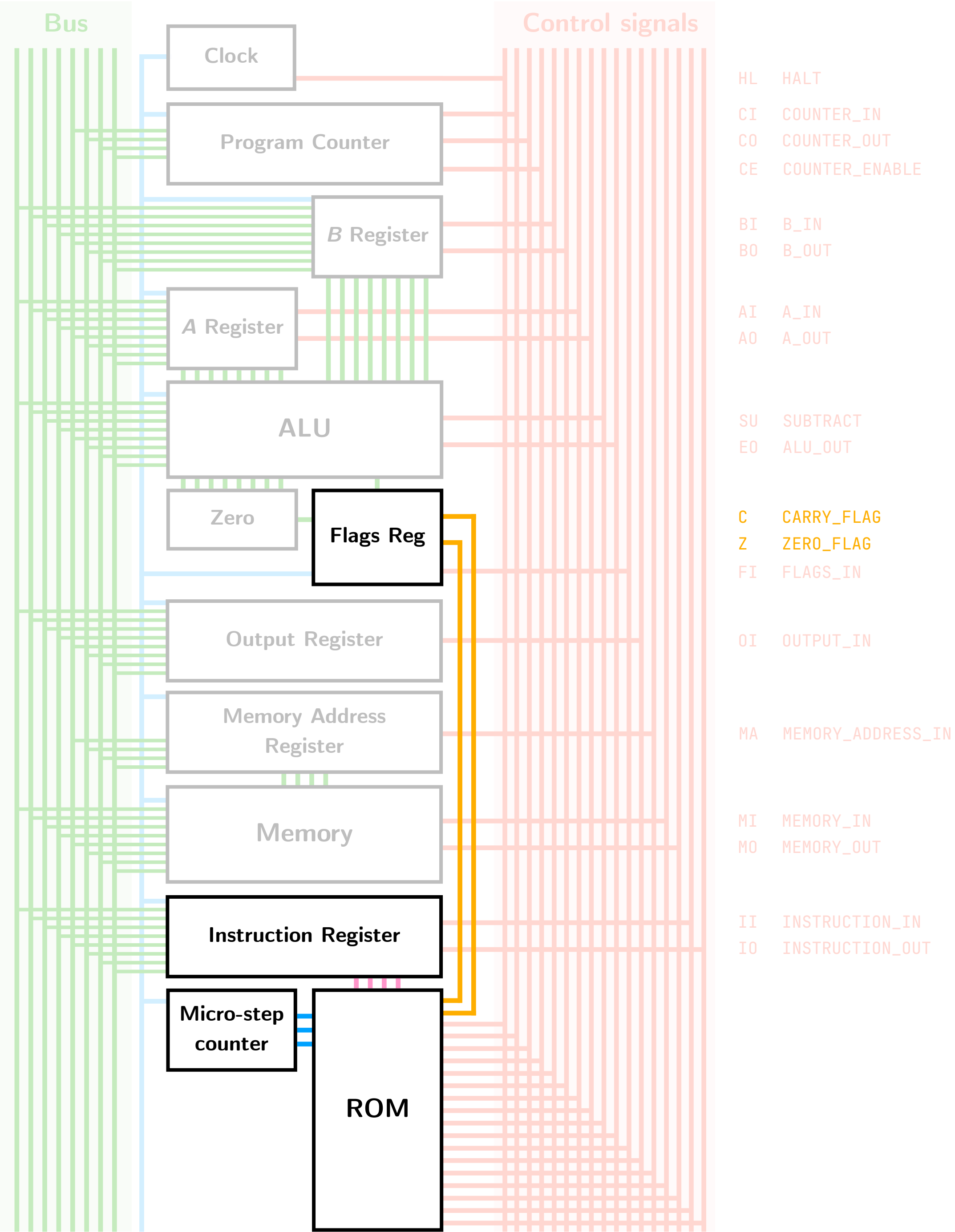

Flags are now connected to ROM!

[flags, opcode, step] → control\_word

!!																											
Mnemonic	Opcode				Step			Flags		Control word																	
								CARRY_FLAG	ZERO_FLAG	HALT	COUNTER_IN	COUNTER_OUT	COUNTER_ENABLE	B_IN	B_OUT	A_IN	A_OUT	SUBTRACT	ALU_OUT	FLAGS_IN	OUTPUT_IN	MEMORY_ADDRESS_IN	MEMORY_IN	MEMORY_OUT	INSTRUCTION_IN	INSTRUCTION_OUT	
Fetch	*	*	*	*	0	0	0	*	*	0	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
	*	*	*	*	0	0	1	*	*	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	1	0
	*	*	*	*	0	1	0	*	*	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
LOAD	0	0	0	1	0	1	1	*	*	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	1
	0	0	0	1	1	0	0	*	*	0	0	0	0	0	0	1	0	0	0	0	0	0	0	1	0	0	
	0	0	0	1	1	0	1	*	*	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	
JMP	0	1	1	0	0	1	1	*	*	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
	0	1	1	0	1	0	0	*	*	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	
	0	1	1	0	1	0	1	*	*	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	
JC	0	1	1	1	0	1	1	0	*	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	0	1	1	1	0	1	1	1	*	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	
	0	1	1	1	1	0	0	*	*	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	
	0	1	1	1	1	0	1	*	*	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	

!!  
!!

**if/else** using a conditional jump

E.g. if the number at memory address 15 is non-negative,  
do something (code1),  
otherwise, do something else (code2),  
afterwards, continue with the rest of the program (code3)

.asm

```
[0]  load  15      } check condition
[1]  cmp   0      } and set flags
[2]  jc    5      } jump to else block
                        if carry flag
[3]  <code1>
[4]  jmp   6      } jump outside of
                        if/else block
[5]  <code2>
[6]  <code3>

[15] 5
```

Pseudocode

```
[15] ← 5
A ← [15]
if CF = 0 then
    ; true if A ≥ 0
    <code1>
else
    ; true if A < 0
    <code2>
end if
<code3>
```

Pseudocode

```
let x ← 5
if x ≥ 0 then
    <code1>
else
    <code2>
end if
<code3>
```



do...while using a conditional jump

E.g. Integer multiplication using addition, subtraction and a conditional jump  
We simply use the first number as a counter,  
and then add the second number to itself and subtract 1 from the counter  
repeatedly until the counter hits 0.

.asm

```

    ; start loop
[0] load 13
[1] add 15
[2] store 13
[3] load 14
[4] sub 1
[5] store 14
[6] jz 8 ; jump out of loop
[7] jmp 0 ; jump to start
    ; end loop
[8] <more code>

[13] 0 ; intermediate result
[14] 5 ; mul1 (counter)
[15] 20 ; mul2
```

Pseudocode

```

do
    ; add mul2 to intermed.
    ; result
    A ← [13]
    A ← A + [15]
    [13] ← A
    ; subtract counter:
    A ← [14]
    A ← A - 1
    [14] ← A
while ZF != 0
<more code>
```

Pseudocode

```

let result ← 0
let counter ← 5
do
    result ← result + x
    counter ← counter - 1
while counter != 0
<more code>
```

**do...while** using a conditional jump

General pattern

.asm

```
    ; start loop
[0] <code>
    ; by this point, flag must
    ; reflect the desired condition
[1] jz    3      ; jump out of loop
[2] jmp   0      ; jump to start
    ; end loop
[3] <more code>
```

Pseudocode

```
do
    <code>
while <flag condition>
    <more code>
```

Pseudocode

```
do
    <code>
while <condition>
    <more code>
```

**while** using a conditional jump

General pattern

.asm


```
[0] <code before loop>
    ; by this point, flag must
    ; reflect the desired condition
    ; start loop
[1]  jz    4          ; jump out of loop
[2]  <code>
    ; by this point, flag must
    ; reflect the desired condition
[3]  jmp   1          ; jump to start
    ; end loop
[4]  <more code>
```

Pseudocode

```
<code before loop>
while <flag condition>
    <code>
end while
<more code>
```

Pseudocode
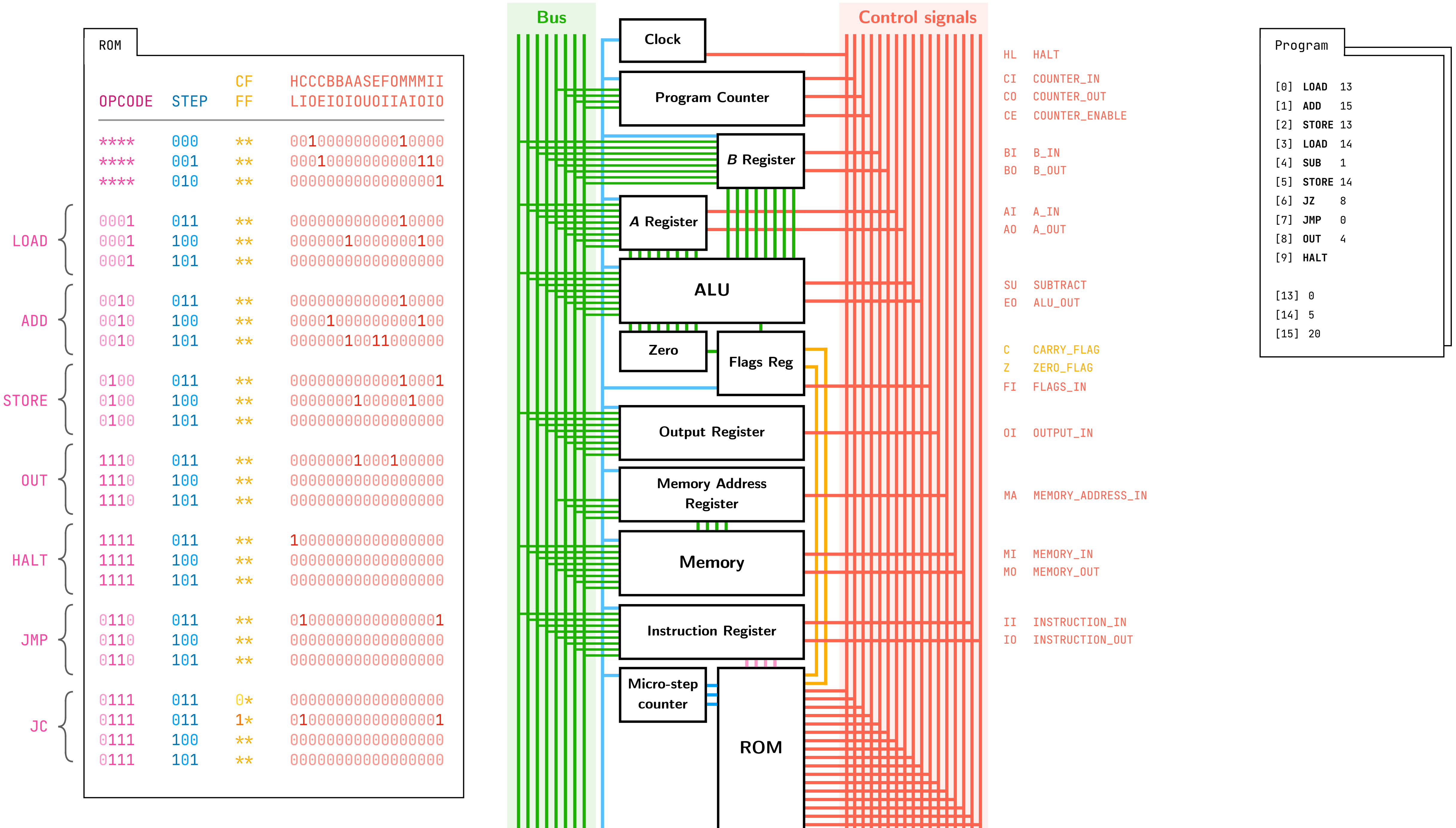
```
<code before loop>
while <condition>
    <code>
end while
<more code>
```



ROM			
OPCODE	STEP	CF FF	HCCCBBAA SEFOMMMI LIOEIOIO UOIIAIOIO
****	000	**	00100000000010000
****	001	**	00010000000000110
****	010	**	00000000000000001
LOAD	011	**	000000000000010000
	100	**	000000100000000100
	101	**	000000000000000000
ADD	011	**	000000000000010000
	100	**	000010000000000100
	101	**	000000100110000000
STORE	011	**	000000000000010001
	100	**	00000001000001000
	101	**	000000000000000000
OUT	011	**	00000001000100000
	100	**	000000000000000000
	101	**	000000000000000000
HALT	011	**	100000000000000000
	100	**	000000000000000000
	101	**	000000000000000000
JMP	011	**	010000000000000001
	100	**	000000000000000000
	101	**	000000000000000000
JC	011	0*	000000000000000000
	011	1*	010000000000000001
	100	**	000000000000000000
	101	**	000000000000000000

- HL    HALT
- CI    COUNTER\_IN
- CO    COUNTER\_OUT
- CE    COUNTER\_ENABLE
- BI    B\_IN
- BO    B\_OUT
- AI    A\_IN
- AO    A\_OUT
- SU    SUBTRACT
- EO    ALU\_OUT
- C     CARRY\_FLAG
- Z     ZERO\_FLAG
- FI    FLAGS\_IN
- OI    OUTPUT\_IN
- MA    MEMORY\_ADDRESS\_IN
- MI    MEMORY\_IN
- MO    MEMORY\_OUT
- II    INSTRUCTION\_IN
- IO    INSTRUCTION\_OUT

Program		
[0]	LOAD	13
[1]	ADD	15
[2]	STORE	13
[3]	LOAD	14
[4]	SUB	1
[5]	STORE	14
[6]	JZ	8
[7]	JMP	0
[8]	OUT	4
[9]	HALT	
[13]	0	
[14]	5	
[15]	20	

Assembly

“Assembly” is not a single programming language like C or Python  
Each CPU has its own specific assembly language corresponding to how that CPU works  
and the corresponding assembler assembles that assembly code into the machine code for that particular CPU

\*.asm

[0]   loadi   3

[1]   store   15

[2]   loadi   0

[3]   addi    15

[4]   out

[5]   jmp     3

Assembler  
→

\*

0101  0011

0110  1111

0101  0000


0010  1111

1110  0000

0110  0011

Executable!

Our instruction format:

 

### Assembly

There are many more ways to make things easier for us by writing a better assembler:

- **Comments:** they make our assembly scripts more understandable, and can simply be ignored by the assembler, and so it doesn't affect the executable binary at all.
- **Labels:** instead of using specific memory addresses in our scripts, we can use labels for positions in our code, and then have the assembler figure out appropriate memory addresses.

Assembly

Let's quickly look at **labels**.

We now longer care about specific addresses in memory.

We simply give a line in our code a name ("label") and then we use the label to, say, jump to whatever address corresponds to it, or to get data from memory.

\*.asm

[0]   mov     a, 5

[1]   call    3

[2]   mov     a, 1

[3]   add     2

[4]   ret

subroutine

Assembly

Let's quickly look at **labels**.

We now longer care about specific addresses in memory.

We simply give a line in our code a name ("label") and then we use the label to, say, jump to whatever address corresponds to it, or to get data from memory.

\*.asm

[0]   **mov**     a, 5

[1]   **call**    3               wrong address!

[2]   **call**    3               wrong address!

[3]   **mov**     a, 1

[4]   **add**     2               subroutine

[5]   **ret**



Assembly

Let's quickly look at **labels**.

We now longer care about specific addresses in memory.

We simply give a line in our code a name ("label") and then we use the label to, say, jump to whatever address corresponds to it, or to get data from memory.

\*.asm

[0] mov a, 5

[1] call 4

[2] call 4

[3] mov a, 1

[4] add 2

[5] ret

fix manually!

fix manually!

subroutine

Assembly

Let's quickly look at **labels**.  
We now longer care about specific addresses in memory.  
We simply give a line in our code a name ("label") and then we use the label to, say, jump to whatever address corresponds to it, or to get data from memory.

\*.asm

```
main:  mov    a, 5
       call   foo
       mov    a, 1
foo:   add     2
       ret
; this is a comment
```

subroutine

Assembler  
(Label resolution)  
→

\*.asm

```
[0]  mov    a, 1
[1]  call   3
[2]  mov    a, 1
[3]  add     2
[4]  ret
```